

TSEA44: Computer hardware – a system on a chip

Lecture 6: Design for FPGAs


Material by Andreas Ehliar

Today

- Influence of goal hardware on architecture and code style
- Motivation
 - Clock speed
 - Area
 - Power
- Target FPGA architecture: Xilinx FPGA with 4-input LUTs
 - Same as VirtexII used in lab
 - Later generations use 6-input LUTs, but same ideas can be used

Clock cycle constraints effects on result

 Comparison of actual performance versus requested performance for various timing constraints



To get the best out of the FPGA


- Understand the architecture
- Use suitable descriptions
- Use available tools to extract implementation information
 - FPGA editor
 - Floorplanner
 - PlanAhead
 - Datasheets
 - Timing reports

FPGA components

- CLB:s
 - Slices
 - LUT
- Hard blocks
 - Block memory
 - Multipliers
 - I/O units


1/2 slice (total 8 of these in one CLB)

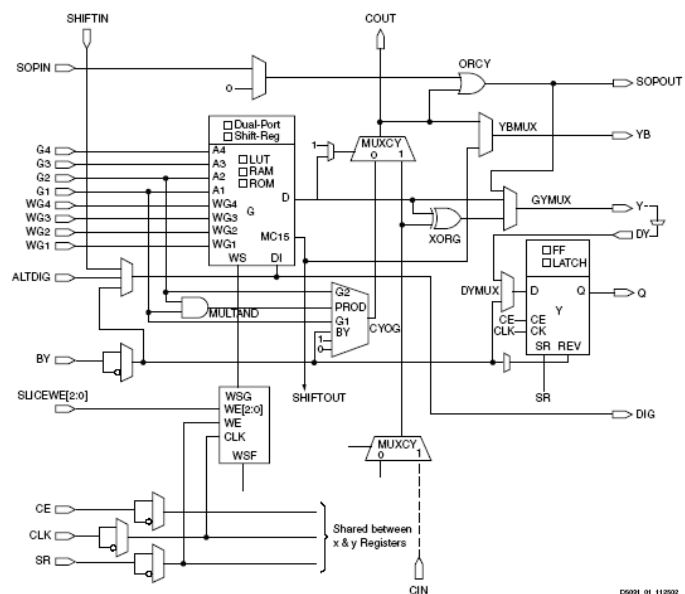- Note
 - 4-input LUT G
 - XORG
 - CYOG
 - MUXCY
 - MULTAND




Combinatorial logic using a LUT

 - 4 inputs give any logic function of at most 4 inputs




Adders and carrychains in Xilinx FPGAs

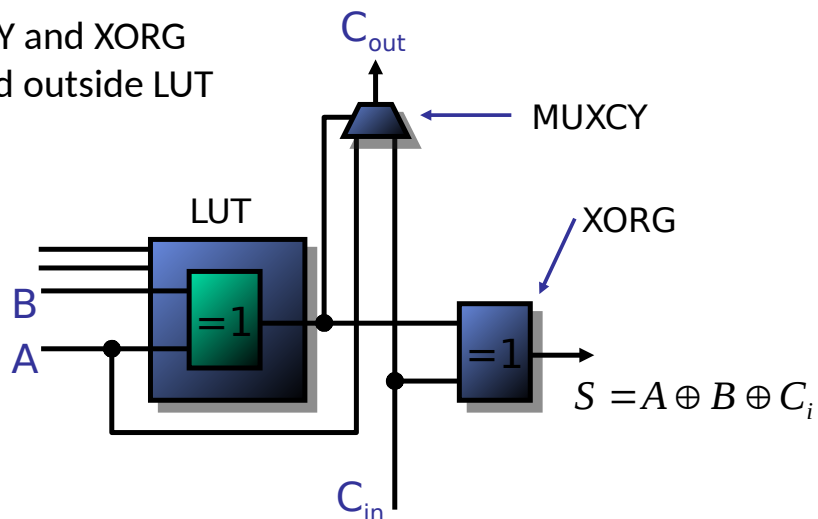- 1 fulladder structure using carry chain acceleration
 - MUXCY and XORG located outside LUT
- 1 LUT/bit




Extend to Add/subtract in Xilinx FPGAs

- Still one unused input to the LUT

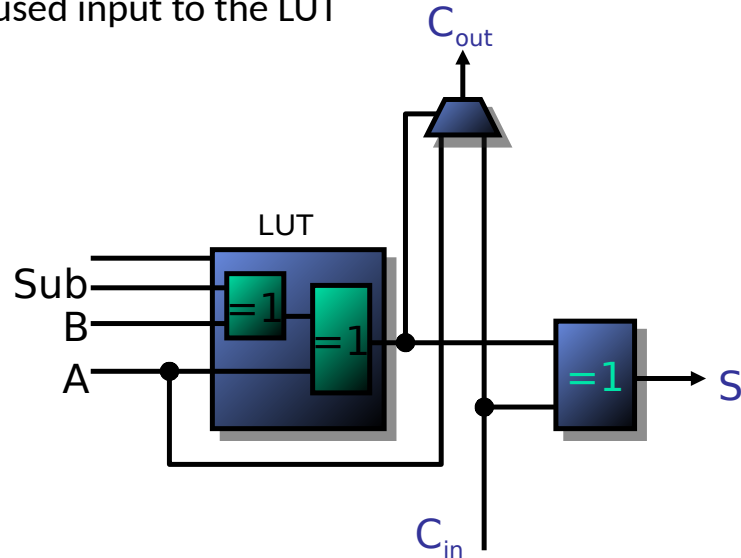


Rule of thumb for efficient adders in 4-input LUT based FPGAs

 - $S = a + K(b,c,d)$
- Plain adder
- Adder/subtractor
- 2-to-1 mux and adder
- More strange versions
 - $S = (opb \mid opc \mid opd) + opa$
 - $S = (opb \& opc) + (opb \& opa)$
(Uses MULT_AND located under LUT in slice figure)




Carry chain for other purposes: Comparators

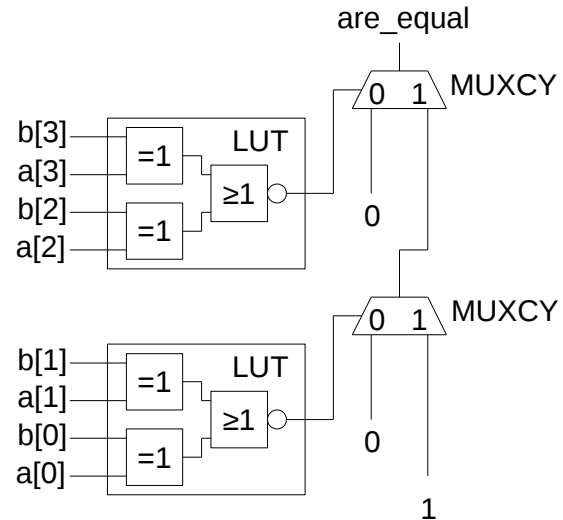- Compare 2 bits per LUT
- Compare 4 bits per LUT if one value is constant!




Carry chain drawbacks

 - Example: Address calculation selecting one byte memory



WE delayed by carry chain

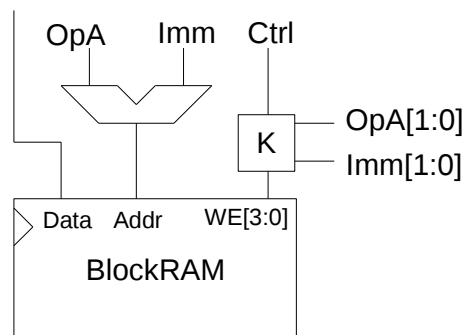


2-bit adder in K using 1 LUT gives faster implementation

- The carry chain itself is extremely fast
- Getting on the chain is not very fast

Multiplexers in FPGAs


- A big difference between ASIC and FPGAs: Multiplexers are cheap in ASIC and expensive in FPGAs
- 4-input LUT: One 2-to-1 mux
- Specialized multiplexers in the slices are used to combine LUTs into larger multiplexers

Multiplexers in Xilinx FPGAs

 

- Possible use of spare input:
 - Invert output, set output to one or zero
 - Tricky variants based on a, b, and s[0]
- How many 4-input LUTs needed for a 4-to-1 mux (without MUXFx components)?

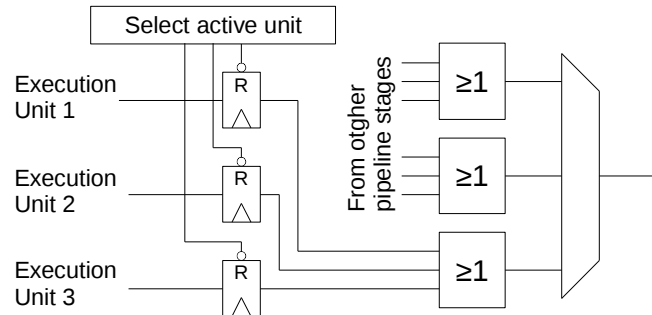Avoiding multiplexers in pipelined designs




- Multiplexers are costly in FPGAs
- Alternative 1: Use or gates and make sure unused inputs are set to 0 using reset input of flip-flops
- Alternative 2: Use and gates and make sure unused inputs are set to 1. (see MULT_AND as well!)

Memory guidelines


- Standard rule: Large memories should be synchronous
- For high frequency design you want to register the output of the memory as well.
- For power reasons you should not enable the memory unless necessary
 - Double check that your enables work when inferring a memory!
- Smaller memories may be asynchronous if necessary
- You should not have a reset signal for your memory array
 - Easy to forget for shift registers!

Memories larger than one BlockRAM

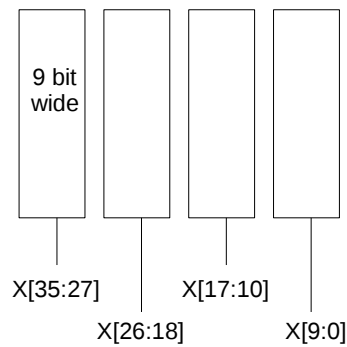72 kilobit using 4 BlockRAMs that are 9 bits wide



 72 kilobit using 4 BlockRAMs that are 36 bits wide




- Why use the right variant? Reduced power consumption!

A case study: A divider for a RISC processor

- Used in a 32-bit RISC processor
- Target frequency: 320 MHz in a Virtex-4 (speedgrade -12)
- Uses restoring division algorithm (basic operations are shift, subtract, and select)
 - Serial computation
 - Very similar to manual division


$$\frac{\text{dividend}}{\text{divisor}} = \text{quotient} \times \text{divisor} + \text{remainder}$$

Initial divider architecture

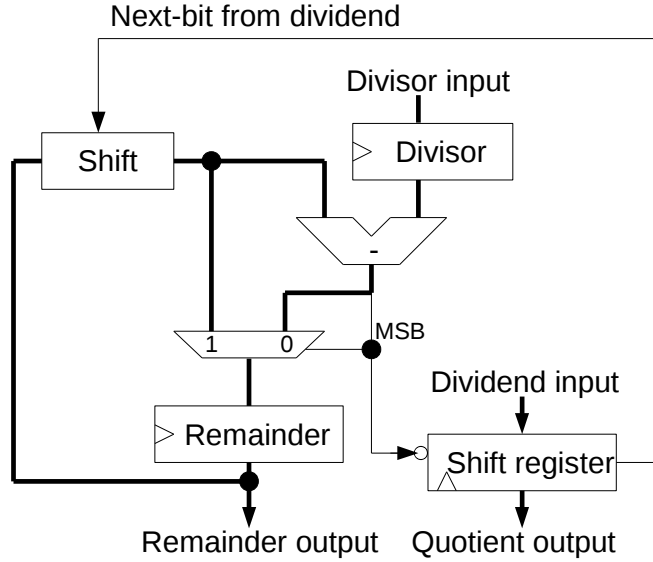

Initial divider architecture


Initial speed:
300 MHz

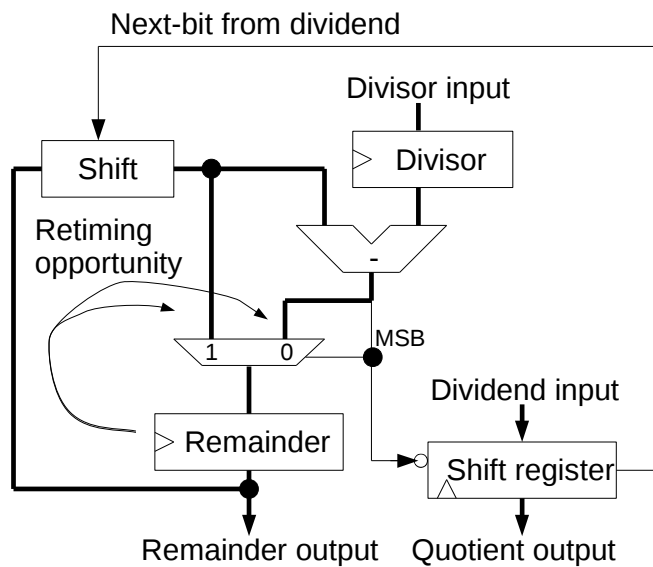

Issues

- Cannot combine subtracter and 2-to-1 multiplexer!
- Solution: Preprocess divisor and use an addition instead

Retimed and using adder

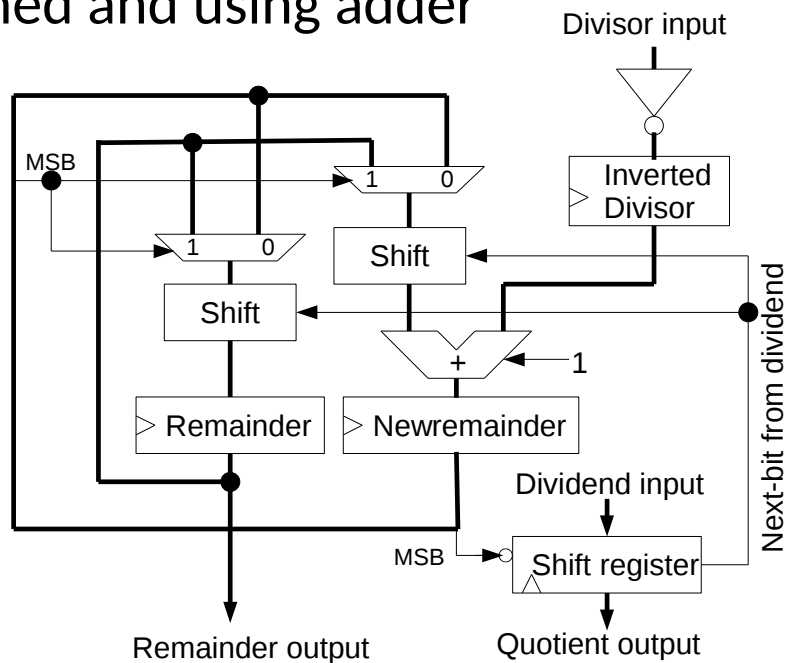


Other issues

- Synthesis tool was too clever
- Manually instantiating the components worked
- Alternatively a complete rewrite of the module worked as well
- Improves clock frequency to 377 MHz (from 300 MHz)


Dealing with negative numbers

- Idea: Take absolute value of dividend and divisor
- Negate quotient and remainder if necessary
- For a 32 bit divider this seems to require around 128 extra LUTs...

Absolute value for divisor

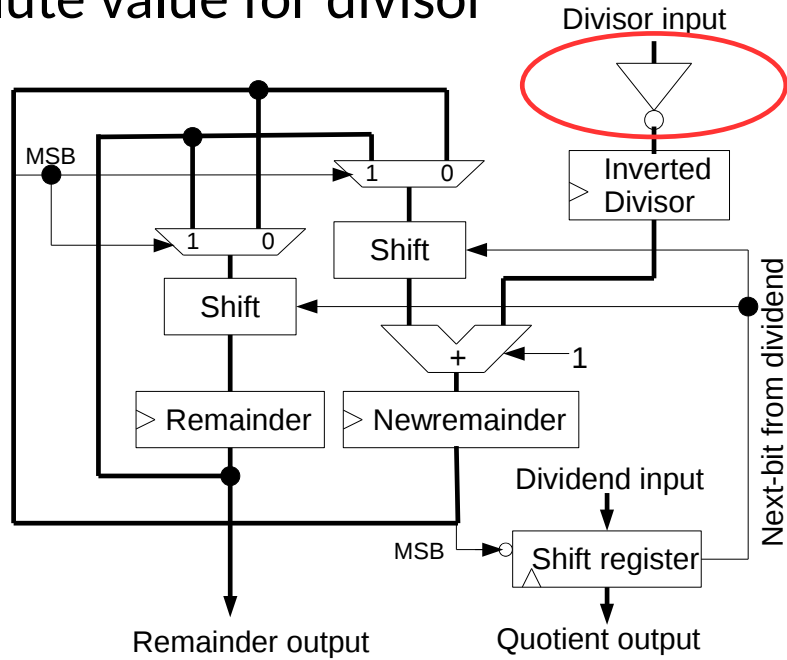

Absolute value for dividend

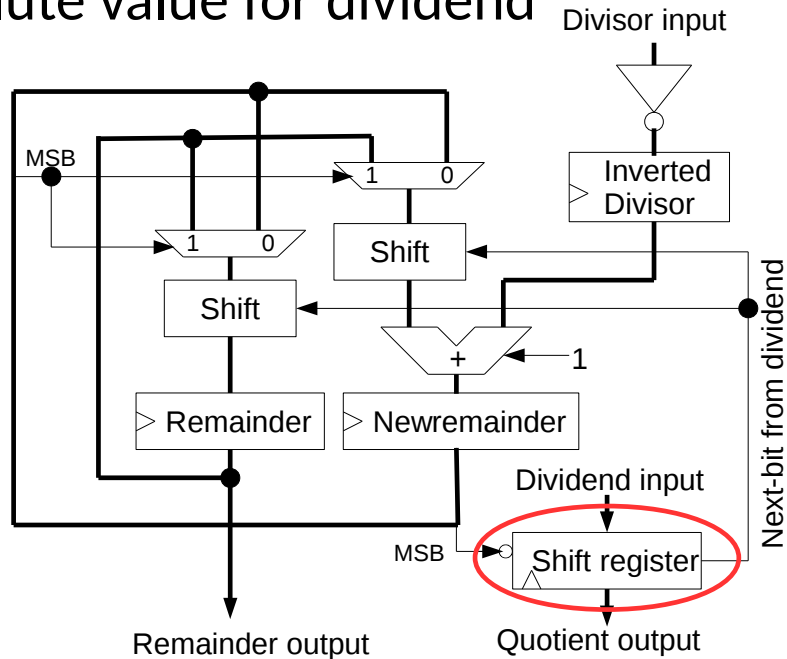

Tricky to do in practice

- Required signals for shift register:
 1. Load enable/shift enable
 2. Invert enable
 3. Input data of new dividend
 4. Input data of new dividend (MSB bit)
 5. Current value of register
- 5 inputs to a 4 input LUT?

Tricky to do in practice - Solution

- Solution: Skip MSB of dividend input for ABS operation
- Always invert the dividend, only add 1 as a carry in if appropriate
 - This can be implemented by adding a few extra LSB bits
 - If we had a positive value we can compensate for the inversion at shift out
 - We can even add a control bit to select between signed/unsigned division
- Manual instantiation was necessary to actually implement this

Results for Virtex-4, speedgrade 12

- Unoptimized, unsigned: 300 MHz, 107 LUTs
- Retimed, unsigned: 377 MHz, 140 LUTs
- Retimed, signed: 361 MHz, 151 LUTs
- Retimed, signed or unsigned: 363 MHz, 153 LUTs

Manual instantiation

- Last resort when synthesis attributes and rewriting the RTL code does not work
- Not portable between FPGA vendors
 - Surprisingly portable to ASIC however

Manual instantiation of flip-flops

- Allows you to ensure that the correct signals are corrected to the D, CE, and SR inputs
 - XST (Xilinx own synthesis tool, not used in the lab) often seem to select the wrong input for SR
 - Background: SR input is quite slow compared to D input
- Can sometimes be avoided by rewriting the code or using synthesis attributes
- Often easier to just instantiate flip-flop primitives directly

Manual instantiation of Memories and DSP Blocks

- Well documented in various application notes

Synthesis attributes

- A convenient way to force the synthesis tool to do what you mean
 - In VHDL:

```
attribute keep : string;  
attribute keep of mysignal: signal is "TRUE"
```
 - In Verilog:

```
(* KEEP = "TRUE" *) wire mysignal;
```
 - Note: Synthesis attributes discussed here are for XST, not Precision!
 - (Read the Precision manual)
-

Synthesis attribute KEEP

- Preserves the selected signal
 - Use case:
 - The synthesis tool makes a bad optimization decision.
 - By using KEEP you can ensure that a certain signal is not hidden inside a LUT and hence guide the optimization process
-

KEEP example from a display controller

```

wire inimagey = (yctr > 31) && (yctr < 192);
wire inimagex = (xctr > 15) && (xctr < 26);
...
always @(posedge clk) begin
  if (inimagey && (xctr == 15) ) begin
    ...
  end else if(inimagey && (xctr == 26)) begin
    ...
  end else if(inimagey && (xctr == 15) ) begin
    ...
  end else if(inimagey && (yctr[2:0] == 7)) begin
    ...
  end
end

```

- Problem: Synthesis tool merged inimagey test with other tests in suboptimal way

Solution: Force inimagey and inimagex to be separate signals

```

(* KEEP = "TRUE" *) wire inimagey;
(* KEEP = "TRUE" *) wire inimagex;

assign inimagey = (yctr > 31) && (yctr < 192);
assign inimagex = (xctr > 15) && (xctr < 26);


```

- Saved area in an area constrained situation
- Especially important when targetting both CPLD and FPGAs with a single IP core

SIGNAL ENCODING attribute


- Allows you to select encoding for state machines
- Useful when synthesis tool make suboptimal state machine encoding choices
- (Alternatively: You can disable FSM optimization if you **really** want to)

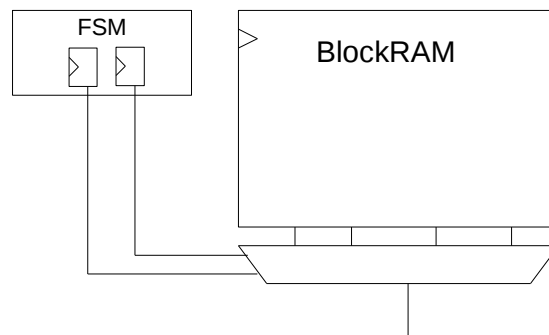Example: Memory byte select in a processor



- Signal encoding specified 2 FF, 4 states.
- Two signals into mux control signal

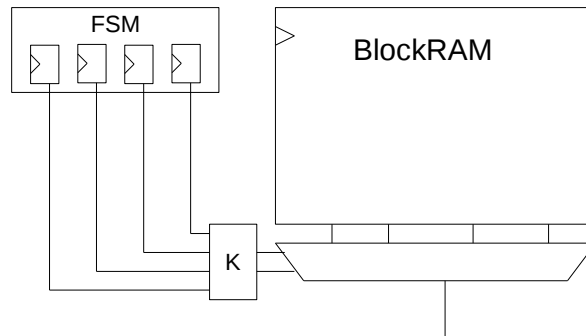Example: Memory byte select in a processor




- Heuristics in the synthesis tool selected one-hot coding for the FSM...

EQUIVALENT REGISTER REMOVAL attribute

- Allows you to specify that certain registers should not be optimized away.
- Perfect when you do not want the synthesis tool to touch your carefully optimized (duplicated) flip-flops


Example: Operand bus in a processor

 

- Problem: Manual register duplication in read operand stage is removed by synthesis tool
- Solution: Disable optimization locally by setting `EQUIVALENT_REGISTER_REMOVAL` to "no"

4-to-1 multiplexer using two LUT4

4-to-1 multiplexer using two LUT4

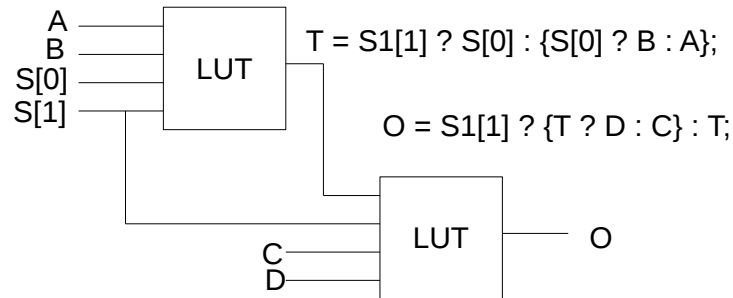

Conclusions

- By mapping your design to the FPGA in an efficient manner you can significantly improve the performance of your design
- Keep this in mind early in the design phase.
- (However, don't optimize unless you really need to.)

www.liu.se

li.u LINKÖPING
UNIVERSITY