

TSEA44: Computer hardware – a system on a chip

Lecture 2: A short introduction to SystemVerilog

(System)Verilog

- Assume background knowledge of VHDL and logic design
- Focus on coding for synthesis
 - Testbenches will be mentioned
- Verilog was initially used for **modelling** of hardware, but later where software created that allowed the model to be synthesized into hardware
 - Adds restrictions on how the code should be written

Practical Issues

- Labs will be in MUX1
 - Schedule update on its way
- 16 computers, all fit in lab?
- If computers stops working (stuck, no respons, unable to login etc.)
 - Contact helpdesk@student.liu.se
 - Include machine name, time, activity
 - Was problems during ht1
- Do not forget to draw block diagrams of your solutions before coding

History of Verilog and SystemVerilog

- 1985 Verilog invented, C-like syntax, initial use: modelling of hardware
 - <- VHDL defined in 1987
- 1995 First standard of Verilog (Verilog-95, IEEE 1364)
- 2001 Extra features added (Verilog-2001, IEEE 1364-2001)
- 2005 Minor extension (Verilog-2005)
- 2005 SystemVerilog standardized (SystemVerilog-2005, IEEE 1800-2005) as an extension to Verilog-2005
- 2009 Merge of SystemVerilog and Verilog (IEEE 1800-2009)

TSEA44: Computer hardware – a system on a chip 2019-11-05 5

Verilog vs VHDL

Verilog-2001 adds a lot of VHDL functionality but still lacks advanced data structures

2001	Architecture configuration	Simple assertions	Dynamic memory allocation	pointers	Associative & Sparse arrays
	Dynamic hardware generation	User-defined types	enums	records/structs	Void type
95	Event handling	Basic datatypes (bit, int, reg, wire...)	Automatic variables	Signed numbers	Strings
	4 state logic	Basic programming (for, if, while...)			
	Hardware concurrency design entity modularization	Gate level modelling and timing			
	Switch level modeling and timing	ASIC timing			

Tom Fitzpatrick, SystemVerilog for VHDL Users, DATE04

TSEA44: Computer hardware – a system on a chip 2019-11-05 7

Synchronization and single pulse

- Asynchronous inputs must be synchronized to the input clock
- Useful: indicate input signal edge detection

```

reg x,y; // variable type (0,1,Z,X)
wire button; // net type (0,1,Z,X)

// SSP
always @(posedge clk) // procedural block
begin
    x <= stb;
    y <= x;
end

assign button = x & ~y; //continuous assignment
    
```

TSEA44: Computer hardware – a system on a chip 2019-11-05 6

SystemVerilog

Constrained Random Data Generation	Program Block	Clocking Domain	Enhanced Scheduling for Testbench and Assertions	Cycle Delays	Sequence Events
Classes, methods & inheritance	Sequential Regular Expressions	Semaphores	Persistent events	Queues	Functional Coverage
Interface Specification	Temporal Properties	Packages	Operator Overloading	Process Control	Virtual Interfaces
Architecture configuration	Simple assertions	Dynamic memory allocation	safe pointers	Associative & Sparse arrays	
Dynamic hardware generation	User-defined types	enums	records/structs	Void type	Further programming (do while, break, continue, ++, --, +=, etc)
Event handling	Basic datatypes (bit, int, reg, wire...)	Automatic variables	Signed numbers	Strings	
4 state logic	Basic programming (for, if, while...)				
Hardware concurrency design entity modularization	Gate level modelling and timing				
Switch level modeling and timing	ASIC timing				
		Packed structs and unions	Coverage & Assertion API	C interface	

SystemVerilog 3.1 provides advanced verification and modeling features

Tom Fitzpatrick, SystemVerilog for VHDL Users, DATE04

TSEA44: Computer hardware – a system on a chip 2019-11-05 8

A variation of the same thing

- Multiple always block

```

reg x,y; // variable type (0,1,Z,X)
wire button; // net type (0,1,Z,X)

// SSP
always @(posedge clk) // procedural block
begin
    x <= stb;
end

always @(posedge clk) // procedural block
begin
    y <= x;
end

assign button = x & ~y;
    
```

Resettable D-flipflop (synchronous)

```
// This is OK
always @(posedge clk)
begin
  x <= stb;
  if (rst)
    x <= 0;
end


// same as
always @(posedge clk)
begin
  if (rst)
    x <= 0;
  else
    x <= stb;
end

// This is not OK
// multiple assignment
always @(posedge clk)
begin
  x <= stb;
end

always @(posedge clk)
begin
  if (rst)
    x <= 0;
end
```

Reg or wire in Verilog

 
- 1) `always ...`
`a <= b & c;`
`reg both`
- 2) `wire both`
`assign a = b & c;`



SystemVerilog: ~~always_{ff, comb, latch}~~

- always blocks does not guarantee capture of intent
- If not edge-sensitive then only a warning if latch inferred
 
```
// forgot else branch
// a synthesis warning
always @(a or b)
  if (b) c = a;
```



- always_ff, always_comb, always_latch are explicit
- Compiler now knows user intent and can flag errors accordingly

```
// compilation error
always_comb
  if (b)
    c = a;

// yes
always_comb
  if (b)
    c = a;
  else
    c = d;
```

SystemVerilog relaxes variable use

- A variable can receive a value from one of these:
 - Any number of always/initial blocks
 - One always_ff/always_comb block
 - One continuous assignment
 - One module instance
- We can skip wire/reg, use logic instead

Signed/unsigned

- Numbers in Verilog (95) are unsigned. If you write


```
// s and d2 4 bits long, d3 5 bit long
assign d3 = s + d2;
```

 s and d3 gets zero-extended

```
wire signed [4:0] d3;
reg signed [3:0] s;
wire signed [3:0] d2;
```

```
assign d3 = s + d2;
```

s and d3 get sign-extended

Blocking vs non-block, combinatorial

```
always_comb begin
  C = A & B;
  E = C | D;
end
```

```
always_comb begin
  C <= A & B;
  E <= C | D;
end
```

Same result

Use = for combinatorial logic

Blocking vs non-blocking, sequential

- Blocking assignment (=)
 - Assignments are blocked when executing
 - The statements will be executed in sequence, one after the other

```
always_ff @(posedge c1k) begin
  B = A;
  C = B;
end
```
- Non-blocking assignment (<=)
 - Assignments are not blocked
 - The statements will be executed concurrently
 - Similar to signals in VHDL

```
always_ff @(posedge c1k) begin
  B <= A;
  C <= B;
end
```

Use <= for sequential logic

Verilog constructs for synthesis

Construct type	Keyword	Notes
ports	input, inout, output	
parameters	parameter	
module definition	module	
signals and variables	wire, reg	Vectors are allowed
instantiation	module instances	E.g., mymux ml(out, iO, il, s);
Functions and tasks	function, task	Timing constructs ignored
procedural	always, if, then, else, case	initial is not supported
data flow	assign	Delay information is ignored
loops	for, while, forever	
procedural blocks	begin, end, named blocks, disable	Disabling of named blocks allowed

Operators

- Note: equal not a single "=" !!!
 - Classic problem with C!

Operator Type	Symbol	Operation
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
		Unary plus
	-	Unary minus
Logical	!	Logical negation
	&&	Logical and
		Logical or
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	inequality

Parameters

```

module w(x,y);
input x;
output y;
parameter z=16;
localparam s=3'h1;
...
endmodule

```

```

w w0(a,b);
w #(8) w1(a,b);
w #(.z(32)) w2(.x(a),.y(b));

```

Operators

- Reduction:
 - return scalar value from vector by pairwise calculation
- Replication
 - {3{a}}
 - same as {a,a,a}

Operator Type	Symbol	Operation
Reduction	~	negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
	~^	xnor
Shift	>>	Right shift
	<<	Left shift
Concatenation	{}	Concatenation
Conditional	?	Conditional

Constants (really substitution macros)



```

`include "myconstants.v"
`define PKMC
`define S0 1'b0
`define S1 1'b1
...
`ifdef PKMC
...
`else
...
`endif

```

Important: It is `, not ' (back tick instead of apostrophe)

Example of an FSM (nextstate + out)

  

```

//NEXT
always_ff @(posedge clk) begin
  if (rst)
    s <= `S0;
  else
    case (s)
      `S0:
        if (x)
          s <= `S1;
        default:
          if (x)
            s <= `S0;
    end
end

//OUT
always_comb begin
  case (s)
    `S0: if (x)
          u = 1'b1;
        else
          u = 1'b0;
    default: if (x)
             u = 1'b0;
            else
             u = 1'b1;
  end
end

```

Adding more datatypes, including struct

```

typedef logic [3:0] nibble;
nibble nibbleA, nibbleB;



typedef enum {WAIT, LOAD, STORE} state_t;
state_t state, next_state;

typedef struct {
  logic [4:0] alu_ctrl;
  logic stb,ack;
  state_t state } control_t;
control_t control;

assign control.ack = 1'b0;

```

Alternative FSM (separate register)

  

```

// COMB
always_comb begin
  ns = `S0; // defaults
  u = 1'b0;
  case (s)
    `S0: if (x) begin
          ns = `S1;
          u = 1'b1;
        end
    default:
      if (~x) begin
        u = 1'b1;
        ns = `S1;
      end
  end
end

// state register
always_ff @(posedge clk) begin
  if (rst)
    s <= `S0;
  else
    s <= ns;
end

```

This description stops us from adding unintentional extra states and flipflops

System tasks

- Initialize memory from file

```

module test;
  reg [31:0] mem[0:511]; // 512x32 memory
  integer i;

  initial begin
    $readmemh("init.dat", mem);
    for (i=0; i<512; i=i+1)
      $display("mem %0d: %h", i, mem[i]); // with CR
  end
  ...
endmodule

```

TSEA44: Computer hardware – a system on a chip 2019-11-05 25

Expand testbench functions using tasks

- Tasks are subroutines (like procedures in VHDL)
- Initial statement only in testbenches

my_test_bench

```

initial begin
uart1.putstr("s 0");
end
    
```

LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 27

In the testbench

```

wire tx,rx;
...
// send a command
initial begin
    #100000 // wait 100 us
    uart1.putstr("s 0");
end

// instantiate the test UART
uart_tasks uart1(.*);

// instantiate the computer
computer computer1(.*);
    
```

LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 26

Tasks example

```

module uart_tasks(input clk, uart_tx,
output logic uart_rx);

initial begin
uart_rx = 1'b1;
end

task getch();
reg [7:0] char;
begin
@{(negege uart_tx);
#4340;
#8680;
for (int i=0; i<8; i++) begin
char[i] = uart_tx;
#8680;
end
$fwrite(32'h1,"%c", char);
end
endtask // getch

task putch(input byte char);
begin
uart_rx = 1'b0;
for (int i=0; i<8; i++)
#8680 uart_rx = char[i];
#8680 uart_rx = 1'b1;
#8680;
end
endtask // putch

task putstr(input string str);
byte ch;
begin
for (int i=0; i<str.len; i++)
begin
ch = str[i];
if (ch)
putch(ch);
end
putch(8'h0d);
end
endtask // putstr
endmodule // uart_tb
    
```

LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 28

Lab 0: Build an UART in Verilog, Zedboard

- Clk = 100 Mhz
- Baud rate = 115200
- Full duplex (support concurrent send and receive)

LINKÖPING UNIVERSITY

UCF = User Constraint File, Zedboard

```

NET "clk_i" LOC = "Y9" | IOSTANDARD=LVCNMOS33; // 100 MHz on Zedboard
NET "rst_i" LOC = "R16" | IOSTANDARD=LVCNMOS18; // BTND (downward) on green flexo
NET "send_i" LOC = "T18" | IOSTANDARD=LVCNMOS18; // BTNU (up) on green flexo
// switches
NET "switch_i<0>" LOC = "F22" | IOSTANDARD=LVCNMOS18; // SWITCH 0
NET "switch_i<1>" LOC = "G22" | IOSTANDARD=LVCNMOS18; // SWITCH 1
NET "switch_i<2>" LOC = "H22" | IOSTANDARD=LVCNMOS18; // SWITCH 2
NET "switch_i<3>" LOC = "F21" | IOSTANDARD=LVCNMOS18; // SWITCH 3
NET "switch_i<4>" LOC = "H19" | IOSTANDARD=LVCNMOS18; // SWITCH 4
NET "switch_i<5>" LOC = "H18" | IOSTANDARD=LVCNMOS18; // SWITCH 5
NET "switch_i<6>" LOC = "H17" | IOSTANDARD=LVCNMOS18; // SWITCH 6
NET "switch_i<7>" LOC = "M15" | IOSTANDARD=LVCNMOS18; // SWITCH 7
// row of LEDs
NET "led_o<0>" LOC = "T22" | IOSTANDARD=LVCNMOS33; // LED L00
NET "led_o<1>" LOC = "T21" | IOSTANDARD=LVCNMOS33; // LED L01
NET "led_o<2>" LOC = "U22" | IOSTANDARD=LVCNMOS33; // LED L02
NET "led_o<3>" LOC = "U21" | IOSTANDARD=LVCNMOS33; // LED L03
NET "led_o<4>" LOC = "V22" | IOSTANDARD=LVCNMOS33; // LED L04
NET "led_o<5>" LOC = "W22" | IOSTANDARD=LVCNMOS33; // LED L05
NET "led_o<6>" LOC = "U19" | IOSTANDARD=LVCNMOS33; // LED L06
NET "led_o<7>" LOC = "U14" | IOSTANDARD=LVCNMOS33; // LED L07
// USART Pmod on top row of JB
NET "rx_i" LOC = "V10" | IOSTANDARD=LVCNMOS33; // PMOD B, JB1
NET "tx_o" LOC = "W11" | IOSTANDARD=LVCNMOS33; // PMOD B, JB2
    
```

Net names must match names used in the module description

UCF = User Constraint File, VirtexII



```

CONFIG PART = XC2V4000-FF1152-4 ;
NET "clk_i" LOC = "AK19"; // 40 MHz in this lab
NET "rst_i" LOC = "C2"; // SW1 (red) on green flexo
NET "send_i" LOC = "B3"; // SW2 (black) on green flexo
// blue DIP switch
NET "switch_i<7>" LOC = "AL3"; // SWITCH 1
NET "switch_i<6>" LOC = "AK3"; // SWITCH 2
NET "switch_i<5>" LOC = "AJ5"; // SWITCH 3
...
// row of LEDs
NET "led_o<7>" LOC = "N9"; // LED D4
NET "led_o<6>" LOC = "P8"; // LED D5
NET "led_o<5>" LOC = "N8"; // LED D6
...
// rainbow flat cable
NET "rx_i" LOC = "N9";
NET "tx_o" LOC = "K5";
NET "clk" LOC = "AK19";
...
    
```

Net names must match names used in the module description

Lab 0: Build an UART in Verilog, VirtexII

  - Clk = 40 Mhz
- Baud rate = 115200
- Full duplex (support concurrent send and receive)



(Voltage level shifter etc not shown)

Additional requirements!

- Only transmit one character on rising edge of pushbutton
- The reset state on the LED should indicate the value of your student id:s last two digits.
 - Example: Linus123 should have the value 23 on the LED when reset is applied (and kept there until a value is received on rx).
 - $23 = 16+4+2+1 = 00010111$
- Remember lab 0 is individual

TSEA44: Computer hardware – a system on a chip 2019-11-05 33

Lab 0: Testbench

Letter C (0x43)
Time per bit is 8.68 μs

li.u LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 35

Bigger example: Personal number check

- Swedish social security number (personnummer) consists of 10 digits, where the last is a checksum digit.

$$d_1 d_2 d_3 d_4 d_5 d_6 d_7 d_8 d_9 d_{10}$$

$$d_{10} = (10 - ([2d_1]+d_2+[2d_3]+d_4+\dots+[2d_9])) \bmod 10$$
 where $[2d_x]$ is digit sum of $2*d_x$ (example $d_x=6 \Rightarrow 2*6=12 \Rightarrow [2d_x]=3$)
- Iterative solution (X2 a function of index and digit)

$$S_0 = 0$$

$$S_k = S_{k-1} \bmod_{10} X 2(d_k) \quad k=1..9$$

$$d_{10} = 10 - S_9$$

li.u LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 34

Things to look out for

- Testbench have automatically synchronization of rx and tx
 - In real life, an rx bit may start when half of a tx bit have been sent

- Do not forget to wait for 1/2 of the stop bit in rx!
 - May otherwise detect last data bit as new start bit!

li.u LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 36

Overall system

- PNR is calculating the checksum, presenting it on the display

li.u LINKÖPING UNIVERSITY

TSEA44: Computer hardware – a system on a chip 2019-11-05 37

Top module (pnr module)

```

`include "timescale.v"
timescale 1ns / 1ps


module pnr(input clk,rst,stb,
input [3:0] kb,
output [3:0] u);

// our design

endmodule
    
```

time unit precision

* No entity/architecture distinction => just module



 

TSEA44: Computer hardware – a system on a chip 2019-11-05 39

Timing diagram

- When button is pressed:

$$d2 = \text{digitsum}(2 \cdot 9) = \text{digitsum}(18) = 9$$

 

$$\text{New } s = (d2 + s) \bmod 10 = (9 + 5) \bmod 10 = 14 \bmod 10 = 4$$

TSEA44: Computer hardware – a system on a chip 2019-11-05 38

Block schematic (thinking hardware!)

- Split into datapath and control
- Green boxes synch FSM
- White boxes comb
- Button is singlepulsed

TSEA44: Computer hardware – a system on a chip 2019-11-05 40

Synch and single pulse shown before

- Always synchronize external inputs!!

 

```

reg x,y; // variable type (0,1,Z,X)
wire button; // net type (0,1,Z,X)

// SSP
always @(posedge clk) // procedural block
begin
x <= stb;
end

always @(posedge clk) // procedural block
begin
y <= x;
end

assign button = x & ~y;
    
```

TSEA44: Computer hardware – a system on a chip 2019-11-05 41

Decade counter


```

reg [3:0] p;
wire odd,last;

// 10 counter
always_ff @(posedge clk) begin
    if (rst)
        p <= 4'd0;
    else begin
        if (button)
            if (p<9)
                p <= p+1;
            else
                p <= 4'd0;
    end
end

assign odd = ~p[0];
assign last = (p==4'h9) ? 1'b1 : 1'b0;
    
```

Digit index start with 1 =>
Odd is complement of LSB



TSEA44: Computer hardware – a system on a chip 2019-11-05 43

 

ADD Reg2, Mod10 K

```

// ADD
assign d3 = {1'b0,s} + {1'b0,d2}; // unsigned

// REG2 and MOD10
always_ff @(posedge clk) begin
    if (rst)
        s <= 4'h0;
    else if (button)
        if (d3 < 10)
            s <= d3[3:0];
        else
            s <= d3[3:0] + 4'd6; // unsigned, 4 bitar
    end
end

// K
assign u = (last == 1'b0) ? d :
           (s == 4'd0) ? 4'd0 :
           4'd10 - s;
    
```

 




TSEA44: Computer hardware – a system on a chip 2019-11-05 42

X2 (multiply and add digits when odd=0)

```

always_comb begin
    if (~odd)
        case (d)
            4'h1: d2 = 4'h2;
            4'h2: d2 = 4'h4;
            4'h3: d2 = 4'h6;
            4'h4: d2 = 4'h8;
            4'h5: d2 = 4'h1;
            4'h6: d2 = 4'h3;
            4'h7: d2 = 4'h5;
            4'h8: d2 = 4'h7;
            4'h9: d2 = 4'h9;
            default: d2 = 4'h0;
        endcase
    else
        d2 = d;
    end
end
    
```

TSEA44: Computer hardware – a system on a chip 2019-11-05 44

Testbench for PNR (1 of 2)


```

#include "timescale.v"

module testbench();
// Inputs
reg clk;
reg rst;
reg [3:0] kb;
reg stb;


// Outputs
wire [3:0] u;

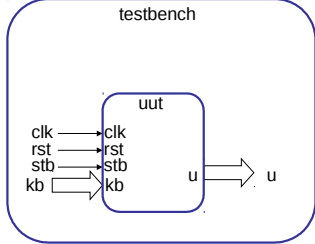// Instantiate the UUT
pnr uut (
    .clk(clk),
    .rst(rst),
    .kb(kb),
    .stb(stb),
    .u(u));
endmodule
    
```



```

// SystemVerilog instantiation
// automatic mapping port-wire
pnr uut(.*)
    
```



Testbench for PNR (2 of 2)

```
// Initialize Inputs
initial begin
  clk = 1'b0;
  rst = 1'b1;
  kb = 4'd0;
  stb = 1'b0;
  #70 rst = 1'b0;
  //
  #30 kb = 4'd8;
  #40 stb = 1'b1;
  #30 stb = 1'b0;
  //
  #30 kb = 4'd0;
  #40 stb = 1'b1;
  #30 stb = 1'b0;
end

always #12.5 clk = ~clk; // 40 MHz
endmodule
```

← Add more digits and strobe pulses to test a complete number