


Digital ICs — Lectures

1) Introduction [Ch. 1]	TSEI03/TSTE86
2) Devices [Ch. 3, 4]	TSEI03/TSTE86
3) Interconnect [Ch. 4, 9]	TSTE86
4) Circuits [Ch. 5]	TSEI03/TSTE86
5) Combinational logic [Ch. 6]	TSEI03/TSTE86
6) Sequential circuits [Ch. 7]	TSEI03/TSTE86
7) Synchronization [Ch. 10]	TSTE86
8) Adders [Ch. 11]	TSEI03/TSTE86
9) Multipliers [Ch. 11]	TSTE86
10) Memory [Ch. 12]	TSEI03/TSTE86
11) Manufacturing [Ch. 2]	TSTE86
12) System design [Ch. 8]	TSTE86

Switch Nets




X if $A \cdot B$
otherwise Z

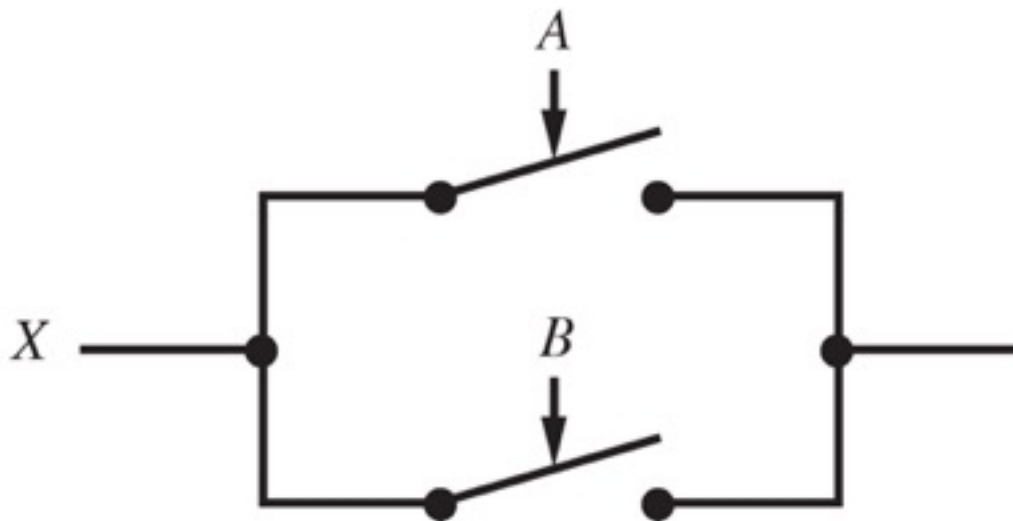


X if $A + B$
otherwise Z

Subnets

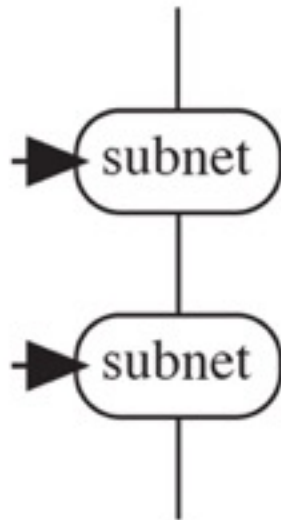

AND net


conducts when all subnets conduct

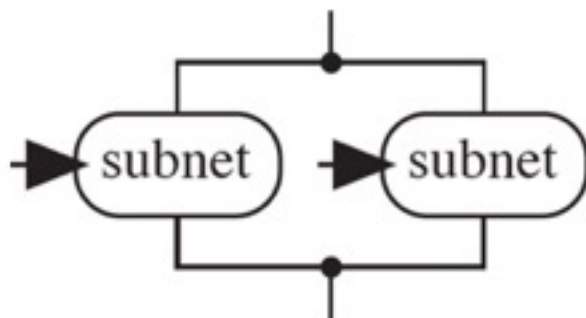

OR net

conducts when any subnet conducts

Static CMOS Switch Nets

 

Conducts when $f(\bar{X}) = 1$


$$S_p = f(\bar{x}_1, \bar{x}_2, \dots, \bar{x}_m)$$

Conducts when $f(X) = 0$


$$S_n = \overline{f(x_1, x_2, \dots, x_m)}$$

Input Pattern Effects on Delay

Propagation delay of a NAND gate

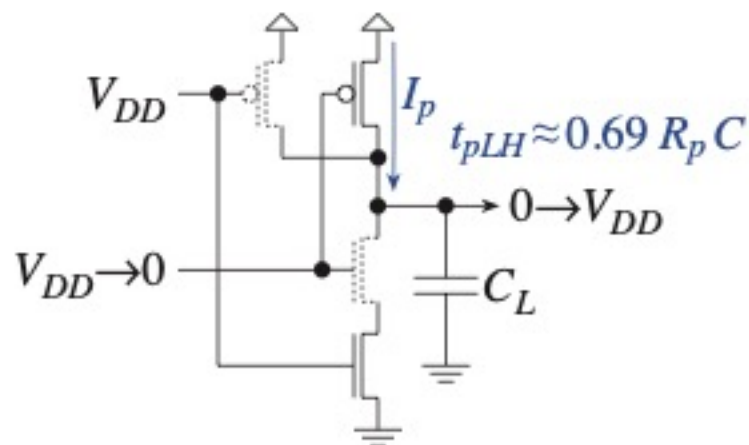


One input switches

 


Two inputs switch

Designing Pass Transistor Logic

 


Start with binary tree


 


Simplify branches


Complementary Pass Transistor Logic

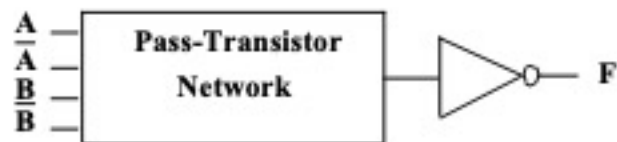


(a)

 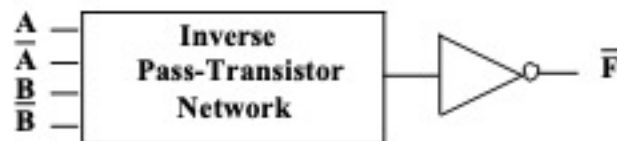

AND/NAND

 


OR/NOR

 


EXOR/NEXOR

(b)

Carry Function in CPL


 


Binary carry tree

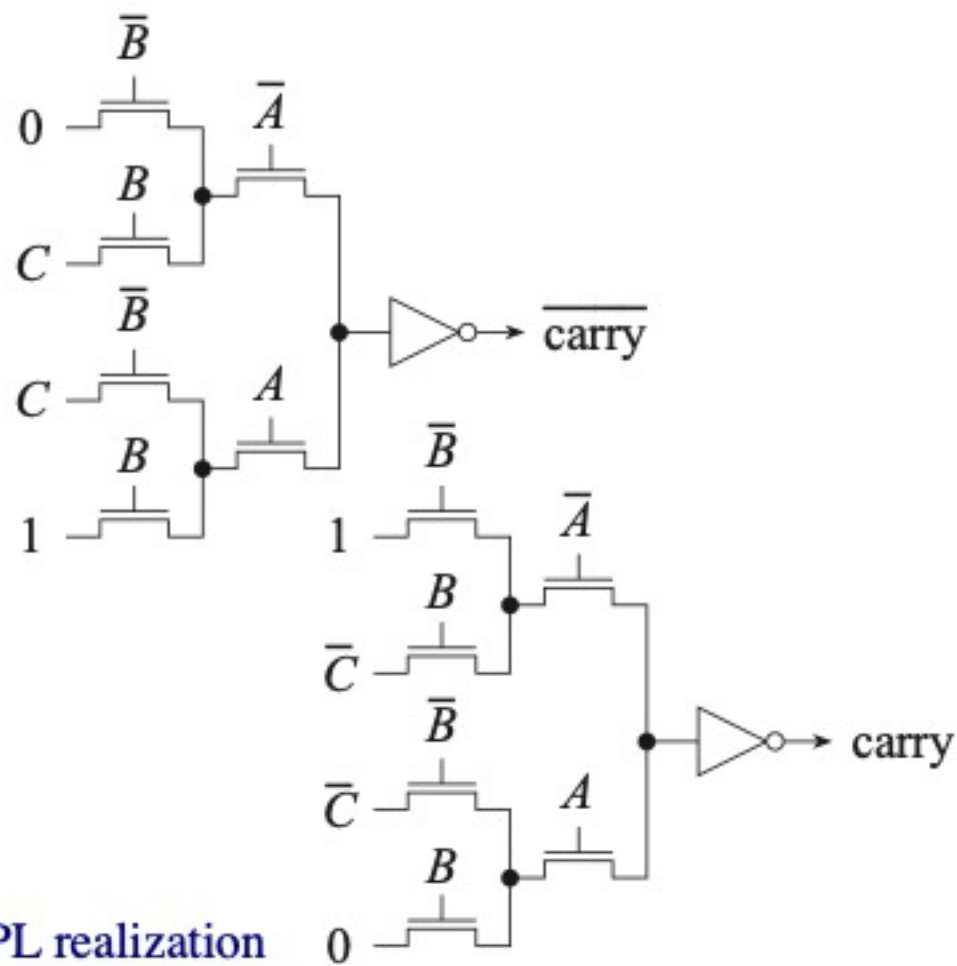

CPL realization

Level Restoring Transistor

 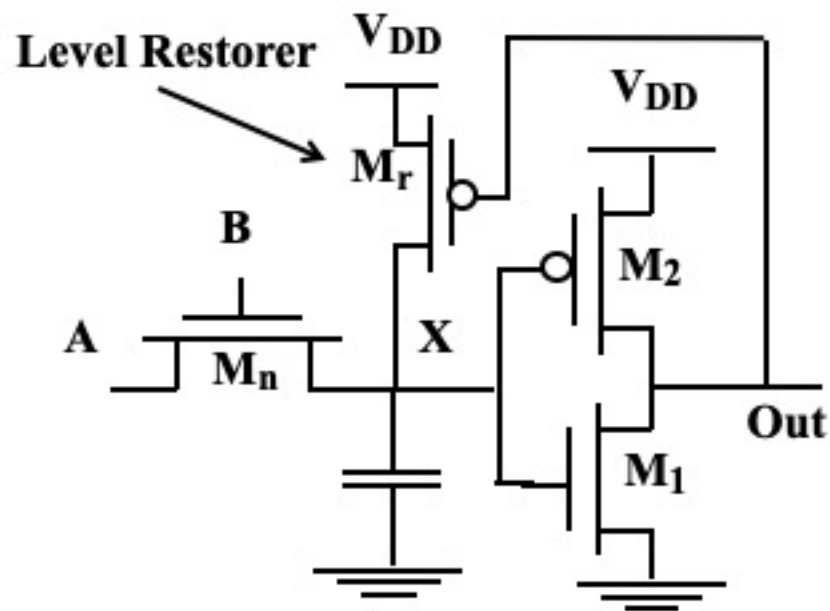

Improved Switch: Transmission Gate

