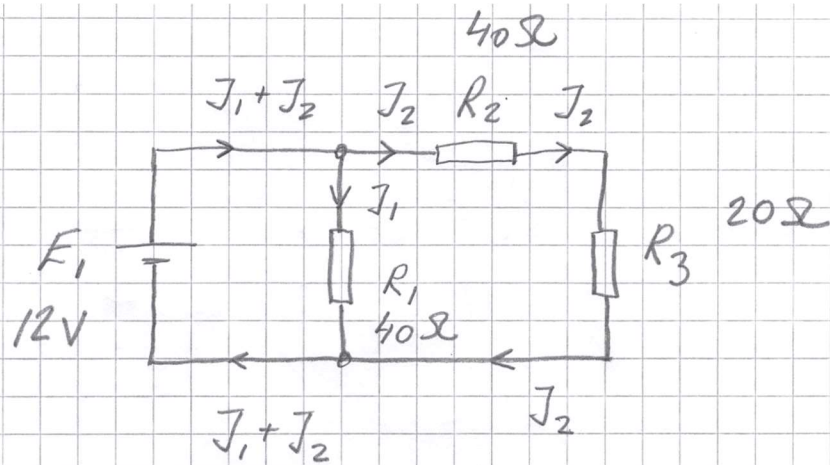


01.



OHMS LAG \Rightarrow

$$J_1 = \frac{E_1}{R_1} \Rightarrow J_1 = 0,30 A$$

$$J_2 = \frac{E_1}{R_2 + R_3} \Rightarrow J_2 = 0,20 A$$