

a/

$$I = \frac{U}{Z_1 + Z_2}$$

$$I = \frac{220\sqrt{2} \cdot e^{j0^\circ}}{20 - j10} =$$

$$= \frac{220\sqrt{2} (20 + j10)}{400 + 100} \approx$$

$$= 8,8\sqrt{2} + j4,4\sqrt{2} \quad A$$

$$I \approx 9,8\sqrt{2} e^{j27^\circ}$$

$$b/ \quad \arg U_1 = \arg Z_1 I = \arg Z_1 + \arg I$$

$$\arg U_2 = \arg Z_2 I = \arg Z_2 + \arg I$$

$$\rightarrow \arg U_1 - \arg U_2 = \arg Z_1 - \arg Z_2 =$$

$$= \arg \frac{Z_1}{Z_2}$$

$$\frac{Z_1}{Z_2} = \frac{8,0 + j6,0}{12 - j16} = \frac{(8,0 + j6,0)(12 + j16)}{(12 - j16)(12 + j16)} =$$
$$= \frac{96 + j128 + j72 - 96}{400} = j0,50$$

$$\arg(j0,50) = 90^\circ$$

$$\text{Alltså } \arg \frac{Z_1}{Z_2} = \arg U_1 - \arg U_2 = \underline{90^\circ}$$