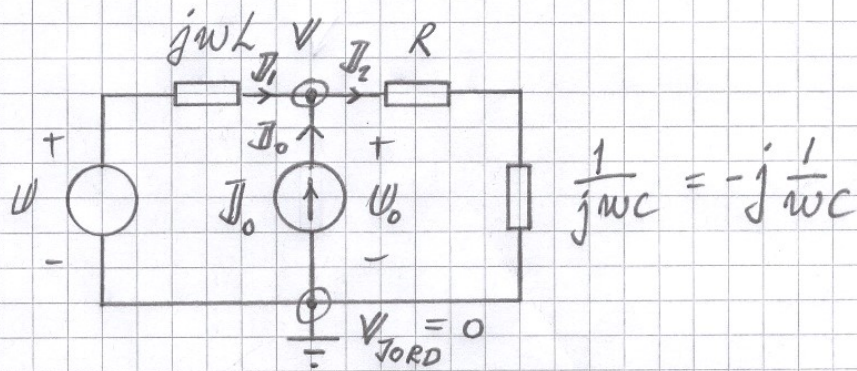


$$P_o = U_o I_o \cos \varphi_o \dots (1)$$

$$\text{DÄR } \varphi_o = \arg U_o - \arg I_o$$



$$u(t) = 100\sqrt{2} \sin(10000t + 0^\circ) \text{ V}$$

$$i_o(t) = 2,0\sqrt{2} \sin(10000t + 0^\circ) \text{ A}$$

$$U = 100\sqrt{2} e^{j0^\circ} \text{ V} \quad I_o = 2,0\sqrt{2} e^{j0^\circ} \text{ A}$$

NODANALYS:

$$I_1 + I_o - I_2 = 0 \Rightarrow$$

$$\frac{U - V}{j\omega L} + I_o - \frac{V - V_{\text{JORD}}}{R - j\frac{1}{\omega C}} = 0$$

$$\frac{100\sqrt{2} - V}{j200} + 2,0\sqrt{2} - \frac{V - 0}{100 - j100} = 0$$

$$-j0,5\sqrt{2} - \frac{V}{j200} + 2,0\sqrt{2} - \frac{V}{100-j100} = 0$$

$$\frac{-(100-j100)V - j200V}{j200(100-j100)} = j0,5\sqrt{2} - 2,0\sqrt{2}$$

$$\frac{(-100-j100)V}{j20000 + 20000} = -2\sqrt{2} + j0,5\sqrt{2}$$

$$\frac{100\sqrt{2} e^{-j135^\circ} V}{20000\sqrt{2} e^{j45^\circ}} = 2,92 e^{j166^\circ}$$

$$V = 584 e^{j346^\circ} V$$

$$U_o = V$$

$$U_o = \frac{\hat{U}_o}{\sqrt{2}} \Rightarrow U_o = 413 V$$

$$I_o = \frac{\hat{I}_o}{\sqrt{2}} \Rightarrow I_o = 2,0 A$$

$$\varphi_o = 346^\circ - 0^\circ = 346^\circ$$

$$\text{INS, (1)} \Rightarrow P_o = 413 \cdot 2,0 \cos(346^\circ) =$$

$$= \underline{\underline{0,80 \text{ kW}}}$$