

52 a)

$$\hat{U}_2 = U_c + 2 \cdot 0,70$$

\uparrow \uparrow
 SPÄNNINGEN 8,0 V $\Rightarrow \hat{U}_2 = 9,4 \text{ V}$
 ÖVER N_2


$$\frac{N_1}{N_2} = \frac{\hat{U}}{\hat{U}_2} \rightarrow \frac{N_1}{N_2} = \frac{230\sqrt{2}}{9,4} \approx \underline{\underline{35}}$$

b)

$$U_{UT} = U_Z - U_{BE} \Rightarrow \underline{\underline{U_{UT} = 4,9 \text{ V}}}$$

\uparrow \uparrow
 5,6 V 0,70 V

c)

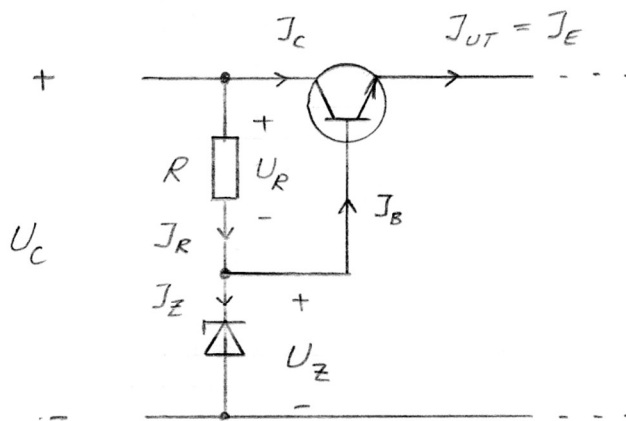

$$J_R = J_Z + J_B$$

$$J_R = \frac{U_R}{R} = \frac{U_c - U_Z}{R} \rightarrow J_R = 20 \text{ mA}$$

$$0,020 = 0,010 + J_B \rightarrow J_B = 10 \text{ mA}$$

$$J_{UT} = J_E = J_B + J_C = J_B + h_{FE} \cdot J_B = J_B (1 + h_{FE})$$

$$\Rightarrow \underline{\underline{J_{UT \text{ MAX}} = 0,010(1 + 99) = 1,0 \text{ A}}}$$