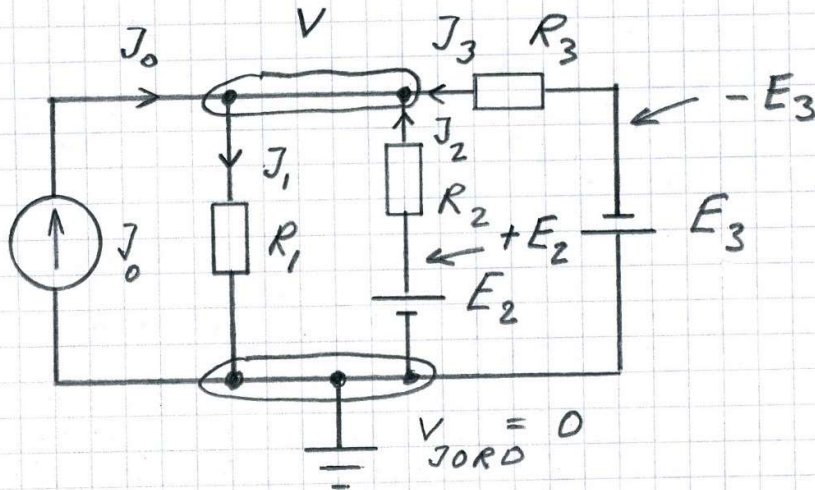


1.

NODANALYS :



$$J_1 = \frac{V - 0}{R_1} \dots (1)$$

$$J_0 - J_1 + J_2 + J_3 = 0 \rightarrow$$

$$J_0 - \frac{V - 0}{R_1} + \frac{E_2 - V}{R_2} + \frac{-E_3 - V}{R_3} = 0$$

$$\Rightarrow V = + 2,25 \text{ V}$$

$$\text{ins i (1)} \rightarrow \underline{\underline{J_1 = 1,5 \text{ A}}}$$

2a)

OM KONDENSATORN ÄR
BORTKOPPLAD

$$I = \frac{U}{R + j\omega L}$$

$$I = \frac{230\sqrt{2} \cdot e^{j0^\circ}}{24 + j100\pi \cdot 0,10} \approx 5,8\sqrt{2} e^{-j53^\circ} \text{ A}$$

$$\underline{i(t) = 5,8\sqrt{2} \sin(100\pi t - 53^\circ) \text{ A}}$$

$$P = R \cdot I^2 \rightarrow P = 24 \cdot 5,8^2 \approx \underline{0,81 \text{ kW}}$$

$$Q = Q_L = \omega L \cdot I^2 \rightarrow Q = 100\pi \cdot 0,10 \cdot 5,8^2 \approx \underline{1,1 \text{ kVAR}}$$

2b) OM KONDENSATORN ÄR
INKOPPLAD

$$Q = Q_L - Q_C \text{ DÄR}$$

$$Q_C = \frac{U^2}{X_C} = \frac{1}{X_C} = \frac{1}{\omega C} = \omega C U^2$$


$$Q_C = 314 \cdot 150 \cdot 10^{-6} \cdot 230^2 = 2,5 \text{ KVAR}$$

$$Q = 1,1 - 2,5 = \underline{-1,4 \text{ KVAR}}$$

STRÖMMEN GENOM R OCH L
PÅVERKAS INTE DÅ C KOPPLAS IN
DVS. P ÄR DENSAMMA SOM FÖRUT.

$$\underline{P = 0,81 \text{ KW}}$$

SKENBARA EFFEKTEN

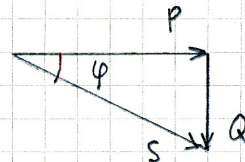

$$S = \sqrt{P^2 + Q^2} \Rightarrow S \approx 1,6 \text{ KVA}$$

$$S = U \cdot I \Rightarrow 1,6 \cdot 10^3 = 230 \cdot I \rightarrow I = 7,0 \text{ A}$$

$$\tan \varphi = \frac{Q}{P} \rightarrow \varphi \approx -60^\circ$$

$$\varphi = \arg U - \arg I \quad -60^\circ = 0^\circ - \arg I$$

$$\rightarrow \arg I = 60^\circ$$

$$\text{ALLTSÅ } \underline{i(t) \approx 7,0 \sqrt{2} \sin(100\pi t + 60^\circ) \text{ A}}$$

3a)
$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2} = \frac{\hat{U}_1}{U_C + 2 \cdot 0,70}$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{230\sqrt{2}}{15 + 1,4} \approx \underline{\underline{20}}$$

3b)
$$U_C - R \cdot J_R - U_Z = 0 \dots (1)$$

$$P_{ZMAX} = U_Z \cdot J_{ZMAX} \dots (2)$$


$$(2) \Rightarrow 2,0 = 12 \cdot J_{ZMAX} \Rightarrow J_{ZMAX} \approx 0,17A$$

"NÄR LAST SAKNAS BLIR
 J_Z MAXIMAL OCH LIKA
 MED J_R .

$$(1) \Rightarrow 15 - R \cdot 0,17 - 12 = 0$$



$$\Rightarrow \underline{\underline{R = 18 \Omega}} \quad (R_{MIN})$$

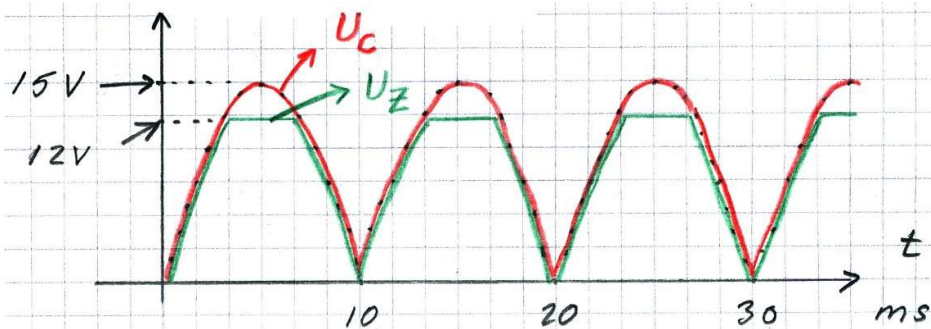3c) TIDSDIAGRAM FÖR U_C OCH U_Z
 DÅ GLÄTTNINGSKONDENSATORN
 GÅTT SÖNDER.



$$\omega = 100\pi \text{ RAD/S} \quad \omega = \frac{2\pi}{T} \Rightarrow T = 20\text{ms}$$

4a)

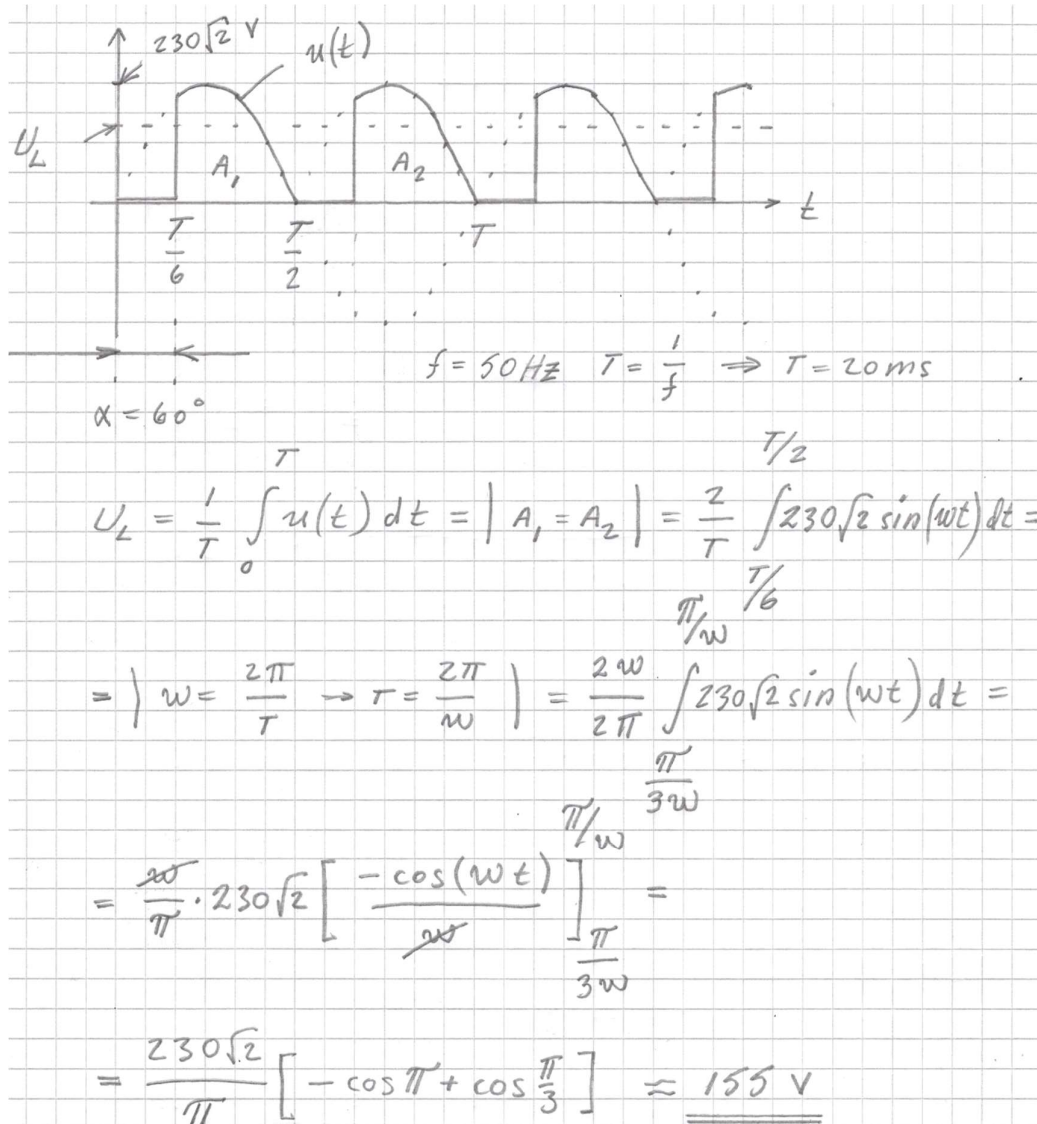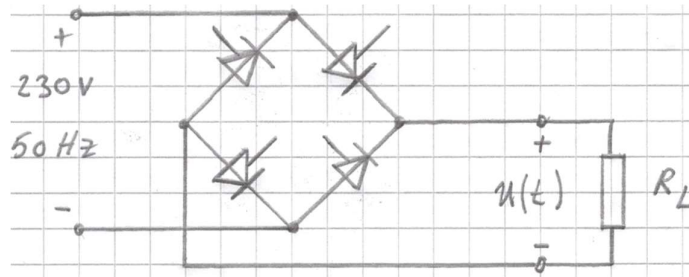

4b)


$$\alpha = \text{MAX} (180^\circ) \Rightarrow U_L = 0$$

$$\alpha = \text{MIN} (0^\circ) \Rightarrow$$

$$\begin{aligned} U_L &= \frac{1}{T} \int_0^T u(t) dt = |A_1 = A_2| - \frac{1}{T} \int_0^{T/2} 230\sqrt{2} \sin(\omega t) dt = \\ &= \left| \omega = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{\omega} \right| = \frac{2\omega}{2\pi} \int_0^{\frac{\pi}{\omega}} 230\sqrt{2} \sin(\omega t) dt = \\ &= \frac{230\sqrt{2}\omega}{\pi} \left[\frac{-\cos(\omega t)}{\omega} \right]_0^{\frac{\pi}{\omega}} = \\ &= \frac{230\sqrt{2}}{\pi} \left[-\cos\pi + \cos 0 \right] = 207 \text{ V} \end{aligned}$$

$$\text{ALTSÄ} \quad \underline{\underline{0 \text{ V} < U_L < 207 \text{ V}}}$$

5. Separatmagnetiserad likströmsmotor

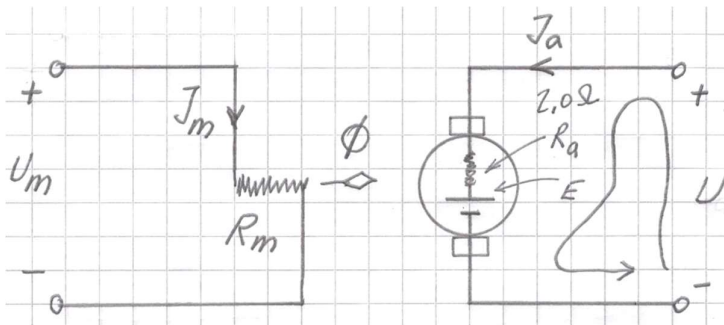

FALL I

$$U_I = 200 \text{ V}$$

$$I_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$I_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

- a) SAMMA MOMENT OCH MAGNETISKT
"FLÖDE" I DE TVÅ FÄLLEN.

$$\left. \begin{aligned} M &= k_2 \Phi I_{aI} \\ M &= k_2 \Phi I_{aII} \end{aligned} \right\} \Rightarrow I_{aII} = I_{aI} = \underline{10 \text{ A}}$$

- b) KIRCHHOFFS SPÄNNINGSLAG $\Rightarrow$

$$+U_I - R_a I_{aI} - E_I = 0 \Rightarrow \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a I_{aII} - E_{II} = 0 \Rightarrow \underline{E_{II} = 150 \text{ V}}$$

c)

$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \Rightarrow \underline{n_{II} = 833 \text{ RPM}}$$