



# Lecture 2, Amplifiers 1

Analog building blocks

# Outline of today's lecture

## Further work on the analog building blocks

Common-source, common-drain, common-gate

Active vs passive load

## Other "simple" analog building blocks

Current mirrors

## Mismatch

And other things related to that

# What did we do until now?

## Stress on the complexity of analog design.

It is not easy and it will take many years before you master.

## Why analog design?


Our world is analog and telecommunication needs analog to interface

Complexity is growing as (n)ever.

## Common-source stage and small signal schematics

Operating point vs small-signal schematics and how they "move" around

# Transistor, revisited

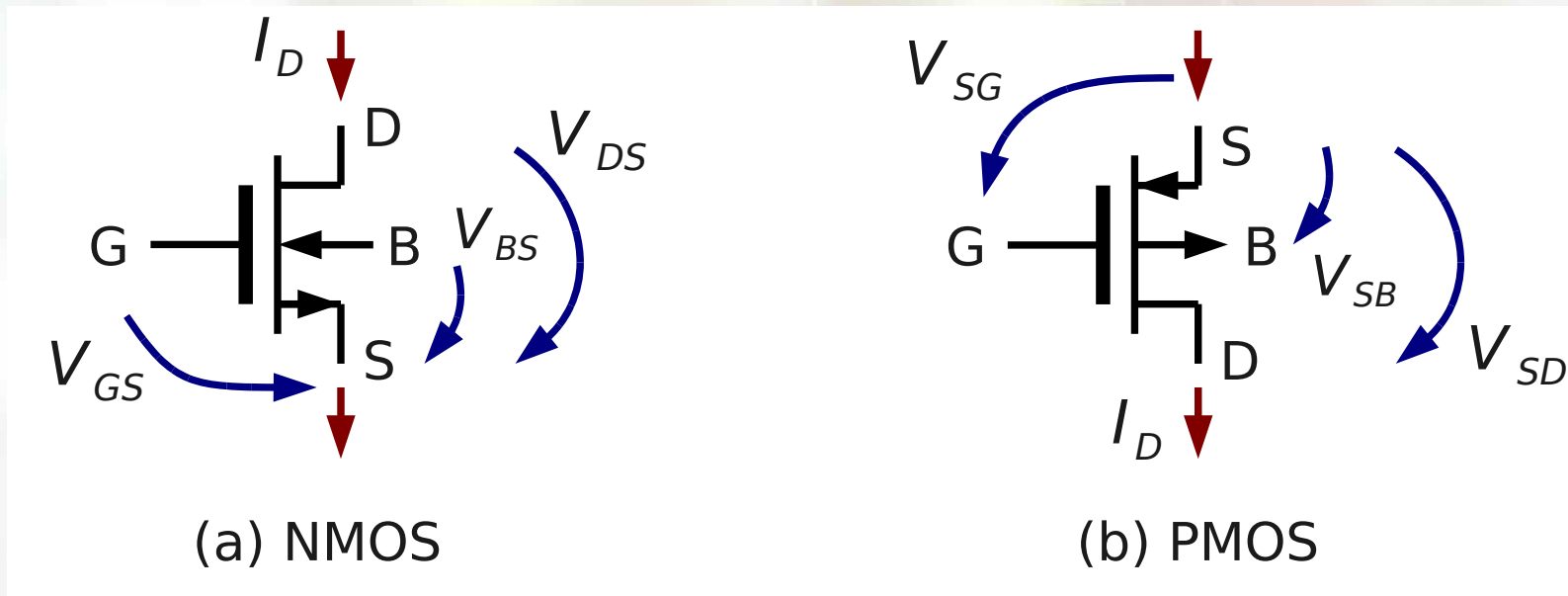

$$I \approx \alpha V_{eff}^2 \cdot \left( 1 + \frac{V_{ds}}{V_{\theta}} \right)$$

# Transistors, small-signal expressions

Linearization gives a small-signal model with these properties:

**Expression**

**Cut-off**

**Linear**

**Saturation**

$$g_m$$

$$\frac{\kappa I_D}{kT/q}$$

$$2\alpha v_{ds}$$

$$\frac{2I_D}{v_{eff}} \quad 2\sqrt{\alpha I_D}$$

$$g_{mbs}$$

$$g_m \cdot \frac{1-\kappa}{\kappa}$$

$$g_m \cdot \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}}$$

$$g_m \cdot \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}}$$

$$g_{ds}$$

$$\lambda I_D$$

$$2\alpha (v_{eff} - v_{ds})$$

$$\lambda I_D$$

# Transistor gain vs region

Using the small-signal parameters gives us the following:

**Expression**

**Cut-off**

**Linear**

**Saturation**

$$A = \frac{g_m}{g_{ds}}$$

$$\frac{\kappa \cdot q}{\lambda \cdot k T}$$

$$\frac{v_{ds}}{v_{eff} - v_{ds}}$$

$$\frac{2}{\lambda \cdot v_{eff}} \quad \frac{2\sqrt{\alpha}}{\lambda\sqrt{I_D}}$$

What can you spot (where is the gain highest)?

$$\kappa \approx 0.75 \text{ and } kT/q \approx 26 \text{ mV.}$$

# Poles, bandwidth, gain, etc.

Bode plot


Approximations

Pole vs gain vs unity-gain

Hand-calculations,  
practical tips


Settling vs pole

Speed

 


# Amplifier stages, passive load
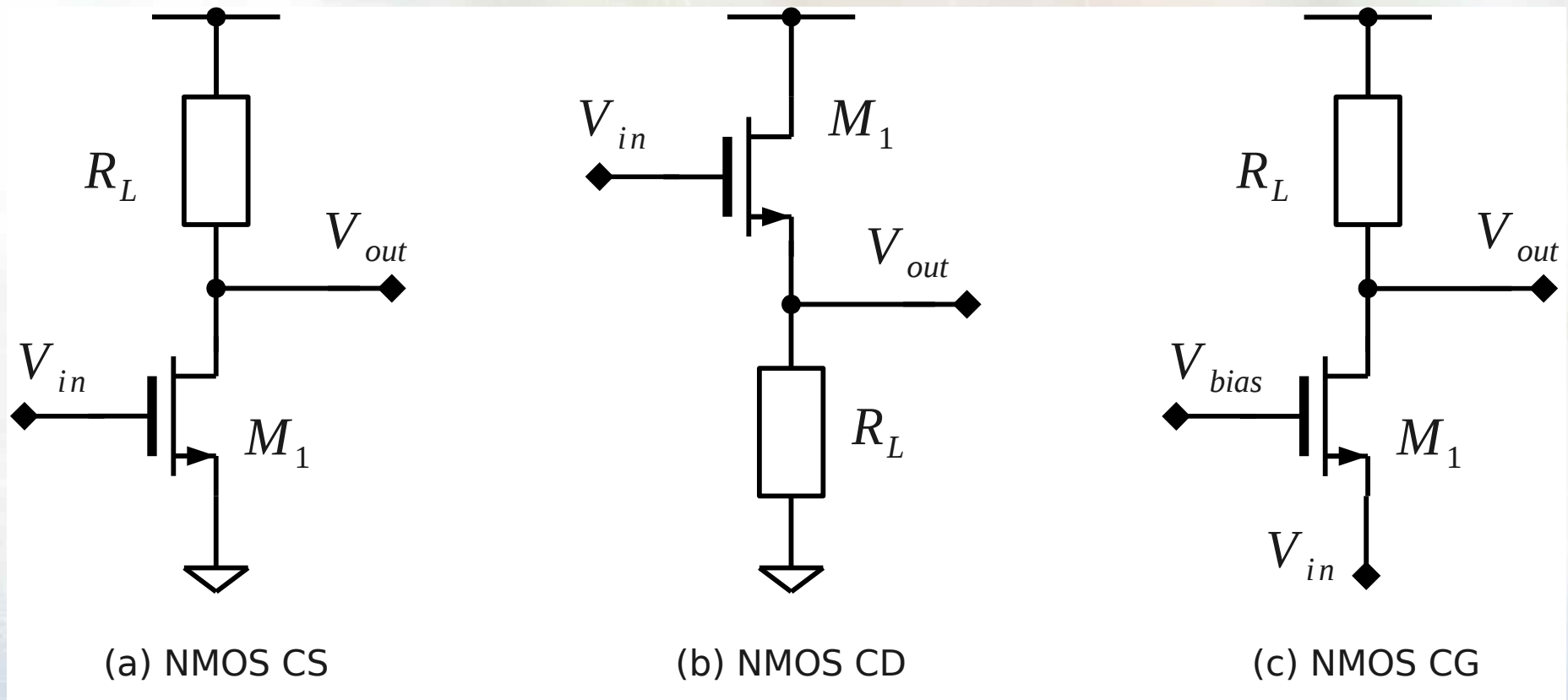
## Common-source, common-drain, common-gate





# Amplifier stages, active load

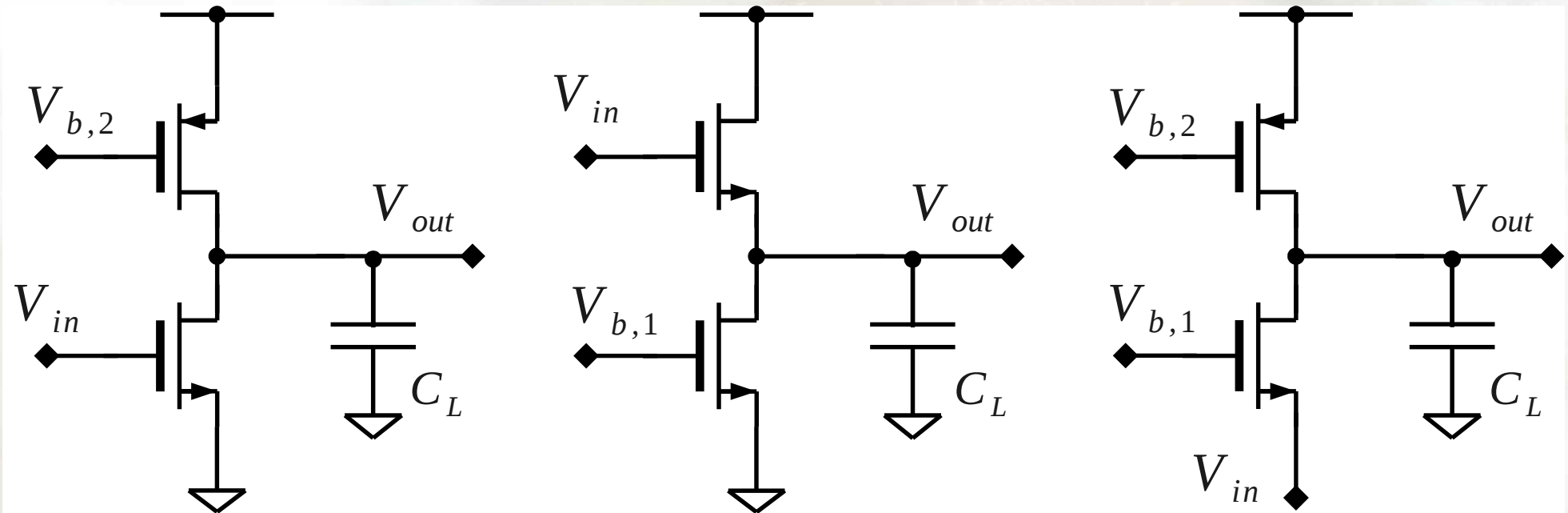

Why active load?

# Amplifier stages, compiled 1

Expression	CS	CD	CG*)
DC gain, $A_0 \approx \frac{g_m}{g_{out}}$	$\approx \frac{g_m}{g_P + g_N}$	$\approx \frac{g_m}{g_m + g_P + g_N} \approx 1$	$\approx \frac{g_m}{g_P + g_N}$
Output impedance, $\approx g_{out}$	$\approx g_P + g_N$	$\approx g_m$	$\approx g_P + g_N$
Bandwidth, $p_1 \approx \frac{g_{out}}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$	$\approx \frac{g_m}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$
Unity gain, $\approx A_0 \cdot p_1$	$\approx g_m / C_L$	N/A (why?)	$\approx g_m / C_L$

Source impedance not mentioned, see exercises.

# Amplifier stages, compiled 2

Expression	CS	CD	CG*)
DC gain, $A_0 \approx g_m / g_{out}$	$\approx 1 / \lambda \cdot v_{eff}$	$\approx 1$	$\approx 1 / \lambda \cdot v_{eff}$
Output impedance, $\approx g_{out}$	$\approx \lambda I_D$	$\approx 2 I_D / v_{eff}$	$\approx \lambda I_D$
Bandwidth, $p_1 \approx g_{out} / C_L$	$\approx \lambda I_D / C_L$	$\approx 2 I_D / C_L \cdot v_{eff}$	$\approx \lambda I_D / C_L \cdot v_{eff}$
Unity gain, $\approx A_0 \cdot p_1$	$\approx I_D / C_L \cdot v_{eff}$	N/A (why?)	$\approx I_D / C_L \cdot v_{eff}$

# Voltage swings

## Walk around the circuit

Check for all the required voltage levels to maintain transistors in their saturation region

## Use the following relations

$$V_{GS} = V_{EFF} + V_T, \quad V_{DS} > V_{EFF} \Rightarrow V_{DS} = V_{EFF}, \quad V_{EFF} = \sqrt{\frac{I_D}{\alpha}}$$


**The lower  $v_{eff}$ , the ...**

higher swing

higher gain
 
# Examples

Consider the three amplifiers and check the potentials



# Some other relationships

**Expression**

**Generic**

**CG/CS**

**CD**

**Slew rate**

$$SR \approx \frac{I_D}{C_L}$$

$$\approx \omega_u \cdot v_{eff}$$

$$\approx \frac{p_1 \cdot v_{eff}}{2}$$

**Noise, input-referred**

$$v_n^2(f) \approx \frac{4kT\gamma}{g_m}$$

$$\approx \frac{2kT\gamma \cdot v_{eff}}{I_D}$$

**Noise, total output**

$$v_{out}^2 \approx \frac{kT\gamma A_0}{C_L}$$

$$\approx \frac{kT\gamma}{\lambda C_L v_{eff}}$$

$$\approx \frac{kT\gamma}{C_L}$$

# Mismatch, or

"In reality, nothing is perfect ..."

## Differences in

Fabs (wafer-to-wafer, fabrication, date)

Wafer locations (chip-to-chip, doping)

Transistor (block-by-block, orientation and side effects, doping)

Temperatures, Voltages, Currents

**You cannot assume that one transistor is identical to another**

Especially not for high-speed, high-accuracy applications

# Mismatch, cont'd

The drain current in the saturation region:

$$\begin{aligned}
 \Delta I_D &= \underbrace{\frac{dI_D}{d\beta} \cdot \Delta\beta + \frac{dI_D}{dS} \cdot \Delta S}_{\Delta\alpha} + \frac{dI_D}{dV_{eff}} \cdot \Delta V_{eff} + \frac{dI_D}{dV_{ds}} \cdot \Delta V_{ds} = \\
 &= \underbrace{\frac{I_D}{\beta} \cdot \Delta\beta + \frac{I_D}{S} \cdot \Delta S}_{\Delta\alpha} + \frac{2I_D}{V_{eff}} \cdot \Delta V_{eff} + \frac{\lambda I_D}{1 + \lambda(V_{ds} - V_{eff})} \cdot \Delta V_{ds} \Rightarrow \\
 \frac{\Delta I_D}{I_D} &= \underbrace{\frac{\Delta\beta}{\beta} + \frac{\Delta S}{S}}_{\Delta\alpha} + \frac{2\Delta V_{eff}}{V_{eff}} + \frac{\lambda \Delta V_{ds}}{1 + \lambda(V_{ds} - V_{eff})} \Rightarrow \\
 \frac{\Delta I_D}{I_D} &\approx \frac{\Delta\alpha}{\alpha} + \frac{2\Delta V_{eff}}{V_{eff}}
 \end{aligned}$$



# Mismatch, cont'd

Ignoring the low-impact ones, and assuming that they are decoupled, gives us, with the help of stochastic variables:

$$\sigma^2 \left( \frac{\Delta I_D}{I_D} \right) = \sigma^2 \left( \frac{\Delta \alpha}{\alpha} \right) + \frac{\sigma^2(\Delta V_{eff})}{V_{eff}^2}$$

## First-order assumptions

$$\sigma^2 \left( \frac{\Delta \alpha}{\alpha} \right) \approx \frac{A_S^2}{W \cdot L} \quad \text{and} \quad \sigma^2(\Delta V_{eff}) \approx \frac{A_{VT}^2}{W \cdot L}$$

## Second-order assumptions

Distance-related, correlations, etc.

# Current mirrors


## Distribute currents

## Set bias levels


"Equal" current through many branches
 
## Decouple design parameters

Gain is now controlled by current instead



# Current mirrors, cont'd

 


# Current mirrors, some maths

Swing

Input impedance

Output impedance

 

# What did we do today?

Went through the other important CMOS building blocks

CG, CD, CS, (CI)

## Current mirrors

How to bias a circuit (current mirrors)

Pros and cons with different current mirrors

## Mismatch

# What will we do next time?

## Amplifiers and differential pairs

Why differential?

## Stability

Why stability?

Phase margin

Compensation