

Chapter 4 - Problems

$$4.1) \text{ dBm}_{(50\Omega)} = 10 \log \frac{V_{\text{rms}}^2}{50 \text{ m}}$$

$$\text{dBm}_{(75\Omega)} = 10 \log \frac{V_{\text{rms}}^2}{75 \text{ m}}$$

$$\therefore \text{dBm}_{(50\Omega)} - \text{dBm}_{(75\Omega)} = 10 \log \frac{75}{50} \approx \underline{1.76}$$

$$\therefore \underline{\text{dBm}_{(50\Omega)} = \text{dBm}_{(75\Omega)} + 1.76}$$

$$4.2) 10 \log \frac{P_1}{1 \text{ mW}} = -20 \Rightarrow P_1 = 10 \mu\text{W}$$

$$10 \log \frac{P_2}{1 \text{ mW}} = -23 \Rightarrow P_2 = 5 \mu\text{W}$$

$$a) P_{\text{total}} = P_1 + P_2 = 15 \mu\text{W} \Rightarrow \underline{P_{\text{total}} = -18.24 \text{ dBm}}$$

$$b) P_{\text{total}} = P_1 + P_2 + 2\sqrt{P_1 P_2} = 19.24 \mu\text{W} \\ \Rightarrow \underline{P_{\text{total}} = -17.16 \text{ dBm}}$$

$$c) \underline{P_{\text{total}} = -15.35 \text{ dBm}}$$

$$d) \underline{P_{\text{total}} = -30.67 \text{ dBm}}$$

$$4.3) \text{ Expected dBm for } 10 \text{ Hz bandwidth} = -40 - 10 \log \frac{30}{10} \\ = \underline{-44.77 \text{ dBm}}$$

$$-40 = 10 \log \frac{P}{1 \text{ mW}} \Rightarrow \underline{P = 0.1 \mu\text{W}}$$

(cont.)

$$4.3) \text{ (cont.) } \text{Spectral density} = \frac{0.1 \mu\text{W}}{30 \text{ Hz}} = \frac{3.3}{1000} \frac{(\text{mV})^2}{\text{Hz}}$$

$$\Rightarrow \text{root spectral density} = \underline{0.058 \frac{\text{mV}}{\sqrt{\text{Hz}}}}$$

$$4.4) 10 \log \frac{P}{1 \text{ mW}} = -60 \Rightarrow P = 1 \text{ nW}$$

$$V_n^2(f) \Big|_{f=0.1 \text{ Hz}} = \frac{1 \text{ nW}}{1 \text{ mHz}} = 1 \frac{(\text{mV})^2}{\text{Hz}}$$

$$\text{Assuming } V_n^2(f) = \frac{K_v^2}{f} \text{ and } V_n^2(f) \Big|_{f=0.1 \text{ Hz}} = 1 \frac{(\text{mV})^2}{\text{Hz}},$$

$$V_n^2(f) = \frac{0.1 (\text{mV})^2}{f}$$

Total noise power in (1mHz, 1Hz) is :

$$\int_{1 \text{ m}}^1 V_n^2(f) df = 0.1 (\text{mV})^2 [\ln 1 - \ln 1 \text{ m}] = 0.69 \mu\text{W}$$

$$10 \log \frac{0.69 \mu}{1 \text{ m}} = \underline{-31.6 \text{ dBm}}$$


$$4.5) V_{n1}^2(f) = 4KTR_1 \ \& \ V_{n2}^2(f) = 4KTR_2$$

The two noise sources are uncorrelated.

$$\therefore V_n^2(f) = V_{n1}^2(f) + V_{n2}^2(f) = 4KTR_1 + 4KTR_2$$

$$= 4KT (R_1 + R_2)$$

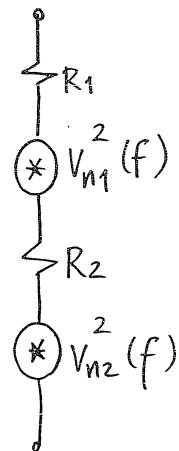which is equal to the noise spectral density of the series combination of R_1 & R_2 .




$$4.6) V_{no}^2(f) = \frac{4KTR}{1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2} \quad \text{where } \omega_{3dB} = \frac{1}{RC}$$

For $C = 100 \text{ pF}$ & $R = 1 \text{ k}\Omega$, $\omega_{3dB} = 10^7 \text{ rad/sec}$.

$$\text{and } V_{no}^2(0) = (4.08 \text{ nV})^2 = 1.66 \times 10^{-17} \text{ V}^2$$

For $C = 100 \text{ pF}$ & $R = 1 \text{ M}\Omega$, $\omega_{3dB} = 10^4 \text{ rad/sec}$
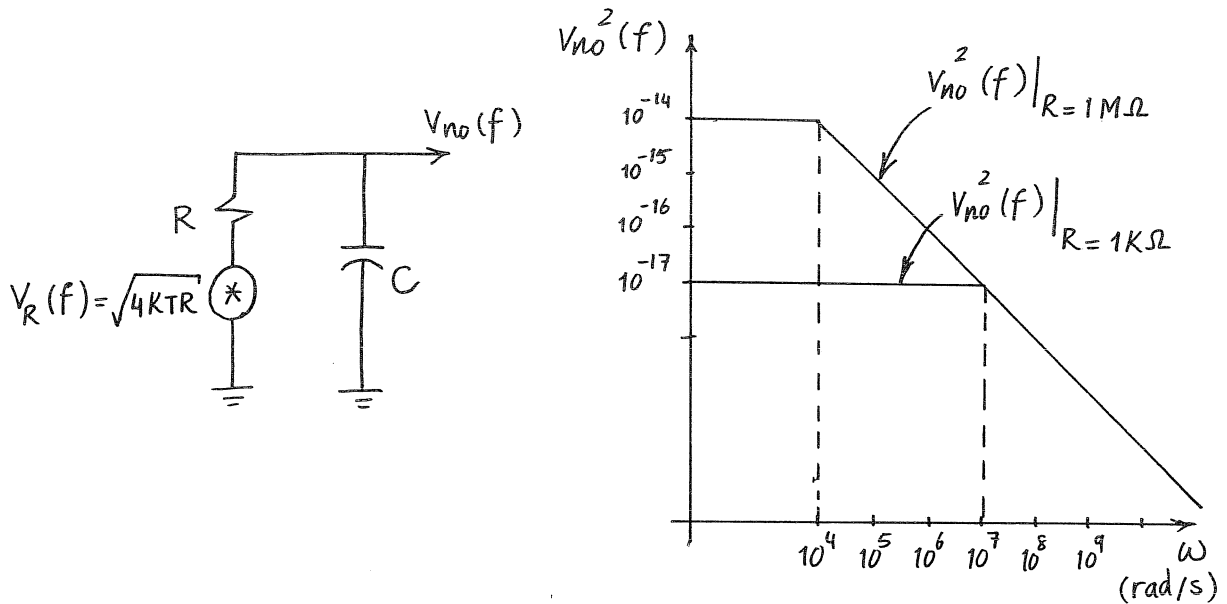
$$\text{and } V_{no}^2(0) = (129 \text{ nV})^2 = 1.66 \times 10^{-14} \text{ V}^2$$



The area underneath both curves are the same and

$$\text{is equal to } \frac{KT}{C} = (6.45 \mu\text{V})^2$$

$$4.7) I_{nf}^2 = 8.28 \times 10^{-25} \left(\frac{\text{A}^2}{\text{Hz}}\right), \quad I_{n1}^2 = 1.656 \times 10^{-24} \left(\frac{\text{A}^2}{\text{Hz}}\right)$$

$$I_{n-}^2(f) = 100 \times 10^{-24} \left(\frac{\text{A}^2}{\text{Hz}}\right)$$

$$V_{no1}^2(0) = (I_{nf}^2(0) + I_{n1}^2(0) + I_{n-}^2(0)) R_f^2$$

$$\approx I_{n-}^2(0) R_f^2 = (0.2 \frac{\mu\text{V}}{\sqrt{\text{Hz}}})^2$$

(cont.)

$$4.7) \text{ (cont.) } V_{no1}^2(\text{rms}) = \left(0.2 \frac{\mu\text{V}}{\sqrt{\text{Hz}}}\right)^2 \times \frac{1}{4(20\text{K})(1\text{n})} = \underline{(22.4 \mu\text{V})^2}$$

$$V_{no2}^2(0) = V_n^2(f) \left(1 + \frac{R_f}{R_1}\right) = \left(60 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2$$

The noise is lowpass filtered at $f_0 = \frac{1}{2\pi R_f C_f} \approx 8 \text{ KHz}$
until $f_1 = \frac{R_f}{R_1} f_0 = 16 \text{ KHz}$.

$$\therefore V_{no2}^2(\text{rms}) = (60 \times 10^{-9})^2 \frac{\pi \times 8\text{K}}{2} + (20 \times 10^{-9})^2 \frac{\pi}{2} (1\text{M} - 16\text{K})$$

$$\approx \underline{(25.9 \mu\text{V})^2}$$

The total output noise is estimated to be:

$$V_{no}^2(\text{rms}) = V_{no1}^2(\text{rms}) + V_{no2}^2(\text{rms}) = (34.2 \mu\text{V})^2$$

$$\Rightarrow \underline{V_{no}(\text{rms}) = 34.2 \mu\text{V rms}}$$

4.8) Since the opamp is assumed to be ideal and noiseless, we have $V_x = 0$ at all times.

$$\therefore V_{nx}^2(f) = 0 \Rightarrow \underline{V_{nx}^2(\text{rms}) = 0}$$

This noise is smaller than $\frac{KT}{1\text{pF}}$ since the voltage across the capacitor is fixed by another device (i.e. opamp).

For the noise at V_o , we have:

$$V_{no}^2(f) = (i_R^2(f) + i_{R_f}^2(f)) \frac{R_f^2}{1 + \omega^2 R_f^2 C^2}$$


$$= \left(\frac{4KT}{R} + \frac{4KT}{R_f}\right) R_f^2 \times \frac{\pi}{2} \frac{1}{2\pi R_f C}$$

(cont.)

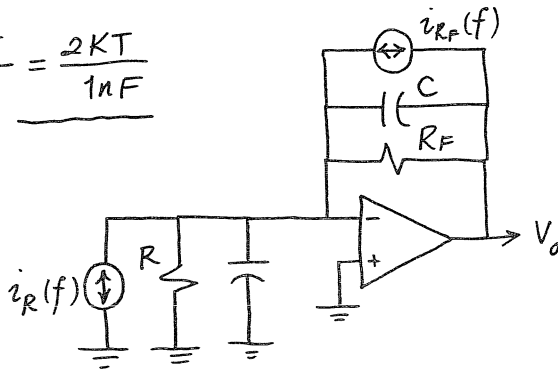4.8) (Cont.)

$$\therefore V_{no}^2(f) = \frac{2KT}{C} = \frac{2KT}{1nF}$$


The noise at V_o is twice as much as $\frac{KT}{1nF}$.



The reason for this increase is the additional noise current source $i_R(f)$. Since the voltage across this current source is fixed (i.e. it is equal to zero), it does not affect the ω_{3dB} of the filter and acts as an ideal noise current source!

$$4.9) \quad I_{no}^2(f) = \left| \frac{R}{R + j\omega L} \right|^2 I_R^2(f)$$
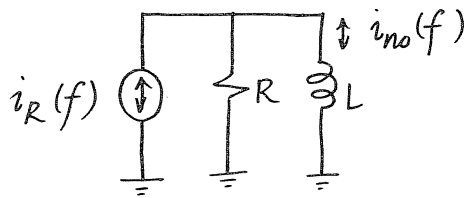
$$= \frac{1}{1 + \frac{L^2}{R^2} \omega^2} \frac{4KT}{R}$$



$$I_{no}^2(rms) = \int_0^\infty \frac{4KT/R}{1 + \frac{L^2}{R^2} \omega^2} df$$

$$= \frac{4KT}{R} \frac{1}{2\pi} \frac{R}{L} \int_0^\infty \frac{d\omega}{1 + \omega^2} = \frac{KT}{L}$$

4.10) a) For circuit (I) :

$$\frac{V_o}{V_i} = \frac{-1}{1 + j\omega(7K)(80n)} \quad (1)$$

For circuit (II) :

$$\left(\frac{V_o}{2} (j\omega(80n)) + \frac{V_i}{14K} \right) 14K = -V_o$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{-1}{1 + j\omega(80n)(7K)} \quad (2)$$

(1) & (2) show identical transfer functions.

$$b) V_{no}^2(0) = [I_{n1}^2(f) + I_{nf}^2(f)] R_f^2 = \left(15.2 \frac{nV}{\sqrt{Hz}} \right)^2$$

$$\therefore V_{no(rms)}^2 = V_{no}^2(0) \frac{1}{4R_f C_f} = \underline{\underline{(0.32 \mu V)^2}}$$

c) the transfer function for current source entering the negative terminal of opamp 1 is :

$$\frac{V_o}{I_{i1}} = \frac{-R_f}{1 + j\omega \frac{C_f R_f}{2}}$$

$$\Rightarrow V_{no1}^2(f) = [I_{n1}^2(f) + I_{nf}^2(f)] \frac{R_f^2}{1 + \omega^2 \frac{C_f^2 R_f^2}{4}}$$

$$V_{no1}^2(0) = [I_{n1}^2(f) + I_{nf}^2(f)] R_f^2 = \left(21.5 \frac{nV}{\sqrt{Hz}} \right)^2$$

$$V_{no1(rms)}^2 = V_{no1}^2(0) \frac{1}{4 \frac{R_f C_f}{2}} = \underline{\underline{(0.45 \mu V)^2}}$$

the transfer function for the current source entering the negative terminal of opamp 2 is :

$$\frac{V_o}{I_{i2}} = \frac{-R_2}{1 + \frac{1}{j\omega C_f R_f / 2}} = \frac{-j\omega R_2 R_f C_f / 2}{1 + j\omega C_f R_f / 2}$$

(cont.)

4.10) (cont.) This is the transfer function of a high-pass filter, which means, ideally, the total output noise due to any current noise at the negative terminal of opamp 2 is ∞ .

$$4.11) \quad \frac{V_o}{V_i} = \frac{-R_F/R_1}{1 + j\omega C_F R_F}$$

C_F is reduced by a factor of 1000. Therefore, to keep the same transfer function, R_F & R_1 must be increased by the same factor. The parameters of the new circuit are:

$$R_F = 7M\Omega, \quad R_1 = 7M\Omega, \quad C_F = 80 \text{ pF}$$

$$\Rightarrow V_{no}^2(0) = [I_{n1}^2(f) + I_{nf}^2(f)] R_F^2 = 8KT R_F$$

$$V_{no}^2(\text{rms}) = 8KT R_F \frac{1}{4R_F C_F} = \frac{2KT}{C_F}$$


\therefore the total noise power is just a function of C_F (for the case $R_F = R_1$) and increases by decreasing C_F :

$$V_{no}^2(\text{rms}) = \underline{(10.2 \mu\text{V})^2}$$

4.12) The $\frac{1}{f}$ tangent line touches the spectral density of Fig. 4.3 at 1000 Hz. The noise power can be estimated

$$\text{as: } V_n^2(\text{rms}) = 10 \frac{(\mu\text{V})^2}{\text{Hz}} \times \frac{\pi \times 1000}{2} = \underline{(125 \mu\text{V})^2}$$

4.13)

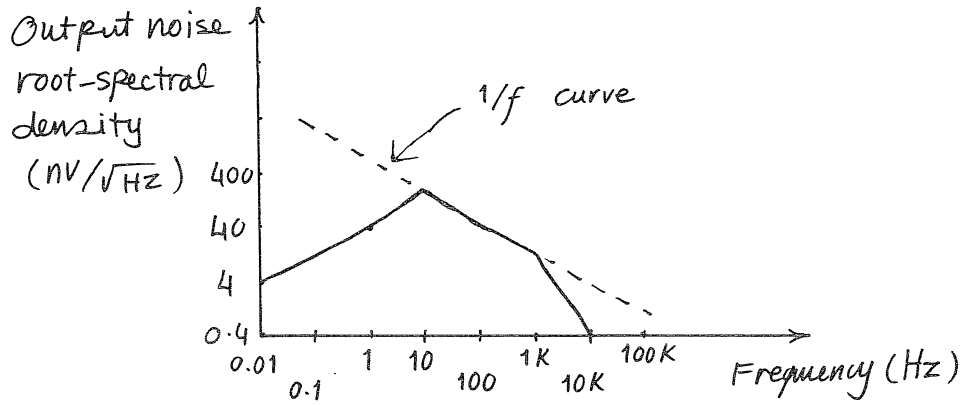

Estimate output noise by integrating from 1 to 10KHz

$$V_{ho(rms)}^2 \cong \int_1^{10} 40^2 f df + \int_{10}^{1k} \frac{400^2}{f} df + \int_{1k}^{10k} \frac{0.4^2 (10k)^2}{f^2} df$$

$$= 7.92 \times 10^4 (mV)^2 + 7.37 \times 10^5 (mV)^2 + 1.44 \times 10^4 (mV)^2$$

$$= 8.31 \times 10^5 (mV)^2 \cong (1 \mu V)^2 \quad \text{Roughly } 1 \mu V \text{ RMS}$$

4.14) A: Graphical Approach

$$\text{Region 1: } 0.01 < f < 1 \quad V_n^2(f) = \left| \frac{10n}{\sqrt{f}} \frac{V}{\sqrt{Hz}} \right|^2 = \frac{10^{-16}}{f} \frac{V^2}{Hz}$$

$$\Rightarrow V_{n1}^2 = \int_{0.01}^1 V_n^2(f) df = 4.6 \times 10^{-16} V^2$$

$$\text{Region 2: } 1 < f < 100 \quad V_n^2(f) = 10^{-16} \frac{V^2}{Hz}$$

$$\Rightarrow V_{n2}^2 = 99 \times 10^{-16} V^2$$

$$\text{Region 3: } 100 < f < 1K \quad V_n^2(f) = \frac{10^{-12}}{f^2} \frac{V^2}{Hz}$$

$$\Rightarrow V_{n3}^2 = \int_{100}^{1K} \frac{10^{-12}}{f^2} df = 90 \times 10^{-16} V^2$$

$$\text{Region 4: } 1K < f < \infty \quad V_{n4}^2 = 10^{-18} \times \frac{\pi}{2} \times 9000 = 14.1 \times 10^{-15} V^2$$

$$\therefore V_n(rms)^2 = V_{n1}^2 + V_{n2}^2 + V_{n3}^2 + V_{n4}^2 = \underline{(0.18 \mu V)^2}$$

(cont.)

4.14) (cont.) B: Using $\frac{1}{f}$ tangent line

The $\frac{1}{f}$ line touches the curve at 100 Hz & 10 KHz simultaneously. If we approximate the noise at 100Hz and 10KHz with two lowpass-filtered noise, we will

$$\text{have: } V_n^2 = 10^{-16} \times \frac{\pi}{2} \times 100 + 10^{-18} \times \frac{\pi}{2} \times 9000 = \underline{(0.17 \mu V)^2}$$

$$4.15) \quad A(s) = \frac{A_0}{\left(1 + \frac{s}{2\pi f_0}\right)^2} \Rightarrow A(j\omega) = \frac{A_0}{\left(1 + j\frac{f}{f_0}\right)^2}$$

$$\Rightarrow \text{equivalent noise bandwidth} = \frac{1}{A_0^2} \int_0^\infty |A(j\omega)|^2 df$$

$$= f_0 \int_0^\infty \frac{df}{(1+f^2)^2} = \underline{f_0 \frac{\pi}{4}}$$

4.16) The equivalent circuits for noise calculations are shown below:

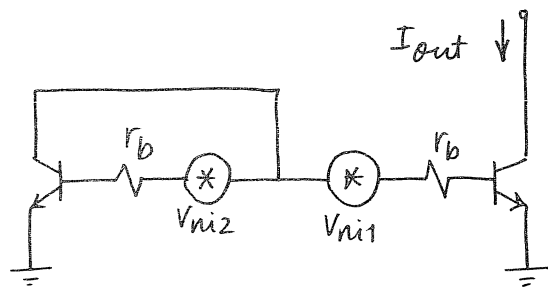


Fig. P4.16(a)

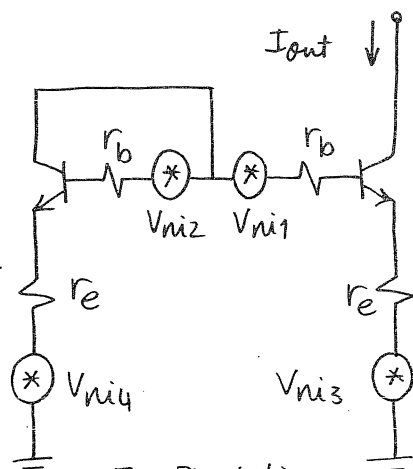


Fig. P4.16(b)

(cont.)

4.16) (cont.) SNR for the current mirror of Fig. P4.16(a):

Using superposition for V_{ni1} & V_{ni2} , and approximating

$\beta + 1 \approx \beta = 100$, we have:

$$I_{no}^2(f) = [V_{ni1}^2(f) + V_{ni2}^2(f)] \frac{\beta^2}{(r_b + r_{\pi})^2}$$

$$\text{where } V_{ni1}^2(f) = V_{ni2}^2(f) = 4kT r_b = 5.46 \frac{(nV)^2}{Hz}$$

$$\text{and } r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = 2.6 k\Omega$$

$$\therefore I_{no}^2(f) = 0.0127 \frac{(nA)^2}{Hz}$$

$$\therefore I_{no(rms)}^2 = 50 \text{ MHz} \times I_{no}^2(f) = (0.8 \mu A)^2$$

$$\therefore \text{SNR} = 20 \log \frac{100 \mu}{0.8 \mu} = \underline{41.94 \text{ dB}}$$

SNR for the current mirror of Fig. P4.16(b):

$$I_{no}^2(f) = [V_{ni1}^2(f) + V_{ni2}^2(f) + V_{ni3}^2(f) + V_{ni4}^2(f)] \frac{\beta^2}{(r_b + r_{\pi} + \beta r_e)^2}$$

$$\text{where } V_{ni3}^2(f) = V_{ni4}^2(f) = 4kT r_e = 3.31 \frac{(nV)^2}{Hz}$$

$$V_{ni1}^2(f) = V_{ni2}^2(f) = 4kT r_b = 5.46 \frac{(nV)^2}{Hz}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = 2.6 k\Omega$$

$$\therefore I_{no}^2(f) = 0.0003336 \frac{(nA)^2}{Hz}$$

$$\therefore I_{no(rms)}^2 = 50 \text{ MHz} \times I_{no}^2(f) = (0.13 \mu A)^2$$

$$\therefore \text{SNR} = 20 \log \frac{100 \mu}{0.13 \mu} = \underline{57.7 \text{ dB}}$$

$$4.17) \text{ Using (4.61): } V_{no1}^2(0) = (I_{n1}^2(0) + I_{nf}^2(0) + I_{n-}^2(0)) R_F^2$$

$$\text{where } I_{nf}^2(f) = \frac{4KT}{R_F} = 1.035 \left(\frac{\text{pA}}{\sqrt{\text{Hz}}} \right)^2$$

$$\therefore V_{no1}^2(0) = (2 \times 0.6^2 + 1.035) (16\text{K})^2 \left(\frac{\text{pV}}{\sqrt{\text{Hz}}} \right)^2 = (21.2 \frac{\text{nV}}{\sqrt{\text{Hz}}})^2$$


$$V_{no1}^2(\text{rms}) = V_{no1}^2(0) \times \frac{1}{4R_F C_F} = (2.65 \mu\text{V})^2$$

$$\text{Using (4.62): } V_{no2}^2(0) = V_n^2(f) \left(1 + \frac{R_F}{R_1} \right)^2 = (220 \frac{\text{nV}}{\sqrt{\text{Hz}}})^2$$

this noise is lowpass filtered at $f_0 = \frac{1}{2\pi R_F C_F}$

until $f_1 = \frac{R_F}{R_1} f_0$

where the noise gain reaches unity.

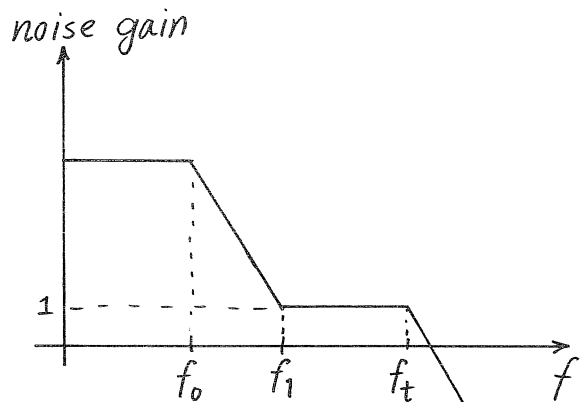

$$V_{no2}^2(\text{rms}) = (220 \times 10^{-9})^2 \frac{1}{4R_F C_F} + (20 \times 10^{-9})^2 \frac{\pi}{2} (f_t - f_1)$$

$$= (44.16 \mu\text{V})^2$$

$$\text{Using (4.64): } \underline{V_{no}^2(\text{rms}) = (44.24 \mu\text{V})^2}$$

$$\text{SNR for a } 100 \text{ mV signal} = 20 \log \frac{100 \text{ m}}{44.24 \mu}$$

$$= \underline{67.08 \text{ dB}}$$

4.18) Using (4.97):

$$\begin{aligned} V_{\text{neg}}^2(f) &= \left(\frac{16}{3}\right) KT \frac{1}{g_{m1}} + \frac{16}{3} KT \left(\frac{g_{m3}}{g_{m1}}\right)^2 \frac{1}{g_{m3}} \\ &= \underline{\underline{\left(5.75 \frac{nV}{\sqrt{Hz}}\right)^2}} \end{aligned}$$

Since $g_m \propto \sqrt{I_{\text{BIAS}}}$, if I_{BIAS} is doubled, g_{m1} & g_{m3} will be increased by $\sqrt{2}$. Therefore, $V_{\text{neg}}^2(f)$ will be reduced by $\sqrt{2}$, and we have:

$$V_{\text{neg}}^2(f) = \frac{1}{\sqrt{2}} \left(5.75 \frac{nV}{\sqrt{Hz}}\right)^2 = \underline{\underline{\left(4.84 \frac{nV}{\sqrt{Hz}}\right)^2}}$$