

TSTE12 Design of Digital Systems Lecture 8

Kent Palmkvist



TSTE12 Design of Digital Systems, Lecture 8

2024-09-19 2

Agenda

- Practical issues
- Hardware description
 - FPGA
- HDL based design

TSTE12 Deadlines Y,D,ED

- Final version of design sketch and project plan this week
 - Show implementation ideas, show sequence of implementation and task partitioning between group members
- Weekly meetings should start
 - Internal weekly meeting with transcript sent to supervisor
- Lab 2 deadline tuesday next week (24/9)

TSTE12 Deadlines MELE, erasmus

- Final requirement specification this week
- First version of design specification and projekt plan tuesday next week (24/9)
- Wednesday 25 September 21.00: Lab 2 soft deadline
 - Lab 2 results will be checked after project completed

Handin (homework), Individual!

- 1st handin deadline Monday 23 September 23:30
- Use only plain text editor (emacs, vi, modelsim or similar) for code entry.
- Solve tasks INDIVIDUALLY
- Submit answers using Lisam assignment function
 - 4 different submissions for code, one for each code task
 - 1 submission for all theory question answers
- Use a special terminal window when working with handins
module load TSTE12 ; TSTE12handin


Control units

- Hard wired
 - Moore (output only dependent on state)
 - Mealy (output dependent on state and input)
 - Fast
 - Custom designed
- Microcoded
 - Cheap
 - Standardized (easy to reuse)

Microcoded control unit

- General structure

 - AG = Address generator
- MAR = Memory Address Register
- MIR = Memory Instruction register



Microcoded control unit

- Advantages


- Easy to create a generic design
- Only ROM contents needs to be replaced
- Easy to change existing design
- Short design time (low design cost)
- May use compiler to create ROM contents

- Drawbacks

- Slower in many cases (ROM must be read)
 - Only Moore type of controllers
- Small controllers are more expensive due to extra register and ROM
- Must be designed for worst case regarding required features


Microcoded control unit, example

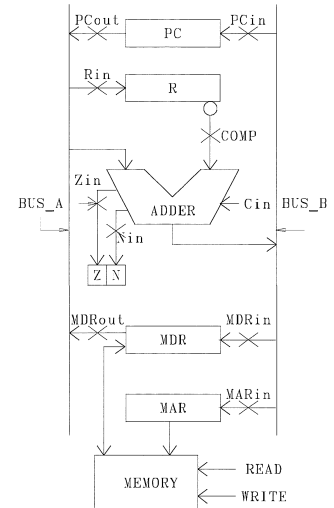- Controller for an extremely small RISC processor
 - 4 register (PC, R, MDR, MIR)
 - 1 subtraction unit
 - Some multiplexers and busses
 - Use the same add unit both for instruction operation and PC update
 - Cost: 9 clock cycles per instruction
- Only one instruction: subtract with branch on negative result
 - 3 byte instruction
 - 1st operand address, 2nd operand address, branch address



Controller for structure

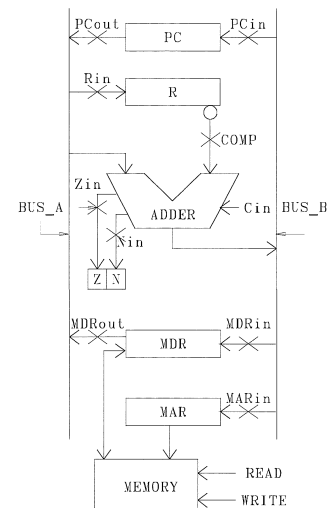- One instruction execution
 0. PCout,Zin,MARin,READ,ZEND
 1. MDRout,MARin,READ
 2. MDRout,Rin
 3. Pcout,Cin,PCin,MARin,READ
 4. MDRout,MARin,READ
 5. MDRout,COMP,Cin,Nin,MDRin,WRITE
 6. PCout,Cin,PCin,MARin,READ
 7. PCout,Cin,PCin,NNEND
 8. MDRout,Pcin
- 2 loops, 0-7 or 0-8



Control with two jumps, microcoded

- All control steps described in a ROM table
- Easy to understand
- Easy to redesign

```

----- The microinstructions ROM -----
ROM: process(C)
  type SQ_ARRAY is array(0 to 8,0 to 8) of BIT;
  constant MEM : SQ_ARRAY:=
  -- 0      1      2      3      4      5      6      7      8      COLUMN
MDR_OUT,MAR_IN,N_IN,R_IN,PC_IN,ZEND,C_IN,WRITE,NNEND,micins
(('0',    '1',  '0',  '0',  '0',  '1',  '0',  '0',  '0'), --0
 ('1',    '1',  '0',  '0',  '0',  '0',  '0',  '0',  '0'), --1
 ('1',    '0',  '0',  '1',  '0',  '0',  '0',  '0',  '0'), --2
 ('0',    '1',  '0',  '0',  '0',  '1',  '0',  '1',  '0'), --3
 ('1',    '1',  '0',  '0',  '0',  '0',  '0',  '0',  '0'), --4
 ('1',    '0',  '1',  '0',  '0',  '0',  '1',  '1',  '0'), --5
 ('0',    '1',  '0',  '0',  '0',  '1',  '0',  '1',  '0'), --6
 ('0',    '0',  '0',  '0',  '1',  '0',  '1',  '0',  '1'), --7
 ('1',    '0',  '0',  '0',  '1',  '0',  '0',  '0',  '0'))--8
begin
  MDR_OUT <= MEM(INTVAL(C),0) after ROM_DEL;
  MAR_IN  <= MEM(INTVAL(C),1) after ROM_DEL;
  N_IN    <= MEM(INTVAL(C),2) after ROM_DEL;
  R_IN    <= MEM(INTVAL(C),3) after ROM_DEL;
  PC_IN   <= MEM(INTVAL(C),4) after ROM_DEL;
  ZEND    <= MEM(INTVAL(C),5) after ROM_DEL;
  C_IN    <= MEM(INTVAL(C),6) after ROM_DEL;
  WRITE   <= MEM(INTVAL(C),7) after ROM_DEL;
  NNEND   <= MEM(INTVAL(C),8) after ROM_DEL;
end process ROM;

```

URISC controller, Mealy

- Inclear sequence
- Hard to modify
- Faster

```

--Hard Wired Control Unit
--Decoder
--First Stage Decoding
ST0 <= not C(2) and not C(1) and not C(0) after AND_DEL;
ST1 <= not C(2) and not C(1) and C(0) after AND_DEL;
ST2 <= not C(2) and C(1) and not C(0) after AND_DEL;
ST3 <= not C(2) and C(1) and C(0) after AND_DEL;
ST4 <= C(2) and not C(1) and not C(0) after AND_DEL;
ST5 <= C(2) and not C(1) and C(0) after AND_DEL;
ST6 <= C(2) and C(1) and not C(0) after AND_DEL;
ST7 <= C(2) and C(1) and C(0) after AND_DEL;
--Second Stage Decoding
ST07 <= ST0 or ST7 after OR_DEL;
ST25 <= ST2 or ST5 after OR_DEL;
ST36 <= ST3 or ST6 after OR_DEL;
ST57 <= ST5 or ST7 after OR_DEL;
ST78 <= ST7 or C(3) after OR_DEL;
--Control Signals
PC_OUT <= (ST07 or ST36) and not C(3)
          after (OR_DEL + AND_DEL);
C_IN <= ST36 or ST57 after OR_DEL;
PC_IN <= ST36 or ST78 after OR_DEL;
MAR_IN <= not(ST25 or ST78) after (OR_DEL + INV_DEL);
MDR_OUT <=not PC_OUT after INV_DEL;
READ <= MAR_IN; COMP <= ST5; N_IN <= ST5; MDR_IN <= ST5;
WRITE <= ST5; R_IN <= ST2; ZIN <= ST0; ZEND <=ST0;
NNEND <= ST7;

```

More on microcoded controllers

- Lecture 11 will cover more details on microcoded controller structures
 - Introduces also lab 3
- Lab 3 includes an example of a microcoded controller structure
 - Controller used to control a user interface and a datapath
 - Y and D program students have seen this approach in computer technology courses
 - Used there for creating machine instruction implementations

Gate level simulation

- All designs will eventually reach the gate level
- Need accuracy to allow check of timing requirements
 - Setup time on flip-flops
 - Clock signals
 - Races, hazards
 - Glitch example (inverter + and with rising edge input)
- Models must be efficient
 - Large number of gates
 - Slow simulation due to accuracy
 - Still much faster than spice simulation

How accurate can a gate model be?

- Example: 2 input OR-gate

Entity OR2 IS

Port (I1, I2 : in bit; O : out bit);

END OR2;

Architecture DELTA_DEL of OR2 IS

BEGIN

O <= I1 OR I2;

END DELTA_DEL;

Architecture FIXED_DEL OF OR2 IS

BEGIN

O <= I1 OR I2 after 3 ns;

END FIXED_DEL;

ENTITY OR2G IS

Generic (DEL: TIME)M

Port (I1, I2 : in bit; O : out bit);

END OR2G;

Architecture GNR_DEL of OR2G IS

BEGIN

O <= I1 OR I2 after DEL;

END GNR_DEL;

Model accuracy

- Models are better and better, but not good enough
 - Multiple timing models required
 - typical delay, max, min
- Want single model, only changing one constant
 - Timing_CONTROL
 - Set one constant to define type of timing (min, max, typical)

Code example

```
use work.TIMING_CONTROL.all;
entity OR2_TV is
  generic(TMIN,TMAX,TTYP: TIME);
  port(I1,I2: in BIT; O: out BIT);
end OR2_TV;

architecture VAR_T of OR2_TV is
begin
  O <= I1 or I2 after T_CHOICE(TIMING_SEL,
                               TMIN,TMAX,TTYP);
end VAR_T;
```

```
package TIMING_CONTROL is
  type TIMING is (MIN,MAX,TYP,DELTA);
  constant TIMING_SEL: TIMING := TYP;
  function T_CHOICE(TIMING_SEL: TIMING;
                    TMIN,TMAX,TTYP: TIME)
    return TIME;
end TIMING_CONTROL;

package body TIMING_CONTROL is
  function T_CHOICE(TIMING_SEL: TIMING;
                    TMIN,TMAX,TTYP: TIME)
    return TIME is
  begin
    case TIMING_SEL is
      when DELTA => return 0 ns;
      when TYP => return TTYP;
      when MAX => return TMAX;
      when MIN => return TMIN;
    end case;
  end T_CHOICE;
end TIMING_CONTROL;
```

Additional timing details

- Timing is asymmetric
 - Different rise and fall times
 - Needs modeling

```
entity OR2GV is
  generic(TPLH,TPHL: TIME);
  port(I1,I2: in BIT; O: out BIT);
end OR2GV;

architecture VAR_DEL of OR2GV is
begin
  process(I1,I2)
    variable OR_NEW,OR_OLD:BIT;
  begin
    OR_NEW := I1 or I2;
    if OR_NEW = '1' and OR_OLD = '0' then
      O <= OR_NEW after TPLH;
    elsif OR_NEW = '0' and OR_OLD = '1' then
      O <= OR_NEW after TPHL;
    end if;
    OR_OLD := OR_NEW;
  end process;
end VAR_DEL;
```

Load dependency


- Every attached gate input slows the output speed
 - Large fan-out
 - Load is gate dependent
 - Number of transistor gates connected
 - Size of transistors on input gate
- Each connection corresponds to a small delay
 - Model each individual input wire delay
 - Gate delay included in output wire delay
- Not good enough still
 - Delay depends on edge slope, temperature, etc.

Common model used in synopsis library compiler

- $D_{\text{TOTAL}} = D_I + D_S + D_T + D_C$
- D_I = Intrinsic delay inherent in gate and independent of where/how it is used
- D_S = Slope delay caused by ramp time of the input signal
- D_T Transition delay caused by loading of the output pin (approx $R_{\text{driver}} (C_{\text{wire}} + C_{\text{pin}})$)
- D_C Connect media delay to an input pin (wire delay).

Different max and min

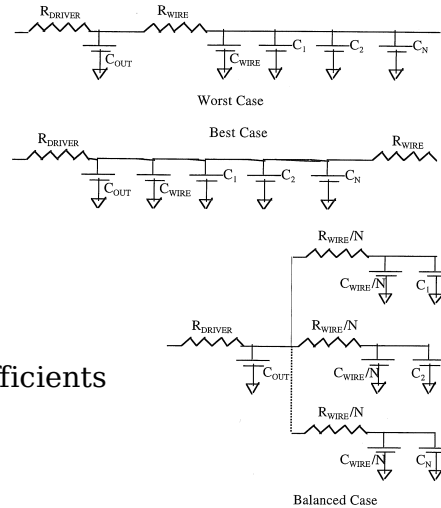- Wire delay (D_C) more complicated
 - Worst case
 - Best case
 - Balanced
- Technology library
 - Large amount of information
 - Usually described as tables
 - Sometimes described as polynomial coefficients



Back annotation

- The process of abstraction
 - adding more details to a high level model by analyzing a lower abstraction level model
 - Example: Layout information used to generate timing information in a gate netlist
- Standardized way: SDF
 - Add timing info from layout to gate level
 - Useful for general timing requirements and properties)
 - Delays module path, device, interconnect, and port

SDF file format

- Timing checks: setup, hold, recovery, removal, skew, width, period, and no change
- Timing constraints: path, skew, period, sum, and diff
- Each trippel defines min, typical, and max delay
 - One for positive edge
 - One for negative edge

```
(CELL
  (CELLTYPE "DFF")
  (INSTANCE top/b/c)
  (DELAY
    (ABSOLUTE
      (IOPATH (posedge clk) q (2:3:4) (5:6:7))
      (PORT clr (2:3:4) (5:6:7))
    )
  )
  (TIMINGCHECK
    (SETUPHOLD d (posedge clk) (3:4:5) (-1:-1:-1))
    (WIDTH clk (4.4:7.5:11.3))
  )
)
```

SDF File format, cont.

- Design/instance-specific or type/library-specific data
- Timing environment:
 - intended operating timing environment
 - Scaling, environmental, and technology parameters
- Incremental delay builds on the previous models timing by adding/subtracting timing information
- Absolute replaces timing information

Gate models of increasing complexity

- Creating accurate library models is time consuming
- Delay, timechecks etc. can be done in many different ways
- A standard has evolved that defines what parameters to use
 - Simplifies back annotation
 - Allows for accelerated models (hard-coded)

VITAL models of gates

- Three parts: Input delay, Functional and Path delay

```
library IEEE;
use IEEE.VITAL_Primitives.all;
library LIBVUOF;
use LIBVUOF.VTABLES.all;
architecture VITAL of ONAND is
  attribute VITAL_LEVEL1 of VITAL : architecture is TRUE;
  SIGNAL A_ipd : STD_ULOGIC := 'X';
  SIGNAL B_ipd : STD_ULOGIC := 'X';
  SIGNAL C_ipd : STD_ULOGIC := 'X';
  SIGNAL D_ipd : STD_ULOGIC := 'X';
begin
  -- INPUT PATH DELAYS
  WireDelay : block
  begin
    VitalWireDelay (A_ipd, A, tpd_A);
    VitalWireDelay (B_ipd, B, tpd_B);
    VitalWireDelay (C_ipd, C, tpd_C);
    VitalWireDelay (D_ipd, D, tpd_D);
  end block;
```

```
-- BEHAVIOR SECTION
VITALBehavior : process (A_ipd, B_ipd, C_ipd, D_ipd)
-- functionality results
  VARIABLE Results: STD_LOGIC_VECTOR(1 to 1):=(others => 'X');
  ALIAS Y_zd : STD_LOGIC is Results(1);
-- output glitch detection variables
  VARIABLE Y_GlitchData : VitalGlitchDataType;
begin
  -- Functionality Section
  Y_zd := (NOT ((D_ipd) AND ((B_ipd) OR (A_ipd) OR C_ipd)))));
  -- Path Delay Section
  VitalPathDelay01 (
    OutSignal => Y,
    GlitchData => Y_GlitchData,
    OutSignalName => "Y",
    OutTemp => Y_zd,
    Paths => (0 => (A_ipd'last_event, tpd_A_Y, TRUE),
              1 => (B_ipd'last_event, tpd_B_Y, TRUE),
              2 => (C_ipd'last_event, tpd_C_Y, TRUE),
              3 => (D_ipd'last_event, tpd_D_Y, TRUE)),
    Mode => OnDetect,
    Xon => Xon,
    MsgOn => MsgOn,
    MsgSeverity => WARNING);
  end process;
end VITAL;
```

Detection of timing errors

- Input path delay: Transport delay dependent on previous value and wire delay
- Functional part. Boolean expression or lookup tables for fast simulation
- Path delay: output delay, glitch handling
- Models often includes error detection
 - Short spikes, short setup/hold timing etc.
 - Unacceptable values (Z or X)
 - Unacceptable input combinations (both set and reset active on SR flipflop)

Hardware overview


- Detailed description of Hardware
- Standard parts
 - TTL (SSI, MSI LSI)
 - Memories, microprocessors, I/O
- ASIC (Application Specific Integrated Circuit)
 - Integrated circuit that has been produced for a specific application and (often) produced in small numbers
 - Memories and microprocessors are general application devices

ASIC technologies

- May use different technologies for ASIC: PLD, Gate array, FPGA, Standard cell, custom. ASIC is however limited to Standard cell and gate array. Custom design is also used.
- CMOS switch. Power consumption: $P \sim CV^2f$
 - Use low power supply, reduce clock, reduce area
- Transistor channel length (old measure of chip manufacturing process) shorter than 0.01 μm (so called 4 nm used today, e.g. TSMC N4P process in Ryzen 9000 series CPUs, 3 nm in Apple A18 Pro in Iphone 16)


Gate array, mask programmable

 - Predefined pattern of transistors
 - Add interconnect metal for each design
 - Fast manufacture (weeks)
 - No transistor sizing
- Example shows inverter design
- Combined with library of existing cells
 - Basic gates, flipflops etc.



Standard cell

 - Transistor placement and metal layers unique for each design, needs to be manufactured
- Limited number of layout cell types (Cell library)
- Cells already characterized
- Slow manufacture (month)




Full custom layout

- Full custom
 - Individual placement and scaling of transistors
 - Full control of wires and connections
 - Maximum control, maximum effort
- Complete freedom to place and route transistors
 - Not limited to existing logic style/library
 - Slow manufacture (months)
 - Higher performance than standard cells
- Requires more testing (simulation)

Programmable devices: PLD

 - Input variables forming AND-OR arrays, flipflops at the outputs.
 - Crosspoint can connect to create products
- Inputs and outputs on chip edge
- Only small circuit designs



Programmable devices: CPLD

- Combine PLD structure with additional onchip interconnect
 - Support larger designs


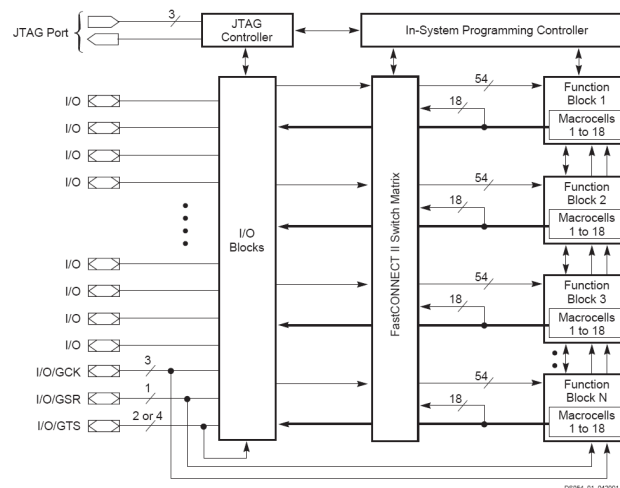


Figure 1: XC9500XL Architecture

FPGA structure

 - Field Programmable Gate Array
- Cells in an array, special I/O blocks around the edges.
- Between cells (CLBs or LEs) are routing wires located (interconnect)




FPGA building blocks

- CLB/Logic Element
 - Different name in different manufacturers designs
 - In many cases are they based on lookup tables (i.e., no simple gates, instead more advanced functions) => less need for routing channels (that are expensive). Lookup table can be viewed as a small RAM or a MUX with fixed inputs.
 - Trade off between big lookup tables and utilization. Optimal around 4-6 bits address.
 - Often a flip-flop included in the CLB/LE


CLB Example: Xilinx (AMD) Spartan II

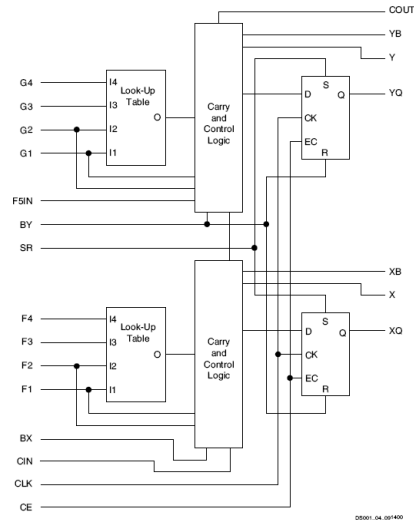- Choose positive or negative clock edge
- May combine lookup tables
- CLB may be rearranged into a memory or shift register




Xilinx Spartan II I/O logic

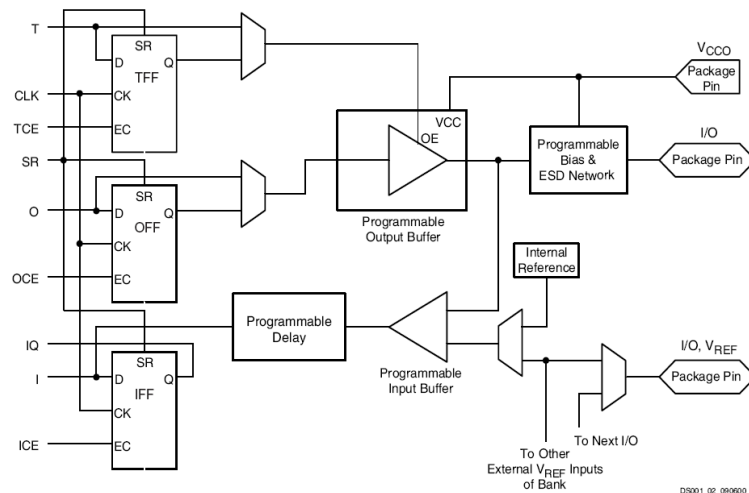- Support multiple I/O standards
 - 3.3V, 1.8V, 1.2V etc.
 - Differential
- Flipflops located close to pin
 - Reduce delays due to routing signal to pin
- Different drive strength




Other FPGA example: Altera (intel) Cyclone

 - Same basic structure
 - Logic Array
 - Separate I/O blocks
 - Dedicated memory
 - PLL for internal clock generation





Altera (Intel) Cyclone

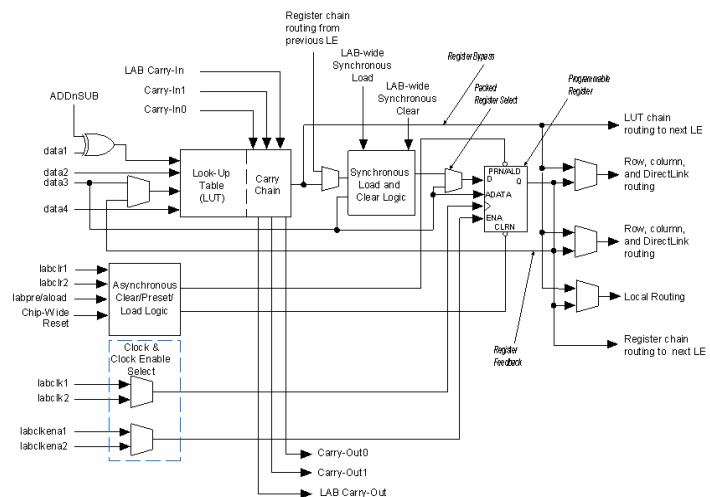- Logic element structure
 - More detailed description
 - One Lookup table + one flipflop




Alternative FPGA structure: Actel (Microsemi)

  - Smaller functions
- Separate register from combination logic



Programming of FPGA

 - Two types: reprogrammable or one-time programmable
- Control a CMOS-switch using a RAM/EPROM/EEPROM-cell. The CMOS switch is slow (compared to the alternative)
- The alternative is fuse/Antifuse (burn together two wires by using high voltage)



Important aspects

- Speed of the switched (impedance, capacitans). Many switches in series ruins the performance
- Reprogrammable? Needs any design changes to be done?
- Volatile designs? What happens at power failure? How is the design put into the chip? How long delay from power on to working design?
- Area of the switches? Needs many switches?

Technology comparison table

- | | | | | | |
|-----------------|------------------|-------|----------|-------|--------------|
| | Volatile | SRAM | Antifuse | EPROM | EEPROM/FLASH |
| • Most common | no | yes | no | no | no |
| - SRAM | Re-programmable | yes | no | yes | yes |
| - EEPROM/FLASH | Chip area | large | small | small | average |
| • Xilinx/Altera | R (routing nets) | large | small | large | large |
| - SRAM/EEPROM | C | large | small | large | large |
- Actel
 - Antifuse
 - Do also create classic FPGA (SRAM/EEPROM based)
 - SRAM based FPGA usually support automatic configuration from serial flash memory at power-on

How to configure the FPGA

- Non-volatile technology
 - FLASH, EEPROM, PROM, etc.
- External programmer
 - Software on PC to program device
- External ROM/FLASH
 - Standard FLASH
 - Serial FLASH
- Embedded microcontroller
 - Boot application configures FPGA
 - Not possible if flash needed for CPU operation

FPGA configuration, cont.

- Large volumes may use non-programmable devices based on FPGA
 - Resynthesize: may give different behavior
 - Strip FPGA: Remove configuration logic

FPGA hardware options

- Multipliers
- DSP blocks
 - Multiply-accumulate
 - Common operation in DSP
 - High precision (> 20 bits)
- Optimized I/O support
 - Differential signaling
 - Low swing/current steering

FPGA hardware options, cont.

- Clock circuits
 - Phase locked loops (PLL), Delay locked loops (DLL)
 - Clock tree distribution
- Serializer/deserializer
 - Support modern PC bus standards such as PCI Express
 - Dedicated block to send/recieve high speed ($> \text{Gbit/s}$) serial data
 - Reduce number of I/O pins

FPGA hardware options, cont.

- A/D and D/A converters
- Memory units
- CPU
 - e.g., physical powerpc or ARM core inside FPGA
 - Usually combined with external memory interfaces and CPU-based I/O support (e.g. wired ethernet, SD-card reader etc.)
- Alternative to dedicated CPU hardware: soft cpu
 - VHDL design of a processor
 - Allows for modification of processor structure

ASIC vs FPGA


- ASIC have a large NRE cost
 - Non-Recurring Engineering cost, price of 1st unit
- FPGA have large per unit cost
- Selection of technology depend on
 - Performance requirements
 - Number of units
 - Time to market

HDL based design

- Structured design using HDL
- FSM descriptions

 Example: Combination logic


- Binary comparison. Compare two two-bit words
 - GE: Greater or equal
 - LE: Less or equal
 - E: Equal
 - G: Greater
 - L: Less



```
entity COM is
  generic (D:time);
  port (N1, N0, M1, M0: in BIT;
        GE, LE, E, G, L: out BIT);
end COM;
```

Descriptions

- ROM
 - Table lookup

 

```

use work.TRUTH4x5.all;
architecture TABLE of COM is
begin
  process (N1,N0,M1,M0)
    variable INDEX: INTEGER;
    variable WOUT: WORD;
  begin
    INDEX := INTVAL (N1&N0&M1&M0);
    WOUT := TRUTH (INDEX);
    GE <= WOUT(4) after D;
    LE <= WOUT(3) after D;
    E <= WOUT(2) after D;
    G <= WOUT(1) after D;
    L <= WOUT(0) after D;
  end process;
end TABLE;

```

```

package TRUTH4x5 is
  constant NUM_OUTPUTS: INTEGER:=5;
  constant NUM_INPUTS: INTEGER:=4;
  constant NUM_ROWS: INTEGER:= 2 ** NUM_INPUTS;
  type WORD is array(NUM_OUTPUTS-1 downto 0) of BIT;
  type ADDR is array(NUM_INPUTS-1 downto 0) of BIT;
  type MEM is array (0 to NUM_ROWS-1) of WORD;
  constant TRUTH: MEM :=
    ("11100", "01001", "01001", "01001",
     "10010", "11100", "01001", "01001",
     "10010", "10010", "11100", "01001",
     "10010", "10010", "10010", "11100");
  function INTVAL(VAL:ADDR) return INTEGER;
end TRUTH4x5;

```


```

package body TRUTH4x5 is
  function INTVAL(VAL: ADDR) return INTEGER is
    variable SUM: INTEGER:=0;
  begin
    for N in VAL'LOW to VAL'HIGH loop
      if VAL(N) = '1' then
        SUM := SUM + (2 ** N);
      end if;
    end loop;
    return SUM;
  end INTVAL;
end TRUTH4x5;

```

Descriptions, CASE statement

- One multiplexer for each output

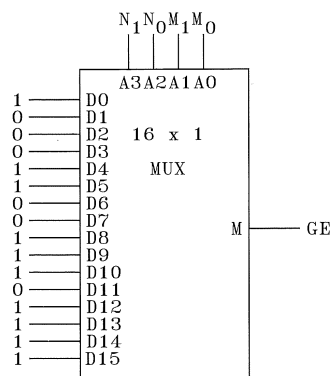

```

architecture MUX of COM is
begin
  process(N1,N0,M1,M0)
  begin
    case N1&N0&M1&M0 is
      when "0000" => GE <= '1' after D; LE <= '1' after D;
        E <= '1' after D; G <= '0' after D; L <= '0' after D;
      when "0001" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "0010" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "0011" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "0100" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "0101" => GE <= '1' after D; LE <= '1' after D;
        E <= '1' after D; G <= '0' after D; L <= '0' after D;
      when "0110" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "0111" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "1000" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "1001" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "1010" => GE <= '1' after D; LE <= '1' after D;
        E <= '1' after D; G <= '0' after D; L <= '0' after D;
      when "1011" => GE <= '0' after D; LE <= '1' after D;
        E <= '0' after D; G <= '0' after D; L <= '1' after D;
      when "1100" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "1101" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "1110" => GE <= '1' after D; LE <= '0' after D;
        E <= '0' after D; G <= '1' after D; L <= '0' after D;
      when "1111" => GE <= '1' after D; LE <= '1' after D;
        E <= '1' after D; G <= '0' after D; L <= '0' after D;
    end case;
  end process;
end MUX;

```

Descriptions, improved CASE


- Remove one variable in the selection of the case statement
- Use the removed variable as output value or its inverse
- More variables can be removed
 - Increase logic in front of multiplexer

architecture MUX3 of COM is

```
begin
process (N1, N0, M1, M0)
begin
case N1&N0&M1 is
when "000" => GE <= not M0 after D; LE <= '1' after D;
  E <= not M0 after D; G <= '0' after D; L <= M0 after D;
when "001" => GE <= '0' after D; LE <= '1' after D;
  E <= '0' after D; G <= '0' after D; L <= '1' after D;
when "010" => GE <= '1' after D; LE <= M0 after D;
  E <= M0 after D; G <= not M0 after D; L <= '0' after D;
when "011" => GE <= '0' after D; LE <= '1' after D;
  E <= '0' after D; G <= '0' after D; L <= '1' after D;
when "100" => GE <= '1' after D; LE <= '0' after D;
  E <= '0' after D; G <= '1' after D; L <= '0' after D;
when "101" => GE <= not M0 after D; LE <= '1' after D;
  E <= not M0 after D; G <= '0' after D; L <= M0 after D;
when "110" => GE <= '1' after D; LE <= '0' after D;
  E <= '0' after D; G <= '1' after D; L <= '0' after D;
when "111" => GE <= '1' after D; LE <= M0 after D;
  E <= M0 after D; G <= not M0 after D; L <= '0' after D;
end case;
end process;
end MUX3;
```

Hardware, improved Case statement

 - One mux plus inverter
- Every output have its own multiplexer (same as for non-improved case statement)



Partitioning

- Rewrite expressions, sharing common subexpression
 - $E = GE \text{ AND } LE$
 - $G = GE \text{ AND NOT } LE$
 - $L = LE \text{ AND NOT } GE$
- That is, two expressions followed by simple generation of E, G, and L
- Designer makes logic synthesis instead of tool
 - Synthesis tool may still modify description

Two-level logic

- Many different choices
- Can be described as structure

```
architecture POSDF of COM is
  signal Z1,Z0: BIT;
begin
  Z1 <= (not N0 or M1 or M0) and (not N1 or M1) and
        (not N1 or not N0 or M0);
  Z0 <= (N1 or N0 or not M0) and (N1 or not M1) and
        (N0 or not M1 or not M0);
  LE <= Z1 after D;
  GE <= Z0 after D;
  E <= Z1 and Z0 after D;
  G <= Z0 and not Z1 after D;
  L <= Z1 and not Z0 after D;
end POSDF;
```


Structural description

```
architecture TWO_LEVEL_OR_AND of COM is
  signal Z10,Z11,Z12,Z00,Z01,Z02: BIT;
  signal N0BAR,N1BAR,M0BAR,M1BAR: BIT;
  signal Z0,Z1,Z0NOT,Z1NOT: BIT;
  component NOT2G
    generic (D: TIME);
    port (I: in BIT; O: out BIT);
  end component;
  for all: NOT2G use entity NOT2(BEHAVIOR);
  component AND2G
    generic (D: TIME);
    port (I1, I2: in BIT; O: out BIT);
  end component;
  for all: AND2G use entity AND2(BEHAVIOR);
  component AND3G
    generic (D: TIME);
    port (I1,I2,I3: in BIT; O: out BIT);
  end component;
  for all: AND3G use entity AND3(BEHAVIOR);
  component OR2G
    generic (D: TIME);
    port (I1,I2: in BIT; O: out BIT);
  end component;
  for all: OR2G use entity OR2(BEHAVIOR);
  component OR3G
    generic (D: TIME);
    port (I1,I2,I3: in BIT; O: out BIT);
  end component;
  for all: OR3G use entity OR3(BEHAVIOR);
  component WIREG
    port (I: in BIT; O: out BIT);
  end component;
  for all: WIREG use entity WIRE(BEHAVIOR);


begin
  C1: NOT2G
    generic map (2 ns)
    port map (N0, N0BAR);
  C2: NOT2G
    generic map (2 ns)
    port map (N1, N1BAR);
  C3: NOT2G
    generic map (2 ns)
    port map (M0, M0BAR);
  C4: NOT2G
    generic map (2 ns)
    port map (M1, M1BAR);
  C5: OR3G
    generic map (2 ns)
    port map (N0BAR, M1, M0, Z10);
  C6: OR2G
    generic map (2 ns)
    port map (N1BAR, M1, Z11);
  C7: OR3G
    generic map (2 ns)
    port map (N1BAR, N0BAR, M0, Z12);
  C8: AND3G
    generic map (2 ns)
    port map (Z10, Z11, Z12, Z1);
  C9: OR3G
    generic map (2 ns)
    port map (N1, N0, M0BAR, Z00);
  C10:OR2G
    generic map (2 ns)
    port map (N1, M1BAR, Z01);
  C11:OR3G
    generic map (2 ns)
    port map (N0, M1BAR, M0BAR, Z02);
  C12:AND3G
    generic map (2 ns)
    port map (Z00, Z01, Z02, Z0);
  C13:NOT2G
    generic map (2 ns)
    port map (Z1, Z1NOT);
  C14:NOT2G
    generic map (2 ns)
    port map (Z0, Z0NOT);
  C15:AND2G
    generic map (2 ns)
    port map (Z0, Z1, E);
  C16:AND2G
    generic map (2 ns)
    port map (Z0, Z1NOT, G);
  C17:AND2G
    generic map (2 ns)
    port map (Z1, Z0NOT, L);
  C18:WIREG
    port map (Z0, GE);
  C19: WIREG
    port map (Z1, LE);
end TWO_LEVEL_OR_AND;
```

Finite state machines (FSM)

 - Example: serial/parallel converter
 - A indicates start of data
 - Output Z only during one clock cycle


 
```
entity STOP is
  port (R, A, D, CLK: in BIT;
        Z: out BIT_VECTOR(3 downto 0);
        DONE: out BIT);
end STOP;
```



FSM design, cont.


- First: Select type of state machine (Moore, Mealy)
 - Moore machine have stable output after a few gate delays
 - Moore machine can not produce output dependent on current input values
 - Moore machine may require more states than Mealy machines
 - Mealy machine may sometimes be required due to direct respons from FSM on input signal change

FSM Design, cont.

- Second: Create a state diagram. Good start is reset-state S0.
 - S1: First data on D, Done=0, Z unspecified
 - S2: Second data on D, Done =0, Z unspecified
 - S3: Third data on D, Done = 0, Z unspecified
 - S4: Fourth data on D, Done = 0, Z unspecified
 - S5: Output on Z, Done= 1
 - In S5 can A also be 1 (indicating new data)
 - Next clock cycle must take care data, i.e., use S1 without passing through S0

FSM state diagram

 - Some tools can translate state diagram automatically to VHDL (e.g., HDL Designer)



Alternate description

- Transition list
 - Textual description of the FSM
 - Useful for large state diagrams
 - Graphs become hard to understand when number of states increase
 - Possible to cope with complexity by use of hierarchy

Current State	Transition Expression	Next State	Data Transfers	Output
S0	R+A	S0	None	DONE=0, Z unspecified
S0	R & A	S1		
S1	R	S2	Store bit 1	DONE=0, Z unspecified
S1	R	S0		
...
S5	R & A	S1	None	DONE=1, Z=parallel data out
S5	R + A	S0		

FSM description in VHDL

```
architecture FSM_RTL of STOP is
  type STATE_TYPE is (S0, S1, S2, S3, S4, S5);
  signal STATE: STATE_TYPE;
  signal SHIFT_REG: BIT_VECTOR (3 downto 0);
begin
  STATE: process (CLK)
  begin
    if CLK='1' then
      case STATE is
        when S0 =>
          -- Data Section
          -- Control Section
          if R='1' or A='0' then
            STATE <= S0;
          elsif R='0' and A='1' then
            STATE <= S1;
          end if;
        when S1 =>
          -- Data Section
          SHIFT_REG <= D & SHIFT_REG(3 downto 1);
          -- Control Section
          if R='0' then
            STATE <= S2;
          elsif R='1' then
            STATE <= S0;
          end if;
      end case;
    end if;
  end process;
```

```
when S2 =>
  -- Data Section
  SHIFT_REG <= D & SHIFT_REG(3 downto 1);
  -- Control Section
  if R='0' then
    STATE <= S3;
  elsif R='1' then
    STATE <= S0;
  end if;
when S3 =>
  -- Data Section
  -- Shift in the third bit
  SHIFT_REG <= D & SHIFT_REG(3 downto 1);
  -- Control Section
  if R='0' then
    STATE <= S4;
  elsif R='1' then
    STATE <= S0;
  end if;
when S4 =>
  -- Data Section
  -- Shift in the fourth bit
  SHIFT_REG <= D & SHIFT_REG(3 downto 1);
  -- Control Section
  if R='0' then
    STATE <= S5;
  elsif R='1' then
    STATE <= S0;
  end if;
end if;
```

```
when S5 =>
  -- Data Section
  -- Control Section
  if R='0' and A='1' then
    STATE <= S1;
  elsif R='1' or A='0' then
    STATE <= S0;
  end if;
end case;
end if;
end process STATE;

OUTPUT: process (STATE)
begin
  case STATE is
    when S0 to S4 =>
      DONE <= '0';
    when S5 =>
      DONE <= '1';
      Z <= SHIFT_REG;
    end case;
  end process OUTPUT;
end FSM_RTL;
```

State machine partitioning

- State machines partitioned into multiple processes
 - Updating (clocked), i.e., the state register
 - Next state calculation
 - Output calculation
- May find different combinations of these
 - Single process
 - Two processes (nextstate + output, state update)
 - Three processes (nextstate, output, state update)
- Multiple processes to avoid creating Mealy instead of Moore machine

State assignment

- States are not coded in VHDL
 - Use enumeration
 - Allows synthesis tools do a better work
 - Powerful computer algorithms usually find better state assignment
 - Possible to control state minimisation and assignment in synthesis tool
 - E.g. one-hot encoding may be more suitable in some cases

Alternative description: table based

- Small statemachine, one input X and one output Z
- Code the state table as an array with nextstate and output

```

entity TWO_CONSECUTIVE is
  port(CLK,R,X: in BIT; Z: out BIT);
end TWO_CONSECUTIVE;
--
architecture FSM of TWO_CONSECUTIVE is
  type STATE is (S0,S1,S2);
  signal FSM_STATE: STATE := S0;
  type TRANSITION is record
    OUTPUT: BIT;
    NEXT_STATE: STATE;
  end record;
  type TRANSITION_MATRIX is array(STATE,BIT) of TRANSITION;
  constant STATE_TRANS: TRANSITION_MATRIX :=
    (S0 => ('0' => ('0',S1), '1' => ('0',S2)),
     S1 => ('0' => ('1',S1), '1' => ('0',S2)),
     S2 => ('0' => ('0',S1), '1' => ('1',S2)));
begin
  process(R,X,CLK,FSM_STATE)
  begin
    if R = '0' then -- Reset
      FSM_STATE <= S0;
    elsif CLK'EVENT and CLK = '1' then -- Clock event
      FSM_STATE <= STATE_TRANS(FSM_STATE,X).NEXT_STATE;
    end if;
    if FSM_STATE'EVENT or X'EVENT then -- Output Function
      Z <= STATE_TRANS(FSM_STATE,X).OUTPUT;
    end if;
  end process;
end FSM;

```

