

Solution to lecture 5 exercises

5-100

The step-down converter in exercise 22-13 is based on a MOSFET switch according to Figure 1. The switching response is defined in 22-13 related to a wave shape as shown in Figure 2.

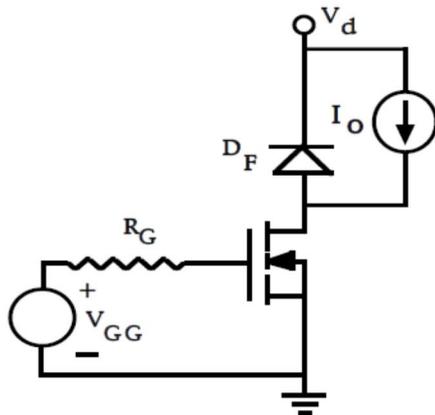


Figure 1

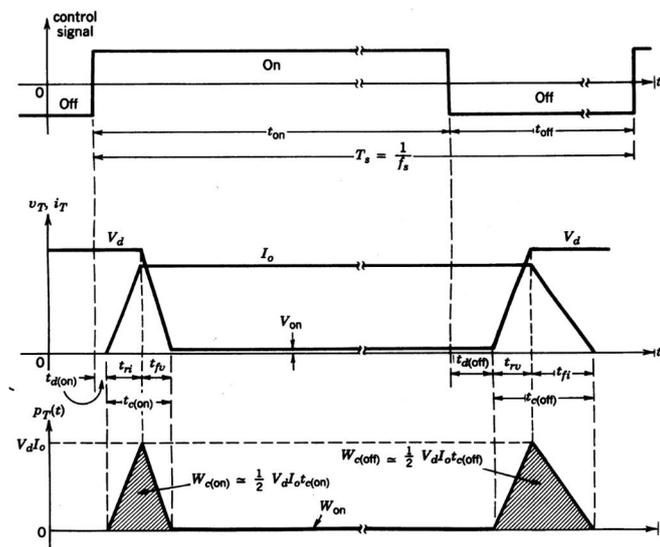


Figure 2

Tomas Jonsson

The task is to determine the gate resistor which gives the turn-on dV/dt according to the given data. The dynamics of the MOSFET can during turn-on be modelled as:

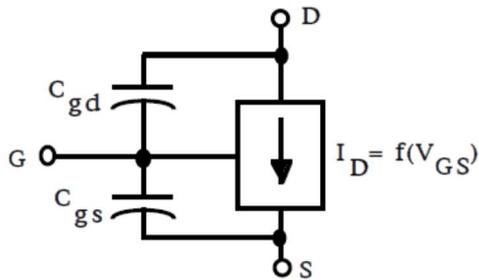


Figure 3

During turn-on the dV/dt between of the drain voltage will discharge the gate-drain capacitance C_{gd} giving a current defined as:

$$I_{gd} = C_{gd} \frac{dV_d}{dt} = 120pF \frac{100}{200ns} = 60mA$$

Specifically related to the Miller plateau where the gate-source voltage is constant during the collapse of the drain voltage, all current from the gate of the MOSFET will go through the gate-drain capacitance according to Figure 4.

- Equivalent circuit during t_{fv1} .

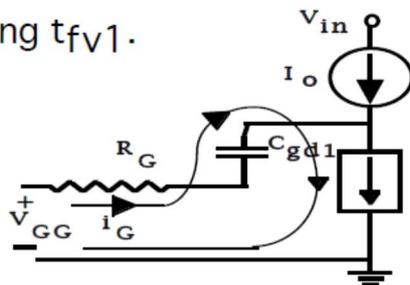


Figure 4

Consequently the gate current is defined by the gate drain capacitance and the dV/dt .

$$I_g = I_{gd}.$$

Related to the gate drive the following equation applies for the gate current when the gate-source voltage is defined by the Miller plateau voltage, V_{GP} .

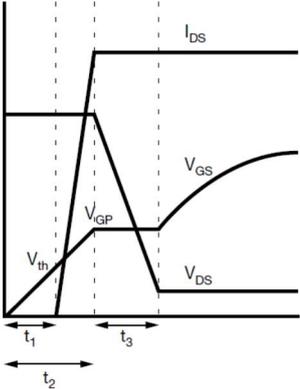


Figure 5

$$R_G = \frac{V_{GG} - V_{GP}}{I_g} = \frac{10 - 4}{60\text{mA}} = 100\text{ohm}$$