

# TSTE19 Power Electronics

Lecture 2

Tomas Jonsson

ICS/ISY

# Lecture 2, outline

- Diode device characteristics
  - Semiconductor theory
  - Data sheet info
- Rectifiers
  - Single phase
- Characteristics
  - Total Harmonic Distortion (THD)
  - Crest Factor
  - Power Factor
- Exercises: 5-1, 5-2, 5-3, 5-4, 5-7, 5-14

# Lecture 2



Diode device characteristics

Semiconductor theory

Data sheet info


# • Diodes

- Characteristic

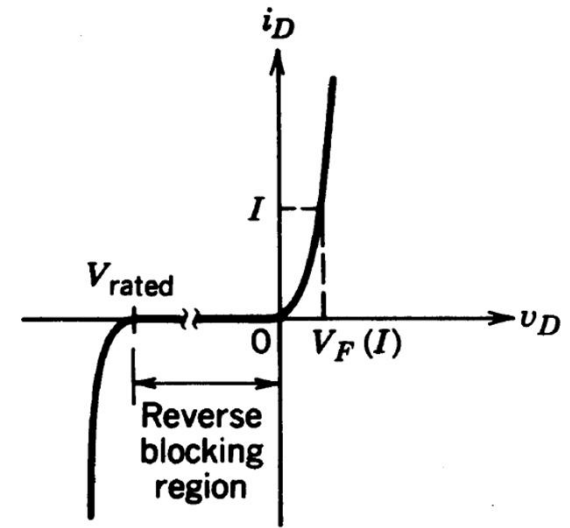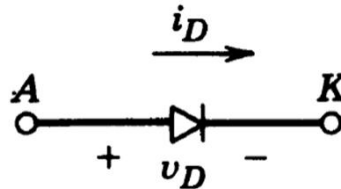




- Idealized characteristic

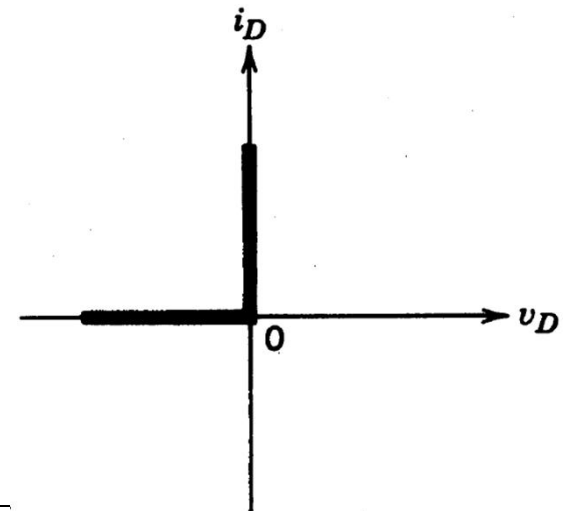- Neglect forward voltage drop
- Neglect breakdown voltage
- Turns off only if current drops to 0



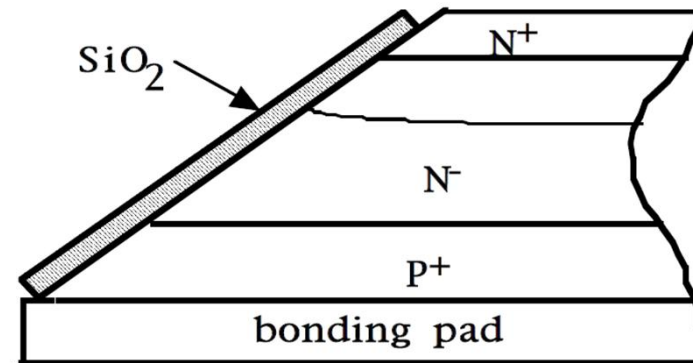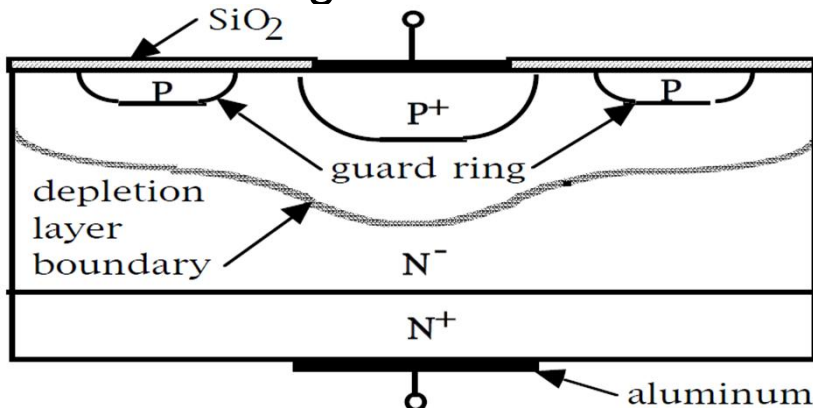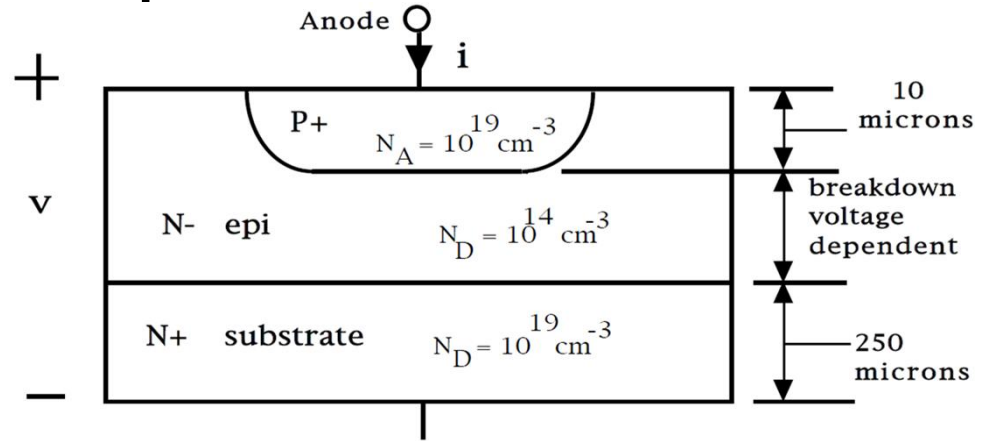
# • Diodes, physical implementation

- P-N junction
- Cross-section area for kA diodes are several square cm
- Additional structures to increase breakdown voltage




# On-state: Carrier injection

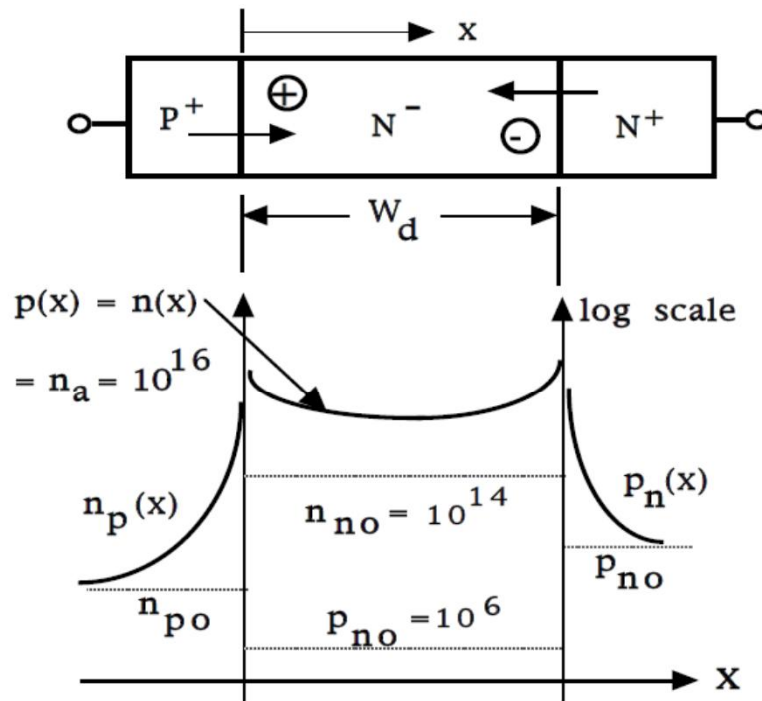

- Forward bias injects holes into drift region from P<sup>+</sup> layer. Electrons attracted into drift region from N<sup>+</sup> layer. So-called double injection.
- If  $W_d \leq$  high level diffusion length  $L_a$ , carrier distributions quite flat with  $p(x) \approx n(x) \approx n_a$ .
- For  $n_a \gg$  drift region doping  $N_d$ , the resistance of the drift region will be quite small. So-called conductivity modulation.
- On-state losses greatly reduced below those estimated on basis of drift region low-level ( $N_d$ ) ohmic conductivity.

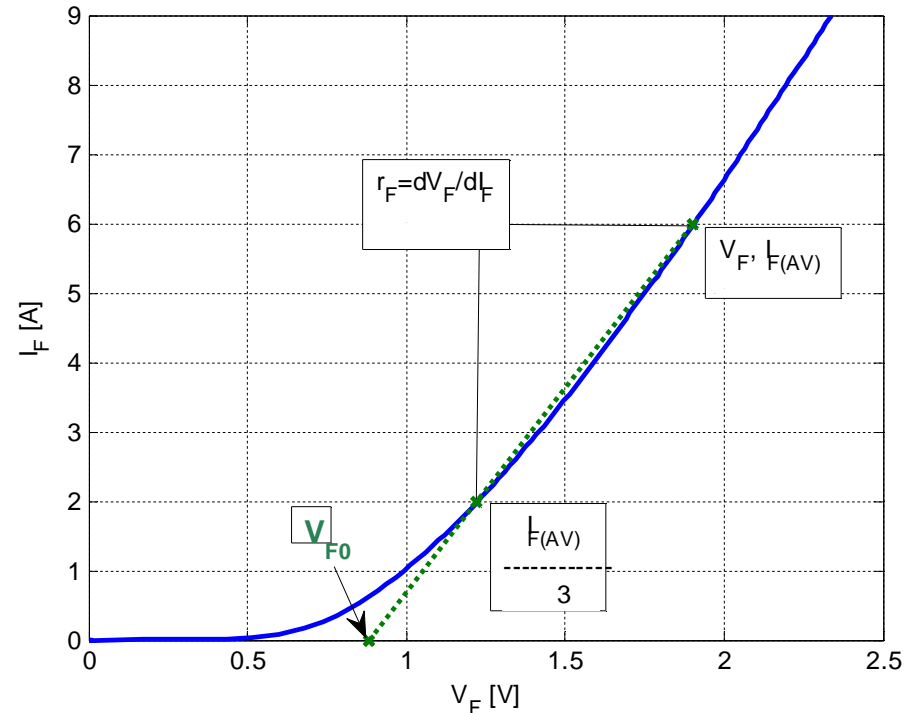
# On-state diode data

- Data sheet
- $I_{F(AV)}$  = Average forward current
- $V_F$  = Voltage at  $I_{F(AV)}$
- 1<sup>st</sup> order model
- On-state characteristics simplified to a straight line through  $I_{F(AV)}$  and  $I_{F(AV)}/3$
- $\Rightarrow V_{F0}$  and  $r_F$
- $I_{FRM}$  = repetitive peak forward current
- $I_{FSM}$  = non-repetitive (surge) forward current


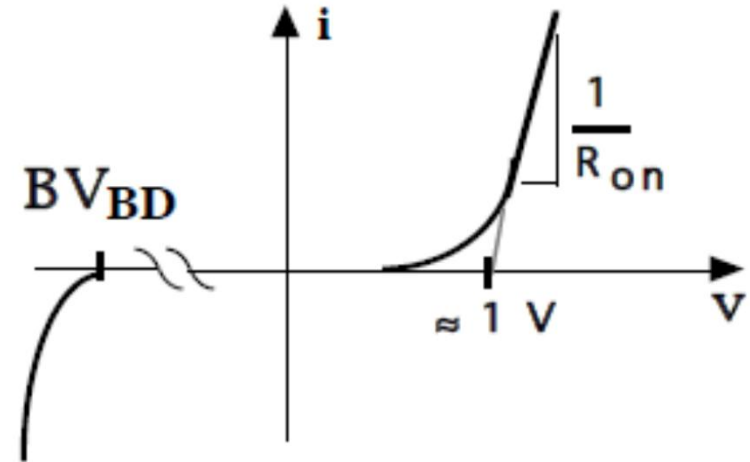
# Off-state diode data

- $V_{RRM}$  = repetitive peak reverse voltage
- $I_R$  = reverse leakage current
- $I_{RRM}$  = repetitive peak reverse current






# Diode behaviour during turn-on

**Fig. 5.13** Characteristic parameters of the turn-on behavior of power diodes

- Over-voltage during diode turn-on
- = Forward recovery
- Initial low carrier concentration gives high voltage
- $V_{FRM}$  = Forward recovery voltage

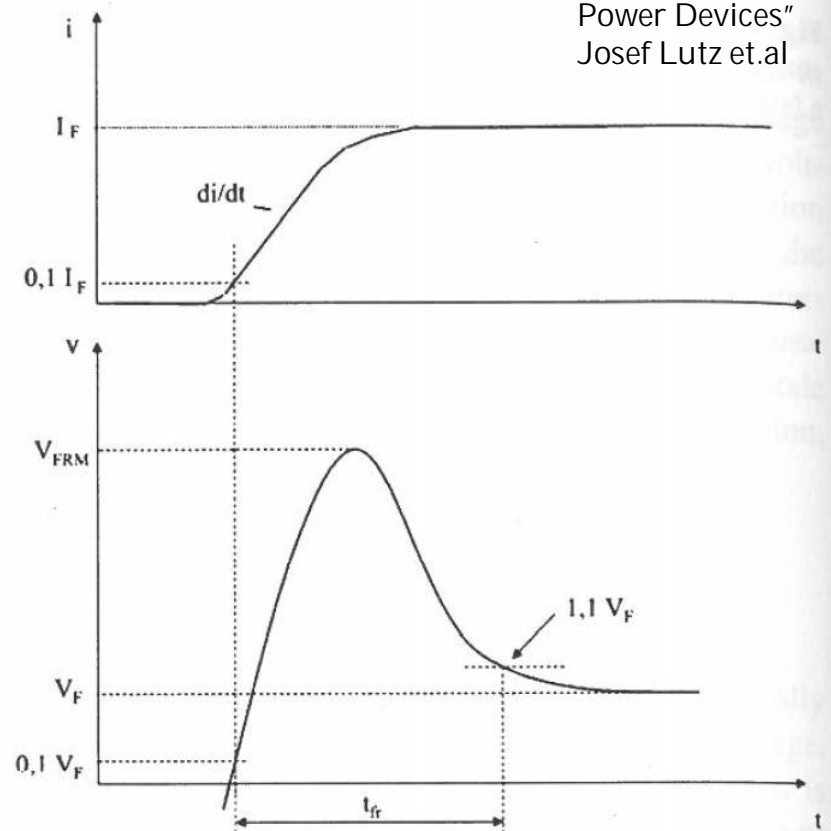"Semiconductor Power Devices"  
Josef Lutz et.al



# Diode behaviour during turn-off

- High carrier concentration in the diode at turn-off
- Carriers need to be removed for the diode to block voltage
- Removal of carriers = negative current
- Carriers removed by negative voltage
- = Reverse recovery
- $Q_{rr}$  = Stored charge extracted
- $I_{rr}$  = Peak reverse recovery current
- $t_{rr}$  = Time until 25% of  $I_{rr}$ .

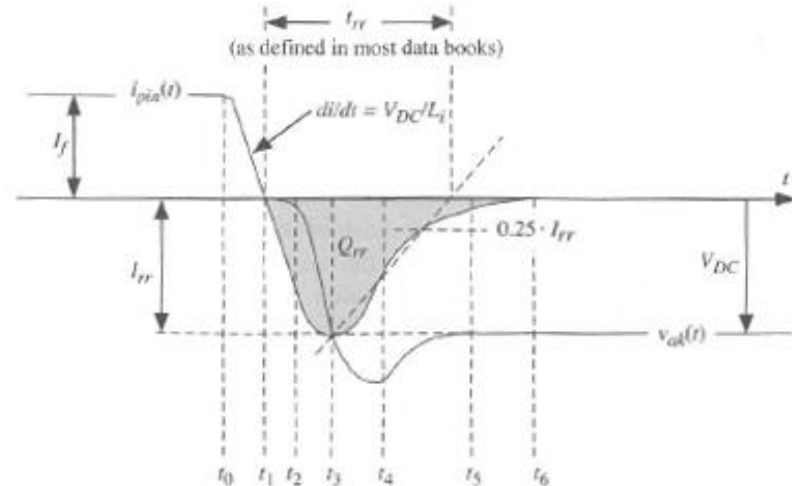


Fig. 3.8 Switching behavior of a pin-diode in the test circuit of Figure 3.7.

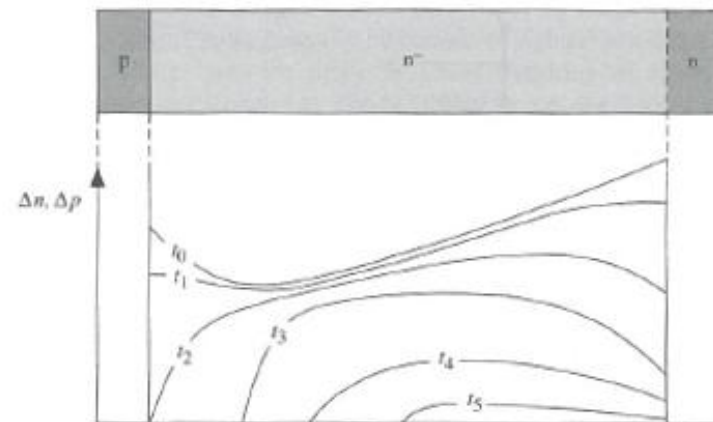


Fig. 3.9 Curves for the excess carrier concentration in the pin-diode, at the instants marked in Figure 3.8.

# Turn-off, reverse recovery factors

- $I_{rr} = \frac{di_R}{dt} t_{rr} = \frac{di_R}{dt} \frac{t_{rr}}{S + 1}$ ; Defined on switching waveform diagram
- $Q_{rr} = \frac{I_{rr} t_{rr}}{2} = \frac{di_R}{dt} \frac{t_{rr}^2}{2(S + 1)}$ ; Defined on waveform diagram
- Inverting  $Q_{rr}$  equation to solve for  $t_{rr}$  yields

$$t_{rr} = \sqrt{\frac{2Q_{rr}(S+1)}{\frac{di_R}{dt}}} \text{ and } I_{rr} = \sqrt{\frac{2Q_{rr}\frac{di_R}{dt}}{(S + 1)}}$$

- If stored charge removed mostly by sweep-out  $Q_{rr} \approx Q_F \approx I_F \tau$
- Using this in eqs. for  $I_{rr}$  and  $t_{rr}$  and assuming  $S + 1 \approx 1$  gives

$$t_{rr} = \sqrt{\frac{2 I_F \tau}{\frac{di_R}{dt}}} \text{ and}$$

$$I_{rr} = \sqrt{2 I_F \tau \frac{di_R}{dt}}$$



# BYW29E-200

Ultrafast power diode


Rev. 5 — 20 March 2012

Product data sheet

- [Electrical data](#)
- [Thermal data](#)
- [Mechanical data](#)
- [BYW29E-200\\_eng\\_tds.pdf](#)
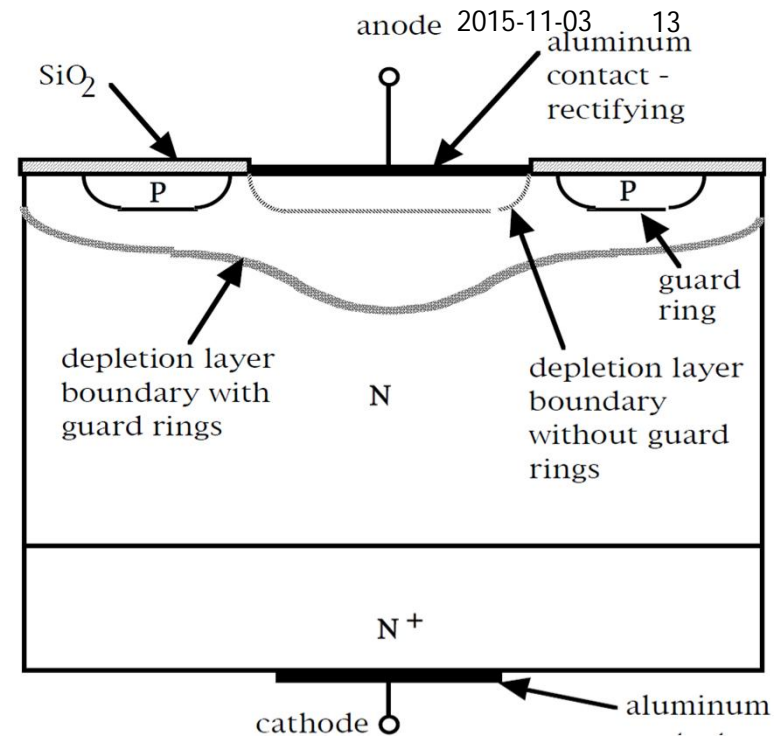
# • Diode types

- Schottky
  - Forward voltage  $\sim 0.3$  V
  - Blocking voltage range 50 - 100V
- Fast-recovery
  - $t_{rr}$  small ( $<$  few microseconds for diodes for 100:s Volt blocking voltage and 100:s Ampere current rating)
- Line-frequency
  - Small forward voltage, little larger  $t_{rr}$ , large blocking voltage and current rating



# Lecture 2

Rectifiers



Single phase

Characteristics

Total Harmonic Distortion (THD), Crest Factor, Power Factor

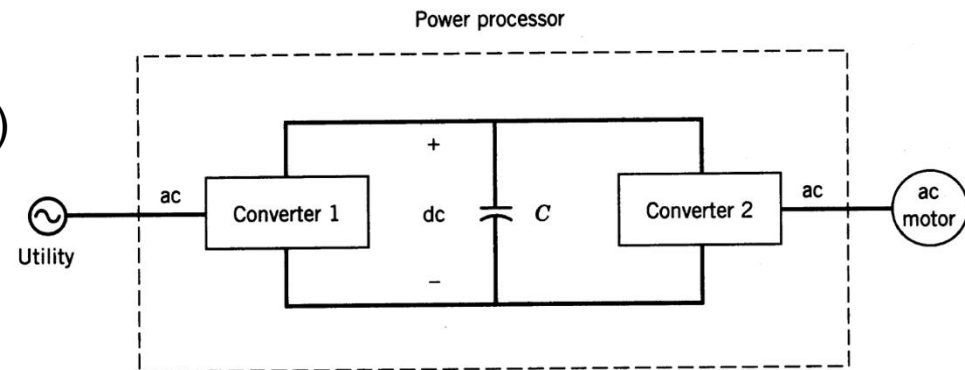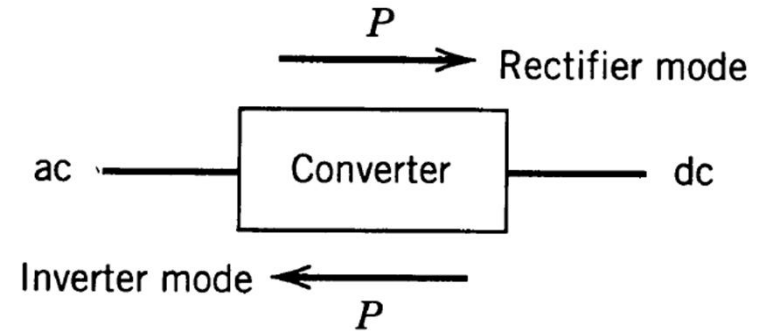
# Rectifiers vs inverters

- Principle
  - AC → DC: rectifier {likriktare}
  - DC → AC: inverter {växelriktare}
- Output may be controlled or uncontrolled
  - Uncontrolled e.g. AC-DC diode rectifier
- AC frequency may be fixed or varying
  - Motor control: varying
  - Line frequency 50 Hz (Europe)


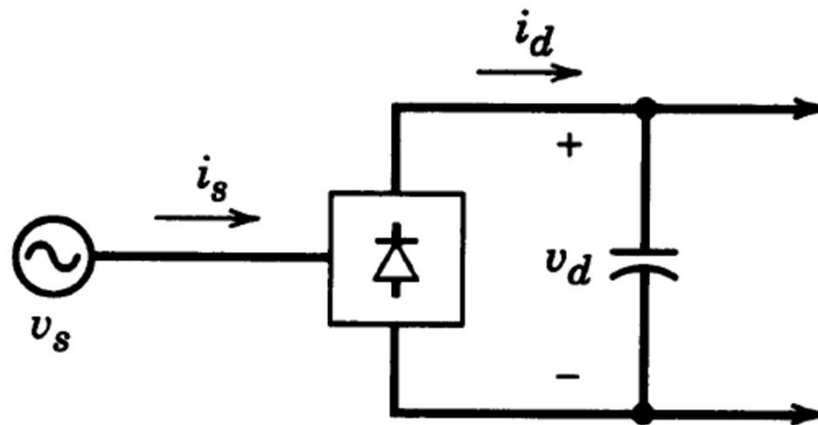
# Line frequency diode rectifier



- Line frequency AC  $\rightarrow$  uncontrolled DC
- Limit DC-side ripple
  - C added at output
- Assume ideal diode






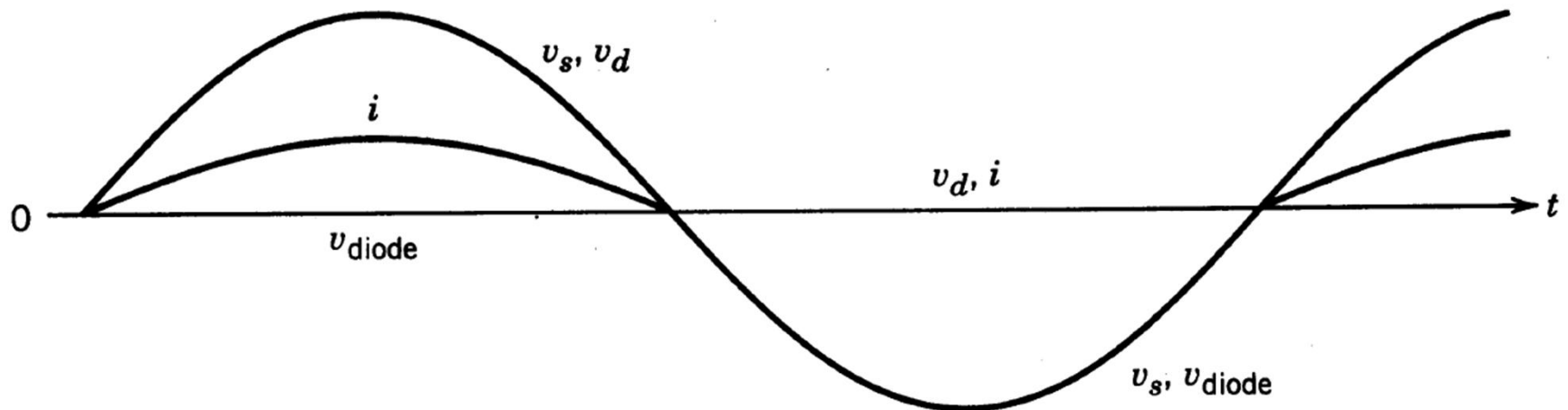
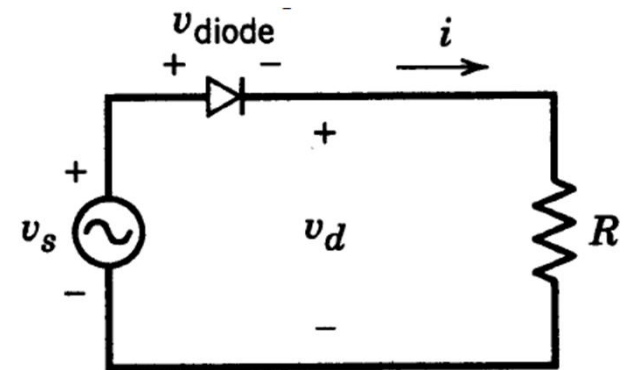
# Inductive load

- Big ripple on  $i$  and  $v_d$
- Half-wave rectifier



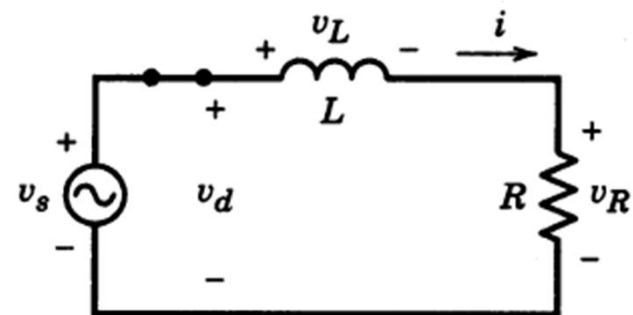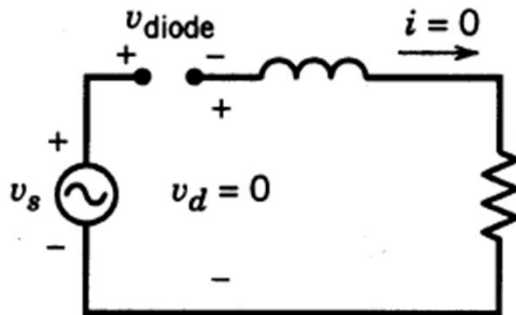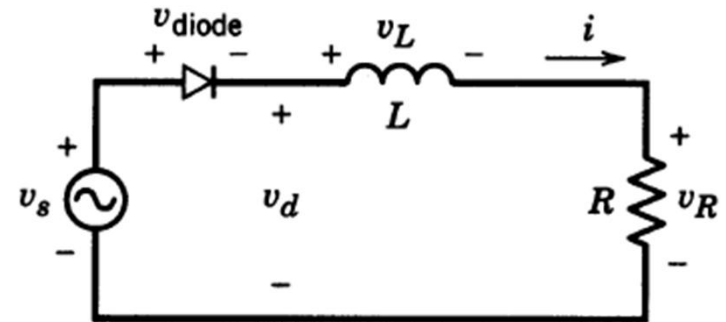
# Inductive load

- Two modes
  - Current = 0
  - Current  $\neq 0$
- Two schematics, diode on and off
- Diode off  $\Rightarrow v_d = 0$



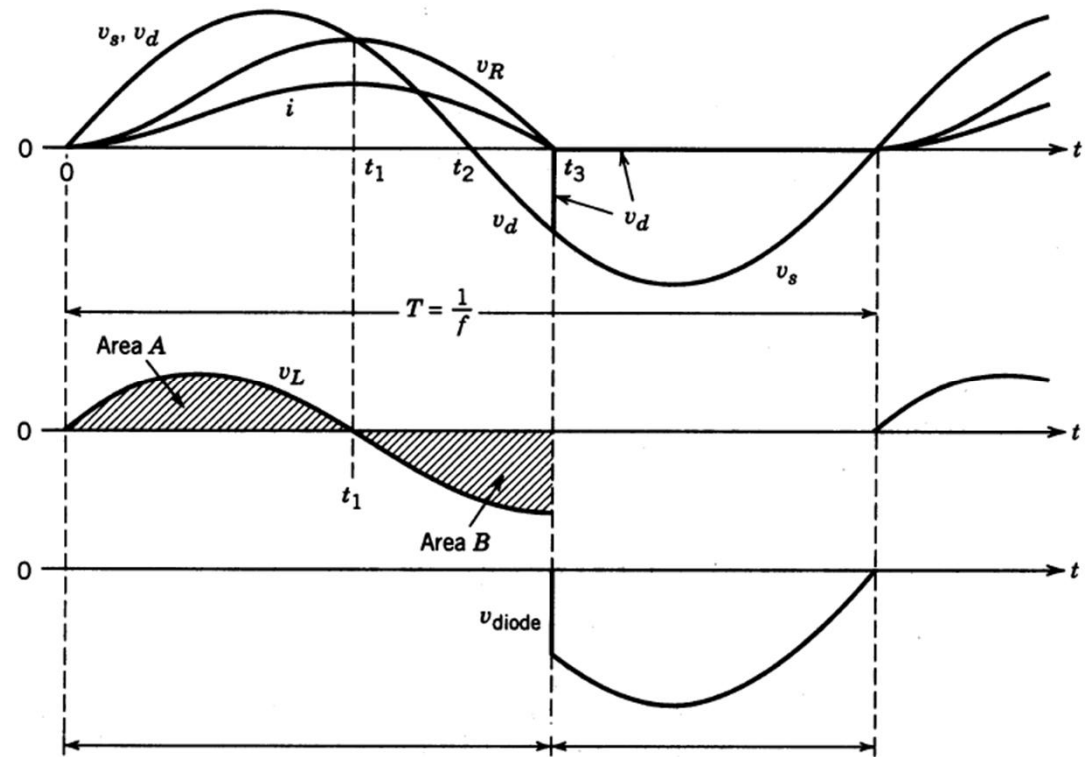
# Inductive load, cont

- From  $t_0$  to  $t_1$ 
  - Inductor is storing energy
- At  $t_1$ :  $v_d = v_R$ 
  - Inductor starts to output energy
- At  $t_2$ : negative input voltage, but still non-zero current
- At  $t_3$ : zero current, diode switch off
- Current even when  $v_s$  negative



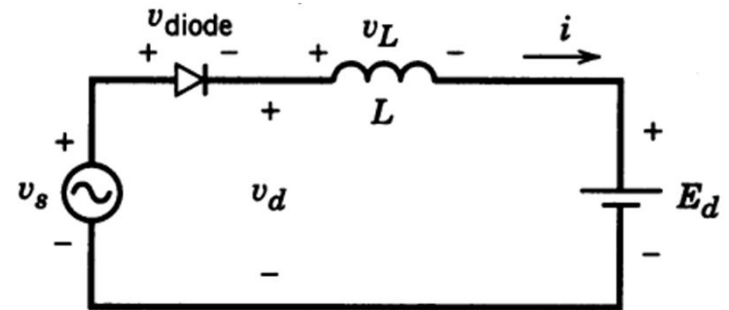
# Load with an internal dc voltage

- Similar to load and capacitance on DC output
- Diode turn on when  $v_s > E_d$ 
  - Store energy in L
- I maximum when  $v_s = E_d$  after  $v_s$  reached its maximum
  - Start energy extract from L after this




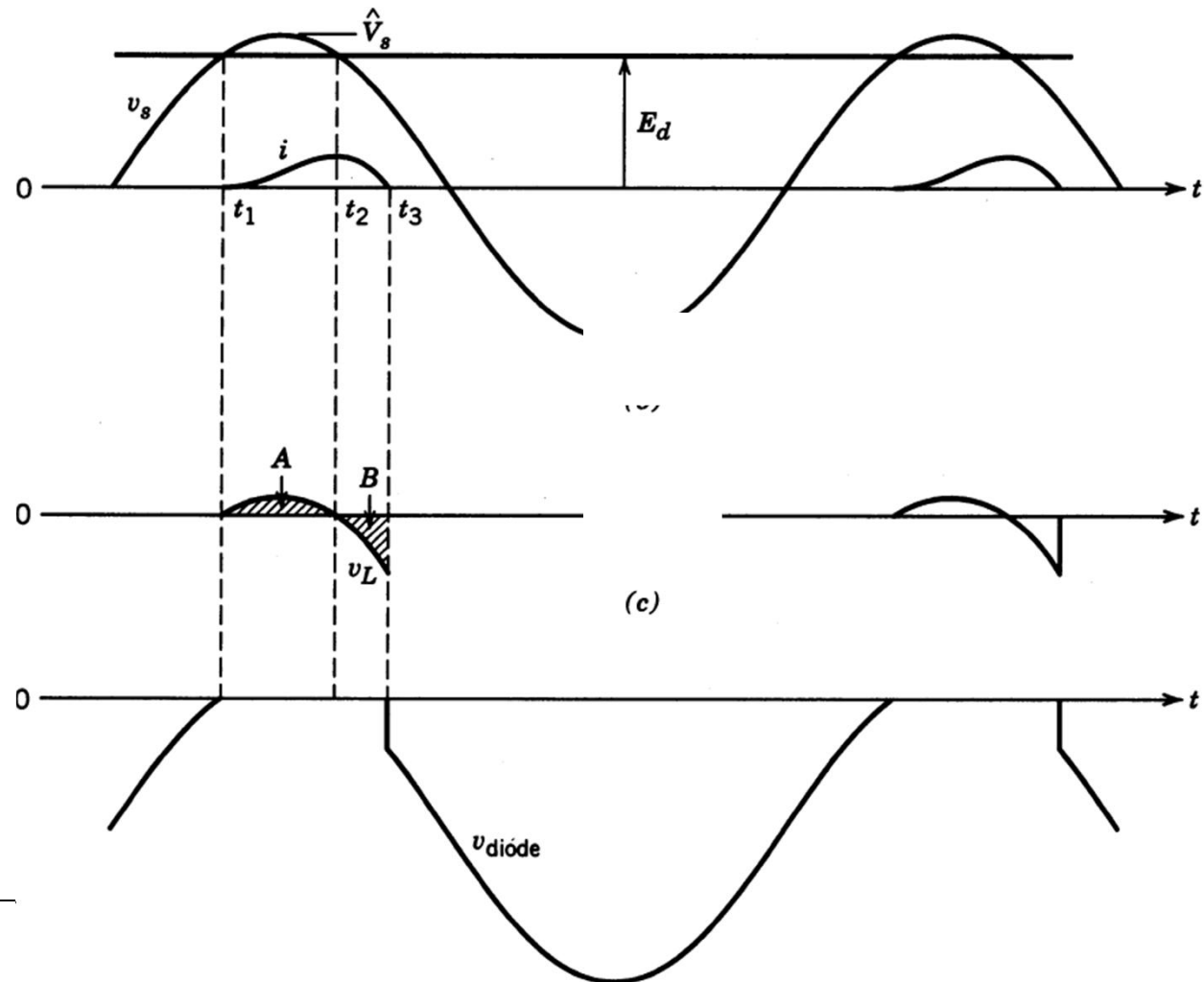
# • Load with internal dc voltage

- $A = B$  because steady state (repeated sequence)
- Input current very different from input voltage waveform



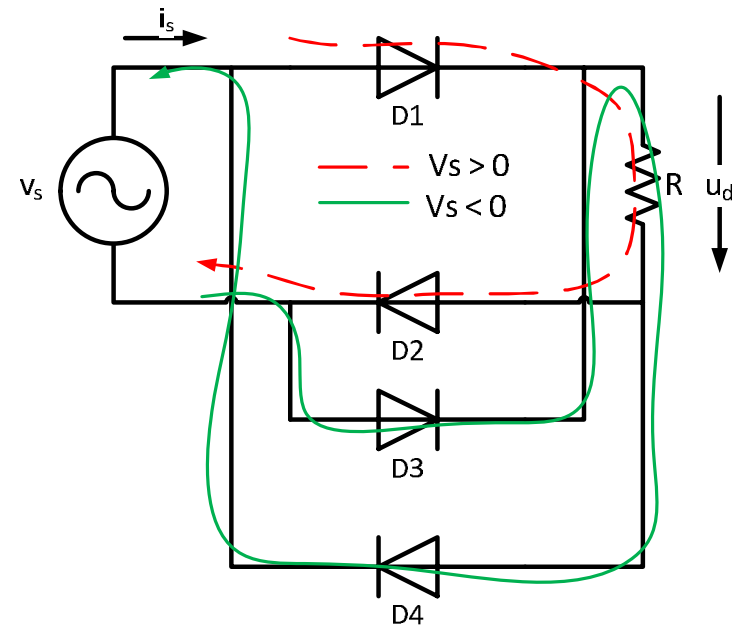
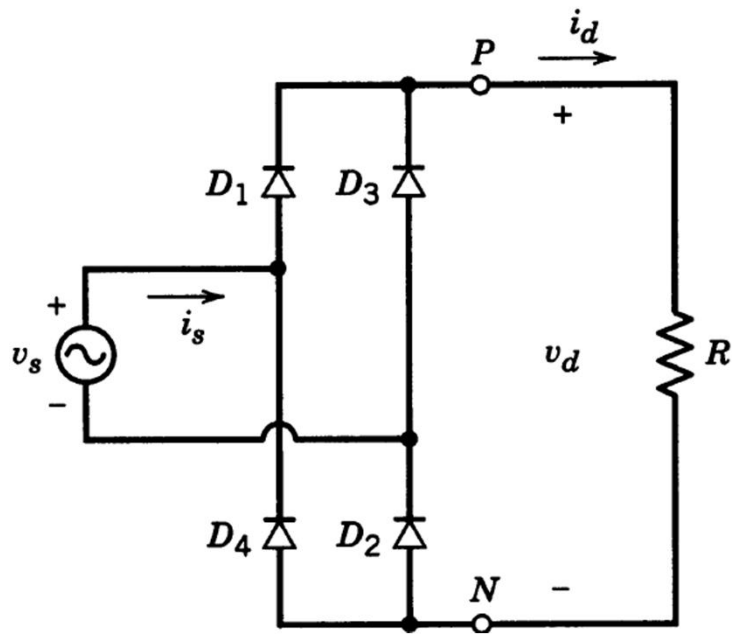
# • Single phase diode bridge rectifier

- Two separate circuits defined related to the polarity of  $v_s$




- Idealized circuit,  $L_s = 0$ , resistive load

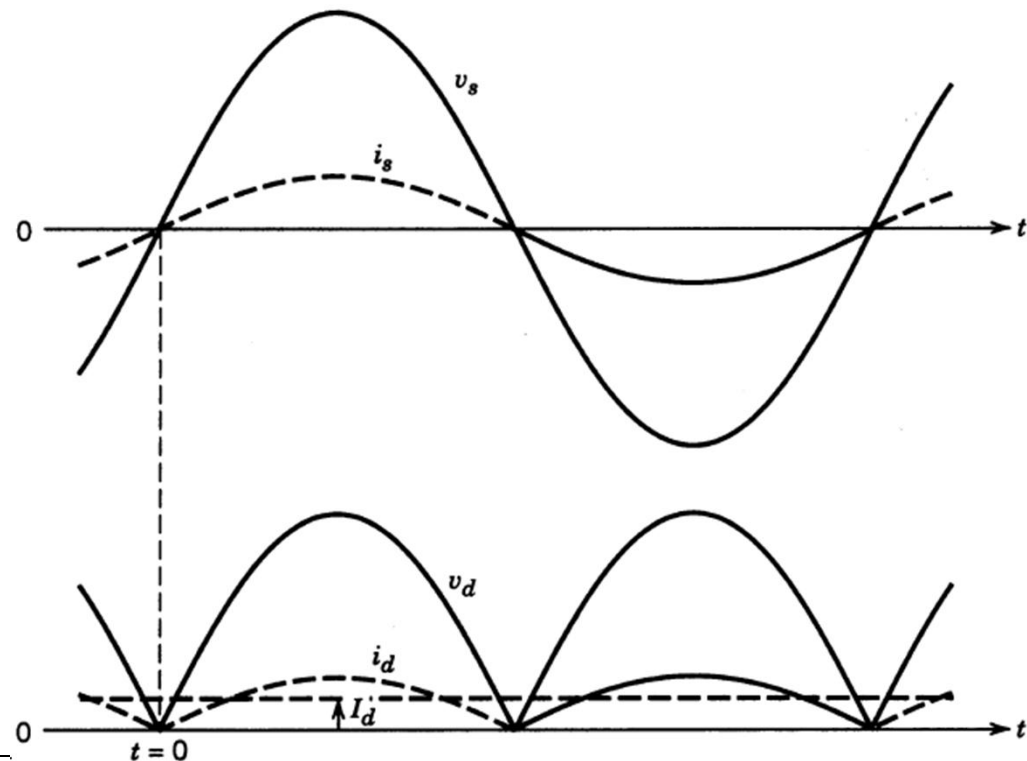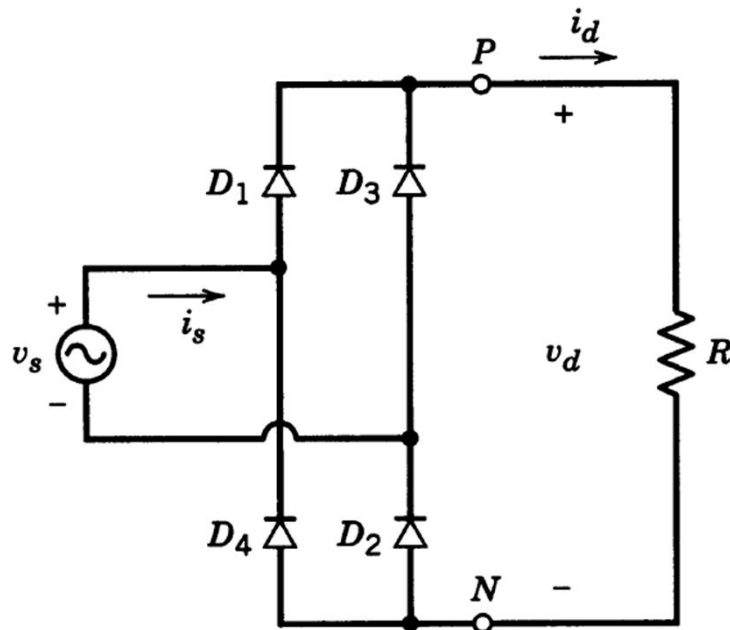- Used to model power factor corrected rectifier
- Note missing  $C_d$ .


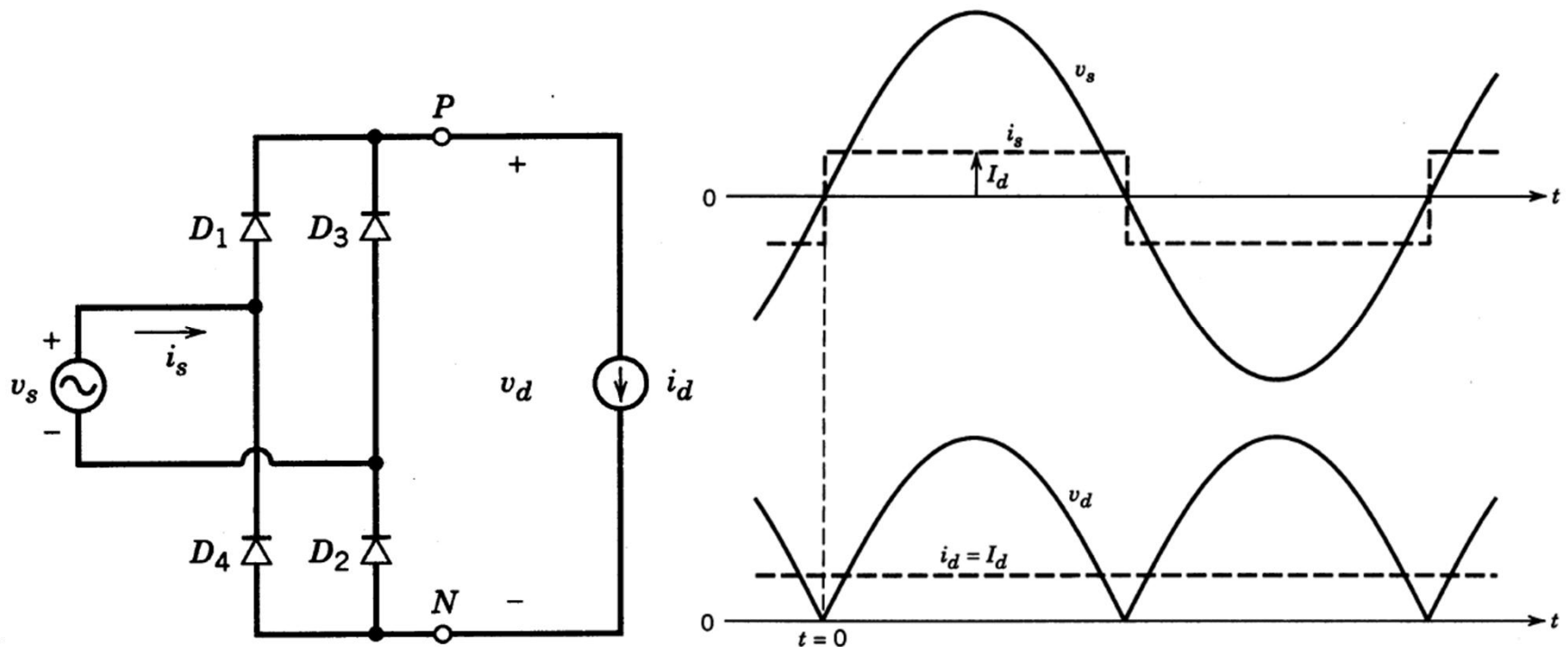
# • Idealized circuit, $L_s = 0$ , current load


- Simplified model of a big inductance in series on the dc-side
- Same  $v_d$  as resistive load




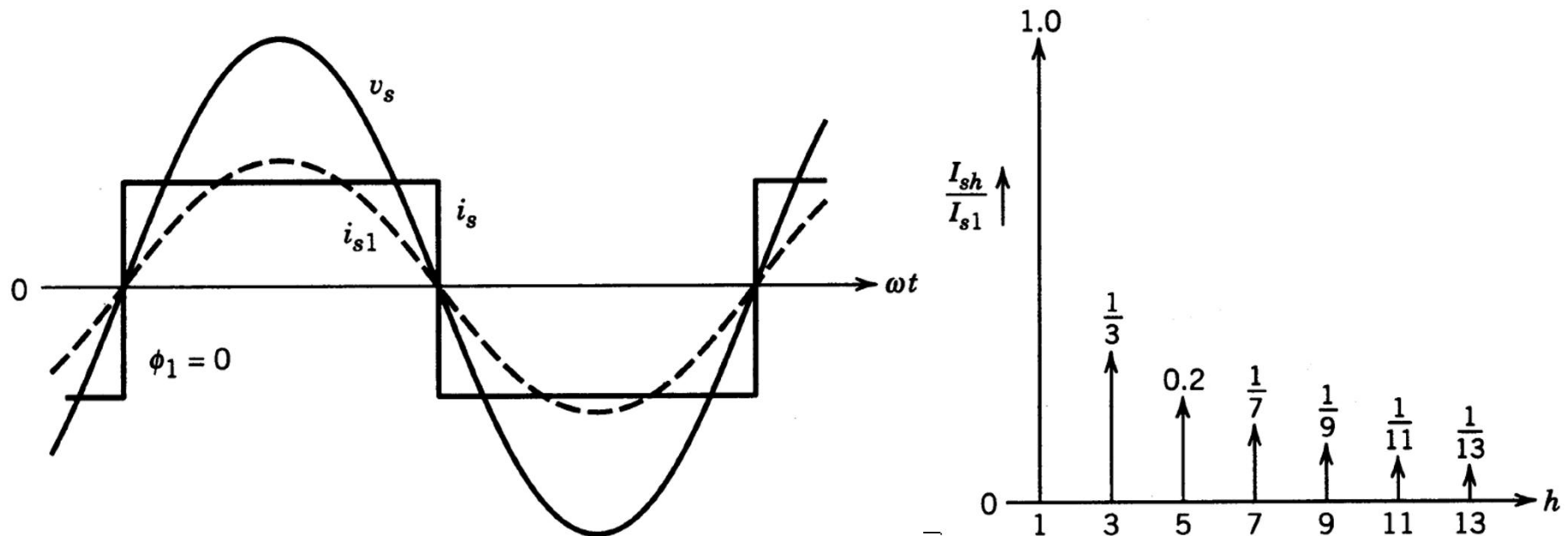
# • Idealized circuit, input current

- Input current is a square wave, not sinusoidal
- Fourier analysis gives additional harmonic components {övertoner}



# • Fourier analysis

- Non-sinusoidal repeated signal with angular frequency  $\omega$

$$f(t) = F_0 + \sum_{h=1}^{\infty} f_h(t) = \\ = \frac{1}{2} a_0 + \sum_{h=1}^{\infty} \{a_h \cos(h\omega t) + b_h \sin(h\omega t)\}$$

$$a_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \cos(h\omega t) d(\omega t) \quad h = 0, \dots, \infty$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(h\omega t) d(\omega t) \quad h = 1, \dots, \infty$$

# • Line current distortion

- Non-sinusoidal currents may give distortion on utility-supply voltage.
- Assume purely sinusoidal voltage at fundamental frequency {grundton}
- Input current is sum of a fundamental plus harmonics {övertoner}

- $$i_s(t) = i_{s1}(t) + \sum_{h \neq 1} i_{sh}(t)$$

- Distortion part is the harmonics (excluding fundamental). In RMS form

$$I_{dis} = \sqrt{\left( \sum_{h \neq 1} I_{sh}^2 \right)}$$

# • THD, Total Harmonic Distortion

- Distortion on a current waveform

$$\%THD_i = 100 \times \frac{I_{dis}}{I_{s1}} = 100 \times \sqrt{\sum_{h \neq 1} \left( \frac{I_{sh}}{I_{s1}} \right)^2}$$

- Energy in the harmonics compared to the fundamental
- THD can be larger than 1! (> 100%)

# • Crest factor

- Comparing peak value (instantaneous) and total rms current

$$\text{Crestfactor} = \frac{I_{s,peak}}{I_s}$$

- Peak value may define component ratings

# • Power factor for non-sinusoidal wave

- Assume fundamental only sinusoidal voltage with no harmonics
  - Harmonics do not contribute to power due to cross-product integrates to zero => only fundamental rms current used

$$P = V_S I_{S1} \cos\phi$$

- Apparent power
  - Include all harmonics

$$S = V_S I_S$$

- Power factor

$$PF = \frac{P}{S} = \frac{V_S I_{S1} \cos\phi_1}{V_S I_S} = \frac{I_{S1}}{I_S} \cos\phi_1$$

# • Displacement Power Factor

- Equals the power factor in case of sinusoidal voltage and current (angle is between fundamental voltage and current)

$$DPF = \cos\phi_1$$

- Combine with previous definitions

$$PF = \frac{I_{s1}}{I_s} DPF$$

$$PF = \frac{1}{\sqrt{1 + THD_i^2}} DPF$$



# • Idealized circuit, input current

- Fourier analysis gives additional harmonic components
  - Remember calculation uses RMS of  $I_s$ ,  $I_{s1}$  and  $I_d$

$$I_{s1} = \frac{2}{\pi} \sqrt{2} I_d = 0.9 I_d$$

$I_{sh} = 0$  for even harmonics

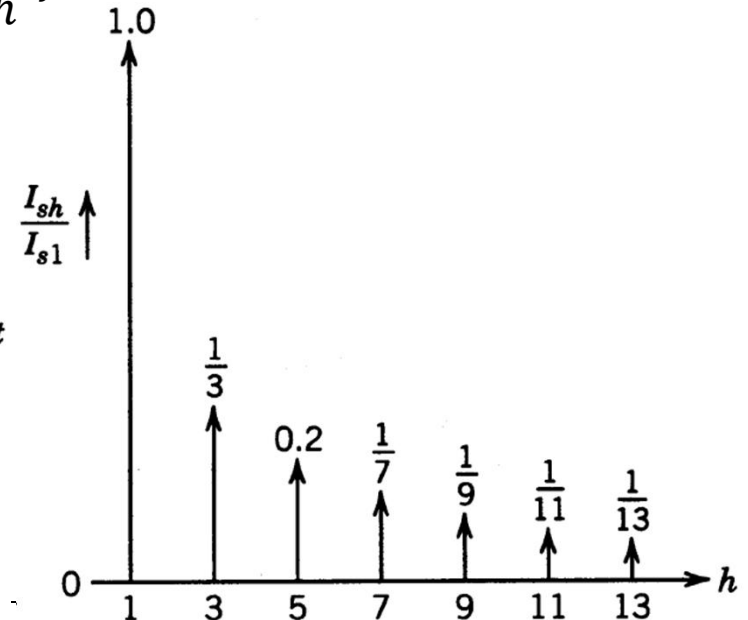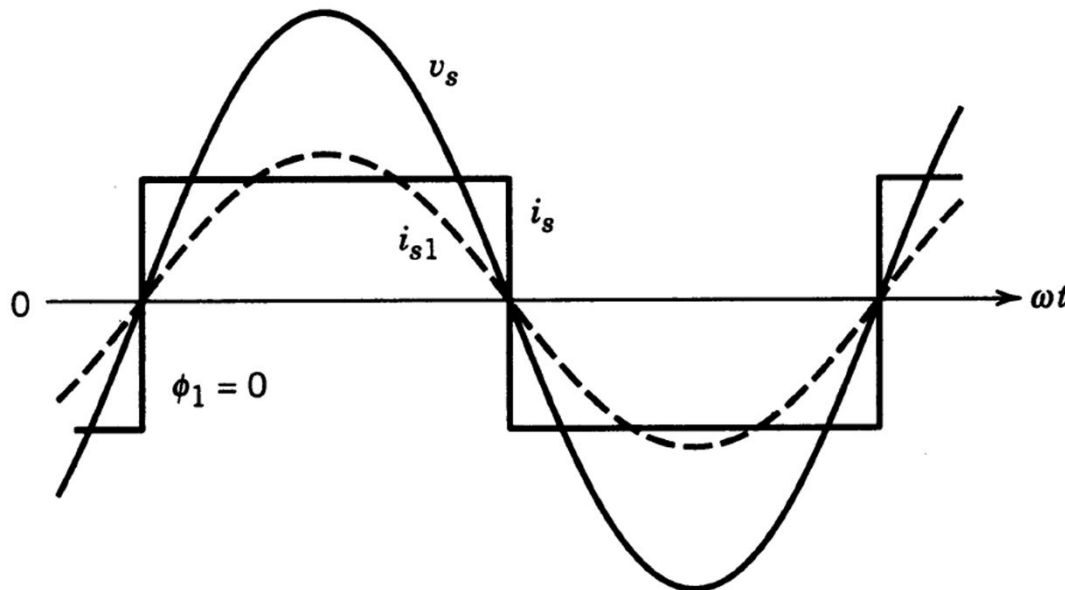$I_{sh} = \frac{I_{s1}}{h}$  for odd harmonics





# Exercises, lecture 2

5-1, 5-2, 5-3, 5-4, 5-7, 5-14

# 5-1

5-1 In the basic circuit of Fig. 5-3a,  $V_s = 120$  V at 60 Hz,  $L = 10$  mH, and  $R = 5$   $\Omega$ . Calculate and plot the current  $i$  along with  $v_s$ .

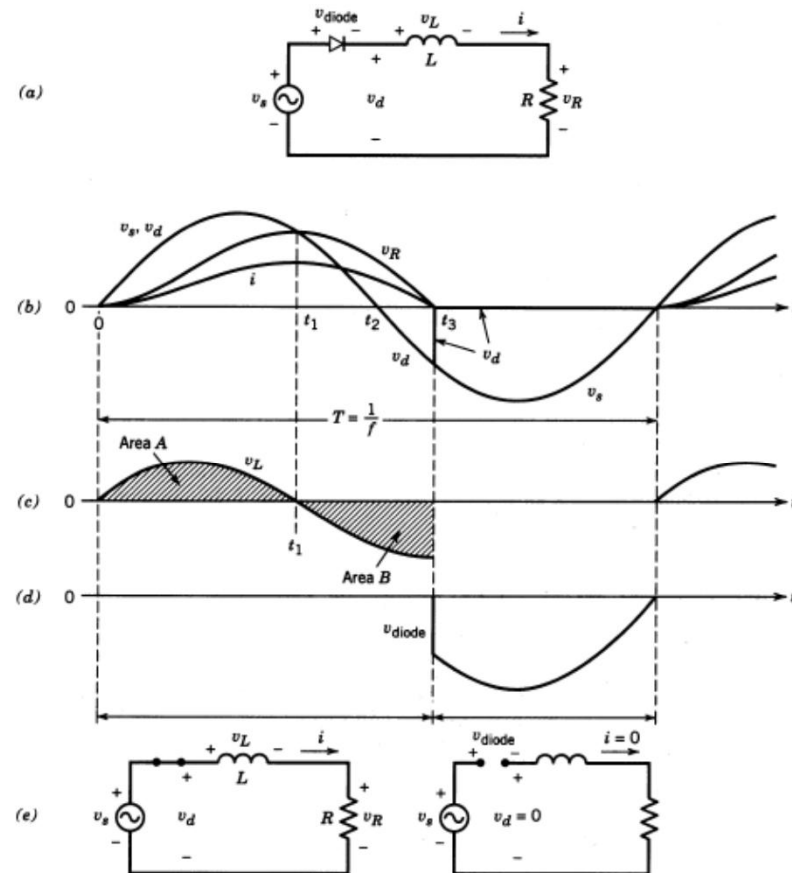


Figure 5-3 Basic rectifier with an inductive load.

# 5-2

5-2 In the basic circuit of Fig. 5-4a,  $V_s = 120$  V at 60 Hz,  $L = 10$  mH, and  $V_d = 150$  V. Calculate and plot the current  $i$

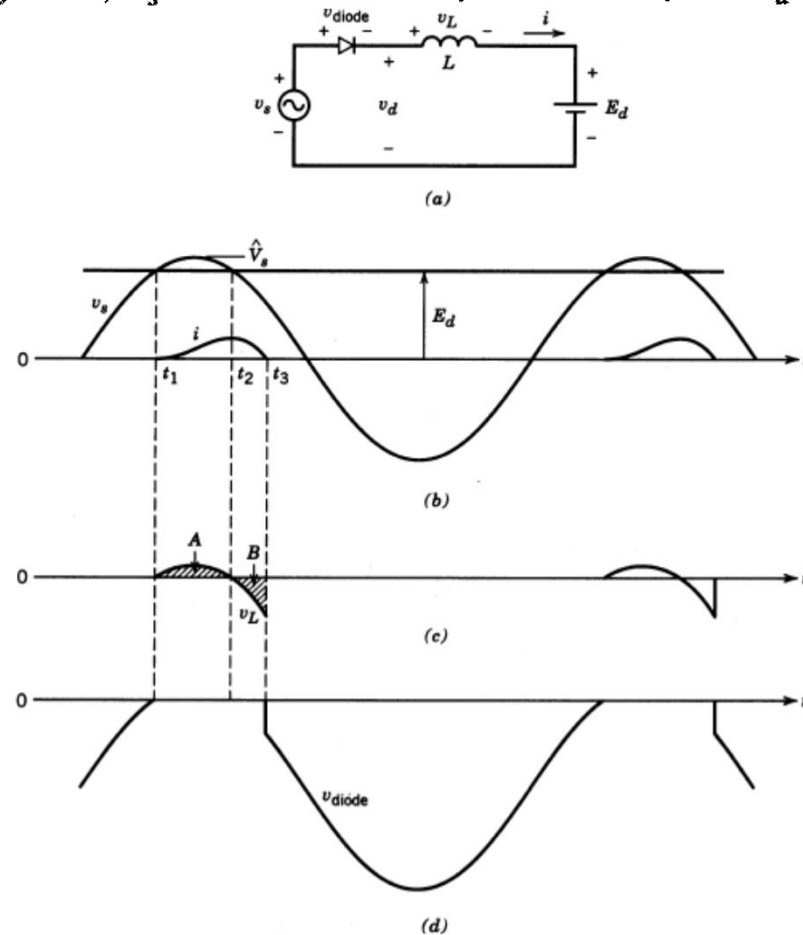


Figure 5-4 Basic rectifier with an internal dc voltage.

# 5-3

5-3 The voltage  $v$  across a load and the current  $i$  into the positive-polarity terminal are as follows (where  $\omega_1$  and  $\omega_3$  are not equal):

$$\begin{aligned}v(t) &= V_d + \sqrt{2}V_1\cos(\omega_1t) + \sqrt{2}V_1\sin(\omega_1t) + \sqrt{2}V_3\cos(\omega_3t) & \text{V} \\i(t) &= I_d + \sqrt{2}I_1\cos(\omega_1t) + \sqrt{2}I_3\cos(\omega_3t - \phi_3) & \text{A}\end{aligned}$$

Calculate the following:

- The average power  $P$  supplied to the load
- The rms value of  $v(t)$  and  $i(t)$
- The power factor at which the load is operating

### SINGLE-PHASE RECTIFIERS

5-4 In the single-phase diode rectifier circuit shown in Fig. 5-6b with zero  $L_s$  and a constant dc current  $I_d = 10$  A, calculate the average power supplied to the load:

- If  $v_s$  is a sinusoidal voltage with  $V_s = 120$  V at 60 Hz
- If  $v_s$  has the pulse waveform shown in Fig. P5-4



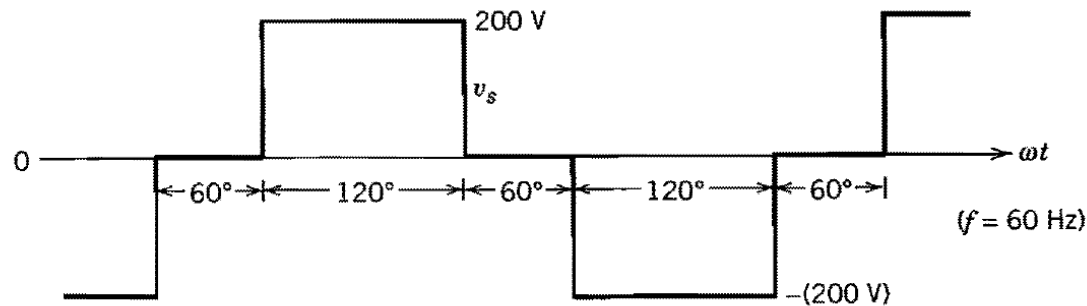


Figure P5-4

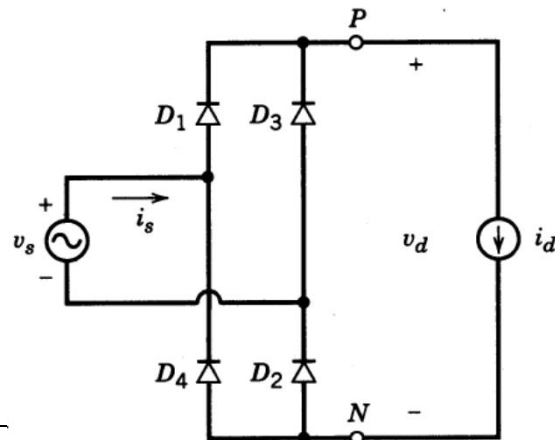

(b)


- 5-7 In the single-phase rectifier circuit of Fig. 5-20, assume the ac-side impedance to be negligible. Instead, an inductance  $L_d$  is placed between the rectifier output and the filter capacitor. Derive the minimum value of  $L_d$  in terms of  $V_s$ ,  $\omega$ , and  $I_d$  that will result in a continuous  $i_d$  assuming that the ripple in  $v_d$  is negligible.

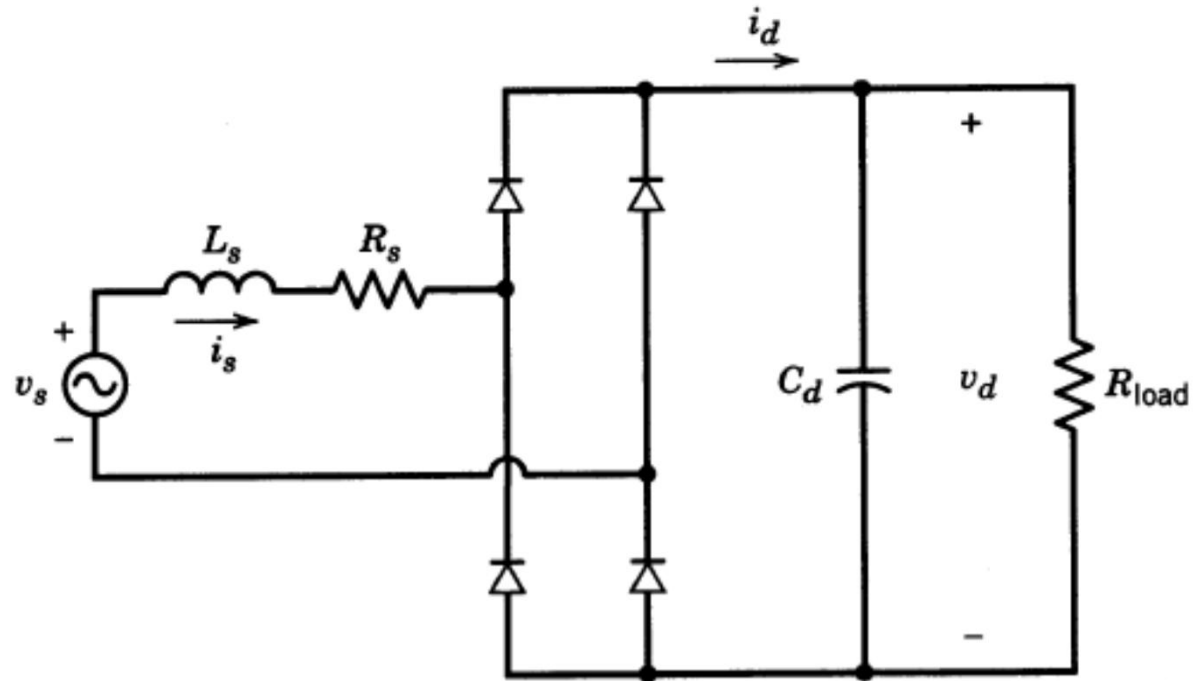

**Figure 5-20** Practical diode-bridge rectifier with a filter capacitor.
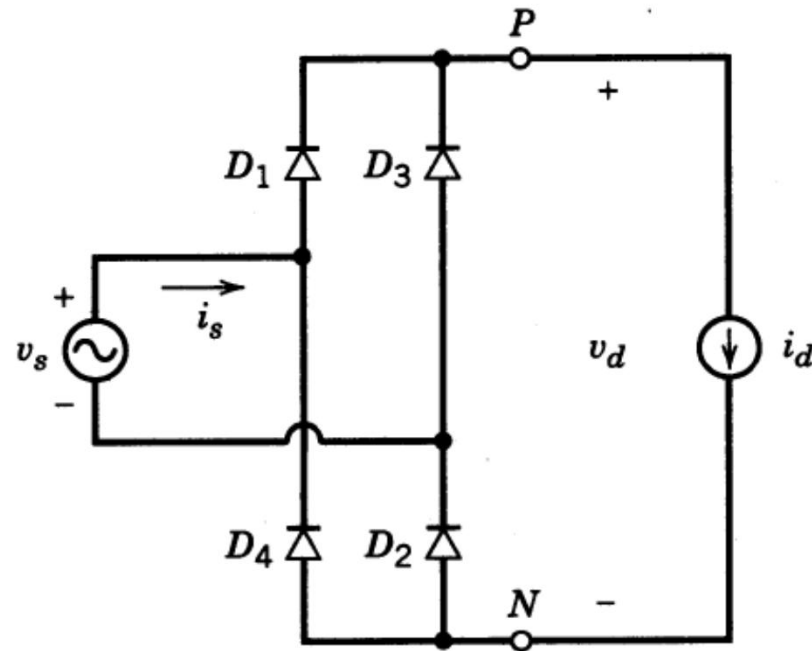
# 5-14

- In the single-phase rectifier circuit of Fig. 5-6b with  $i_d = I_d$ , obtain the THD, DPF, PF, and CF.



(b)

TSTE19/Tomas Jonsson

[www.liu.se](http://www.liu.se)