

TSTE19 Power Electronics

Lecture 5

Tomas Jonsson


ISY/EKS

Outline

- Semiconductor switches
- Thermal aspects



Component choice

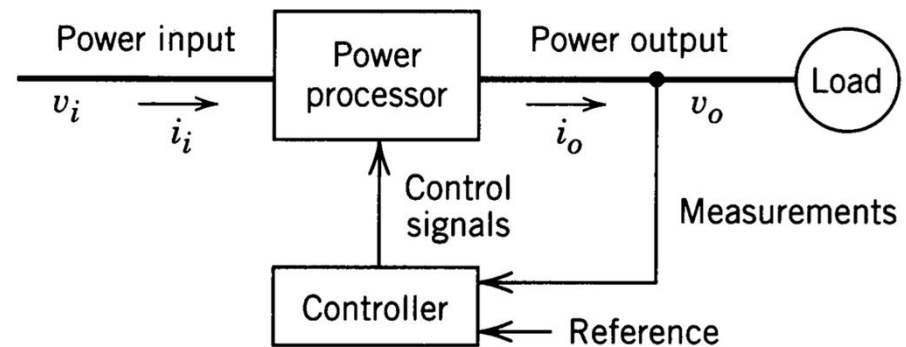- Power processor components should not dissipate active power
 - Avoid resistances
 - Use L, C, transformers, switches (semiconductors)
- Control part may still use “ordinary” components, including resistors
 - Control is assumed to have much smaller power dissipation compared to the power processor





Ideal switch

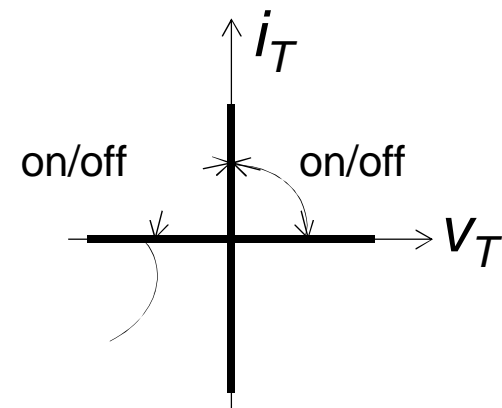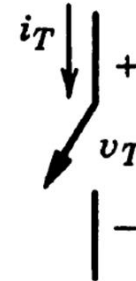- Accept voltages of both polarities
 - Both negative and positive
- Conduct current in one direction
 - Only positive current
- No breakdown voltage
 - Perfect isolation in off state
- Zero on-resistance
 - No voltage drop over the switch
- No switch delay
- Zero energy switching
 - No power dissipated during operation



Non-ideal switch example

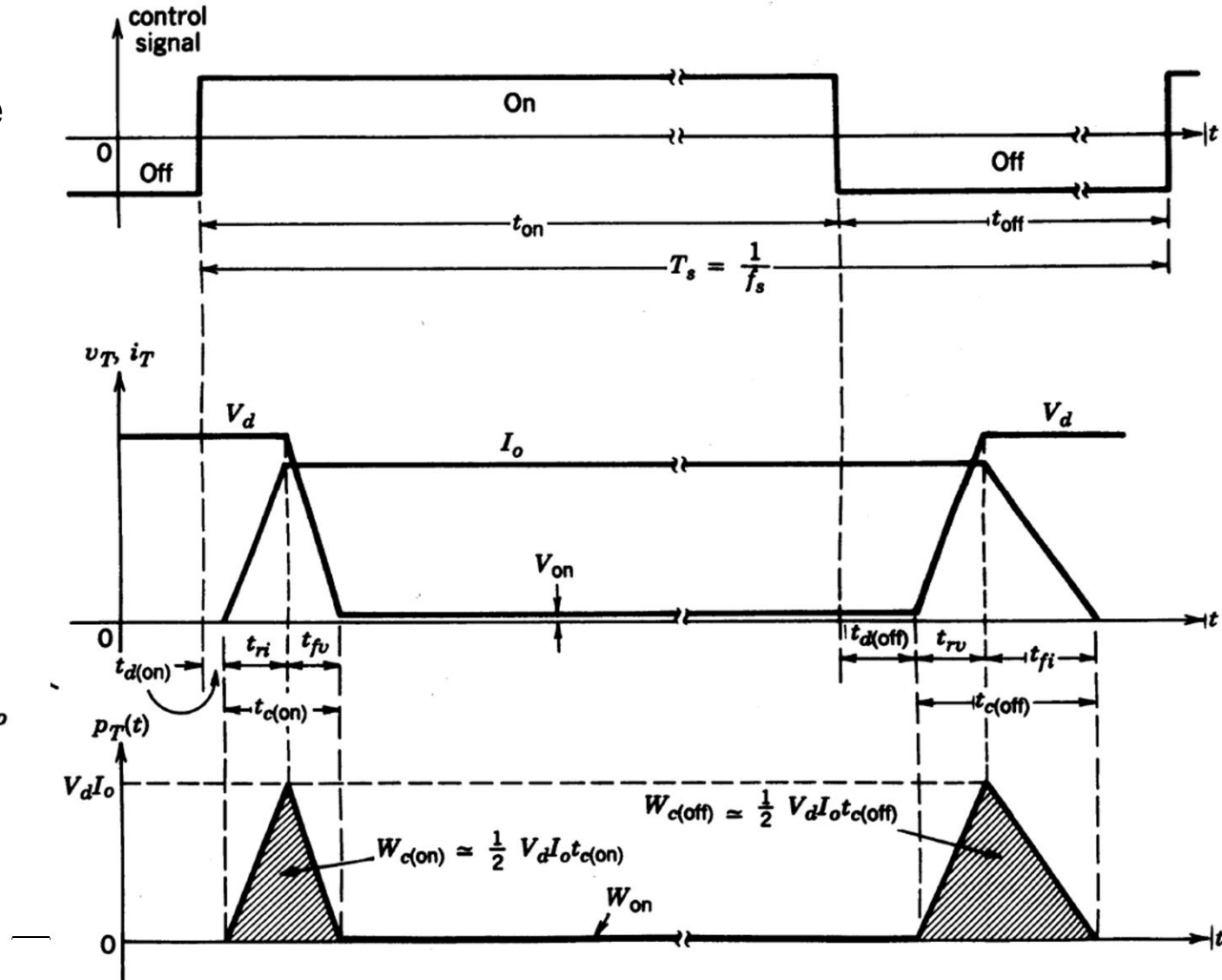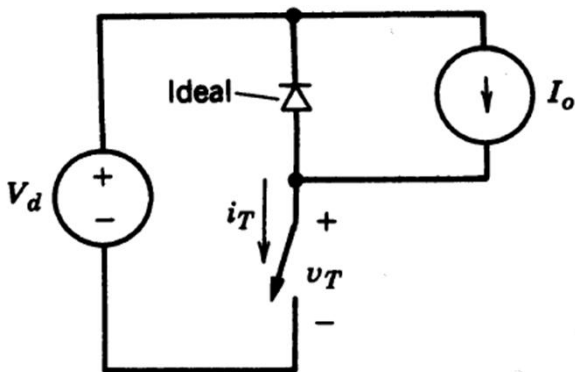- Linear model
 - Rise and fall time on both V and I
 - Voltage drop V_{on}
 - I_o models an inductor
- Power loss!



Non-ideal switch example, cont.

- Power loss during switching


$$P_s = \frac{1}{2} V_d I_o f_s (t_{c(on)} + t_{c(off)})$$

- Power loss during on-state

$$P_{on} = V_{on} I_o \frac{t_{c(on)}}{T_s}$$




- Total power in the switch

$$P_T = P_s + P_{on}$$

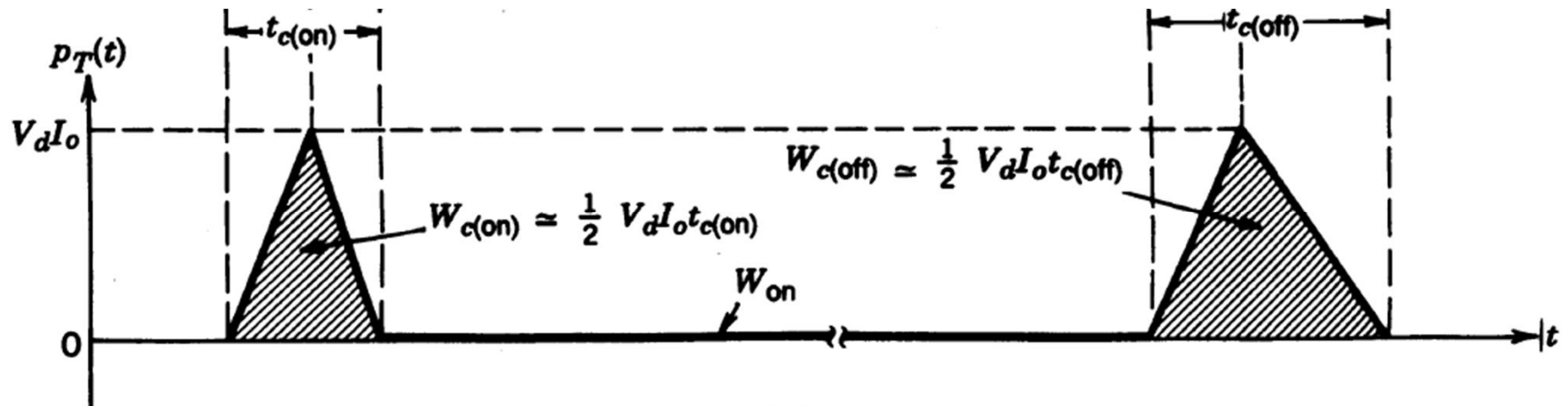



Bipolar junction transistors (BJT)

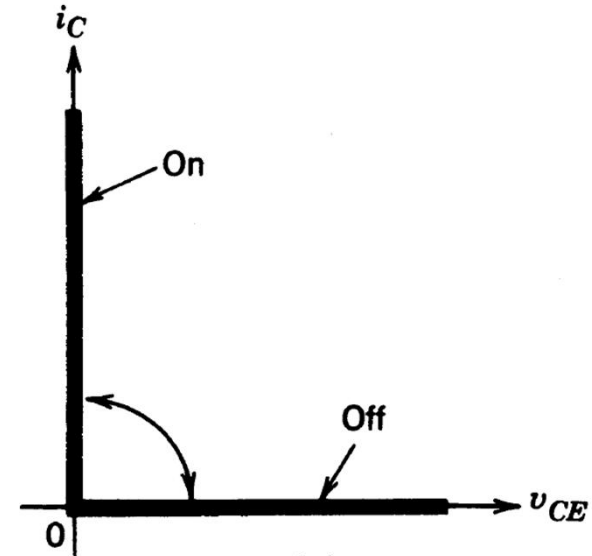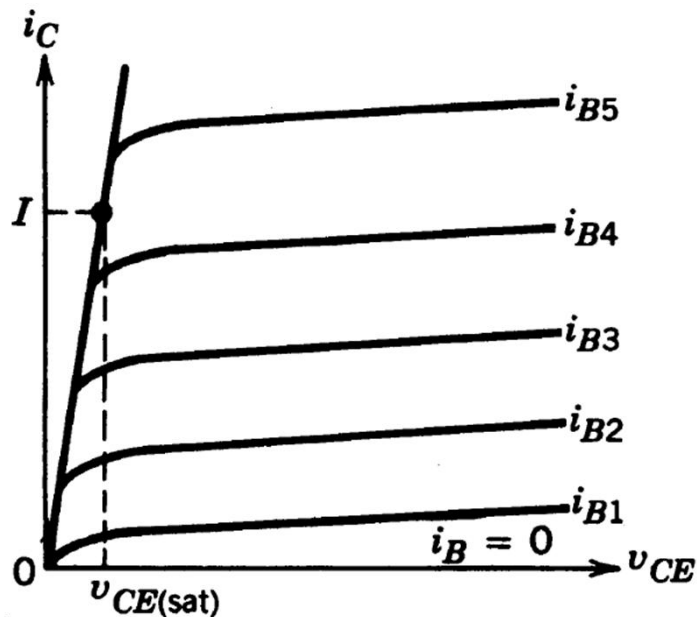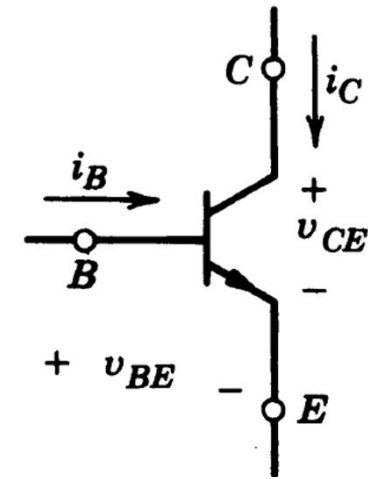- Continuous control current when on
- $5 < h_{FE} = \frac{I_C}{I_B} < 10$ for power BJT
- Possible to turn on and off






Darlington bipolar transistors

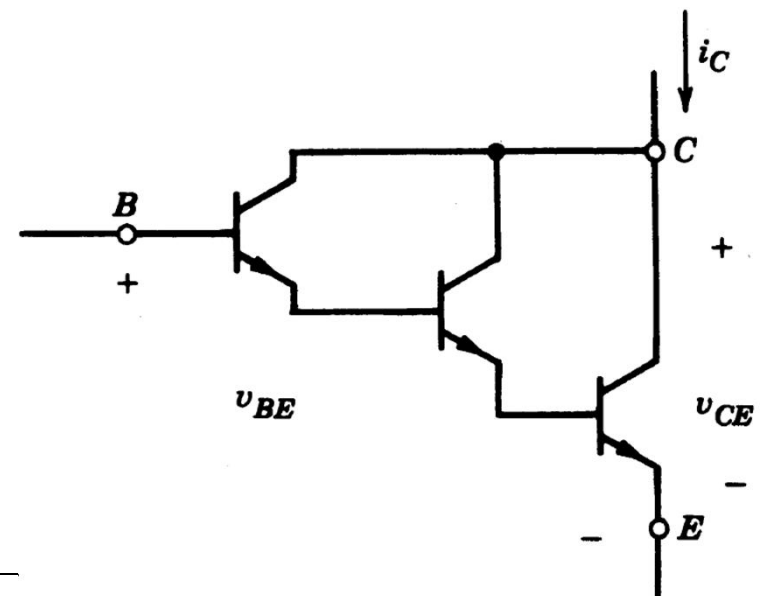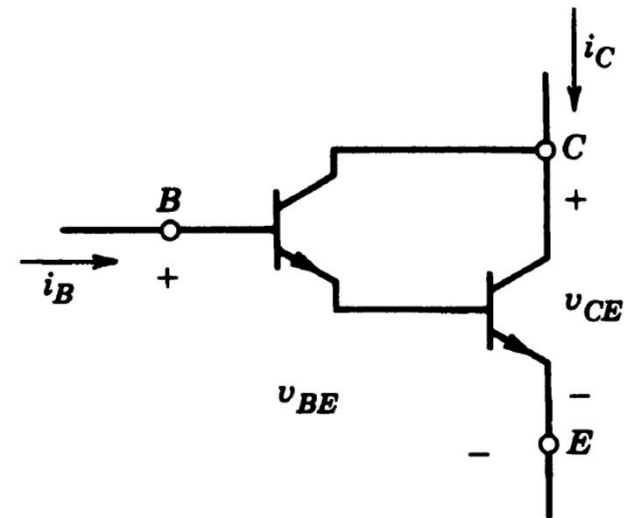- Increase h_{FE}
- Increases also v_{CEsat}
- $0.1 \text{ us} < \text{switching time} < 10 \text{ us}$
- Integrated on a single silicon chip




MOSFET transistors

- Voltage controlled
- Fast switching
 - $10 \text{ ns} < t < 500 \text{ ns}$
- Tradeoff R_{on} vs Blocking voltage

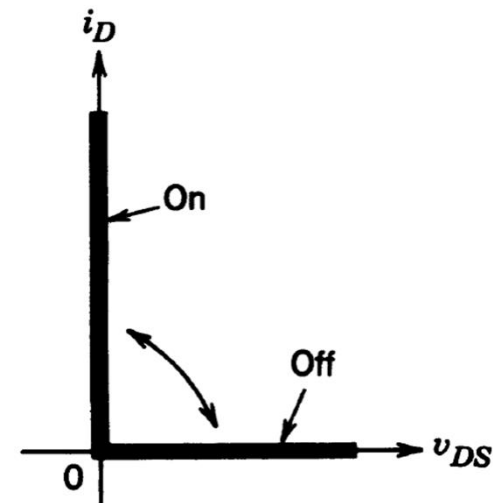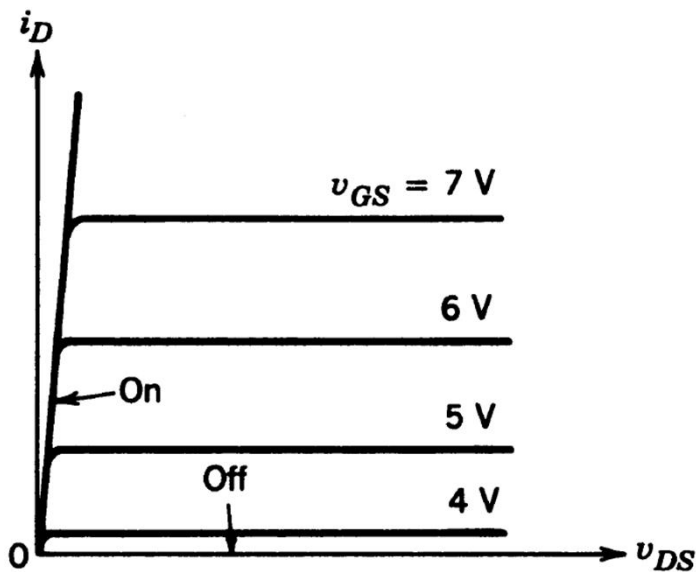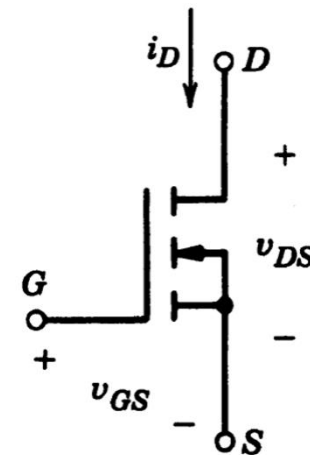

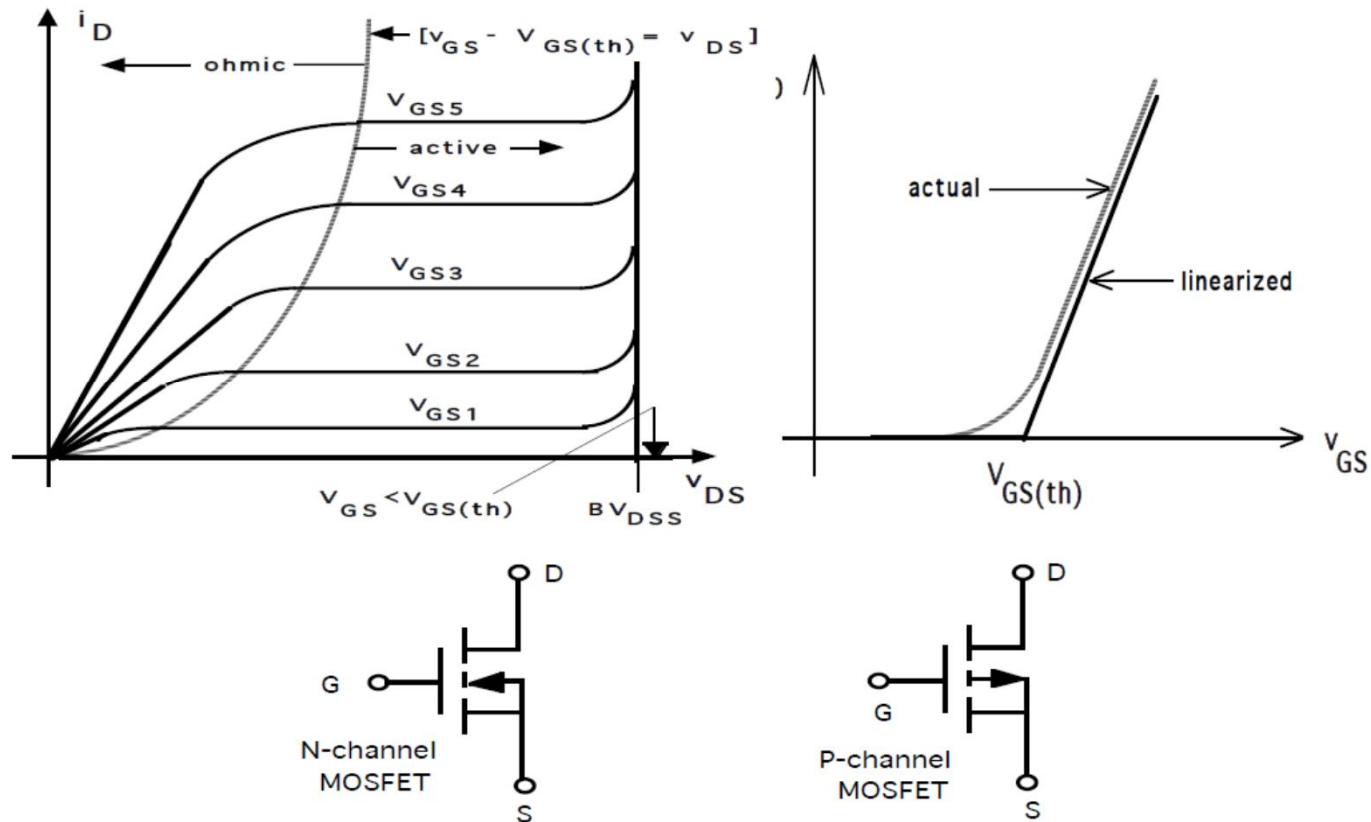
MOSFET I-V Characteristics and Circuit Symbols



Copyright © by John Wiley & Sons 2003


MOSFET implementation

- Thousands of cells in parallel

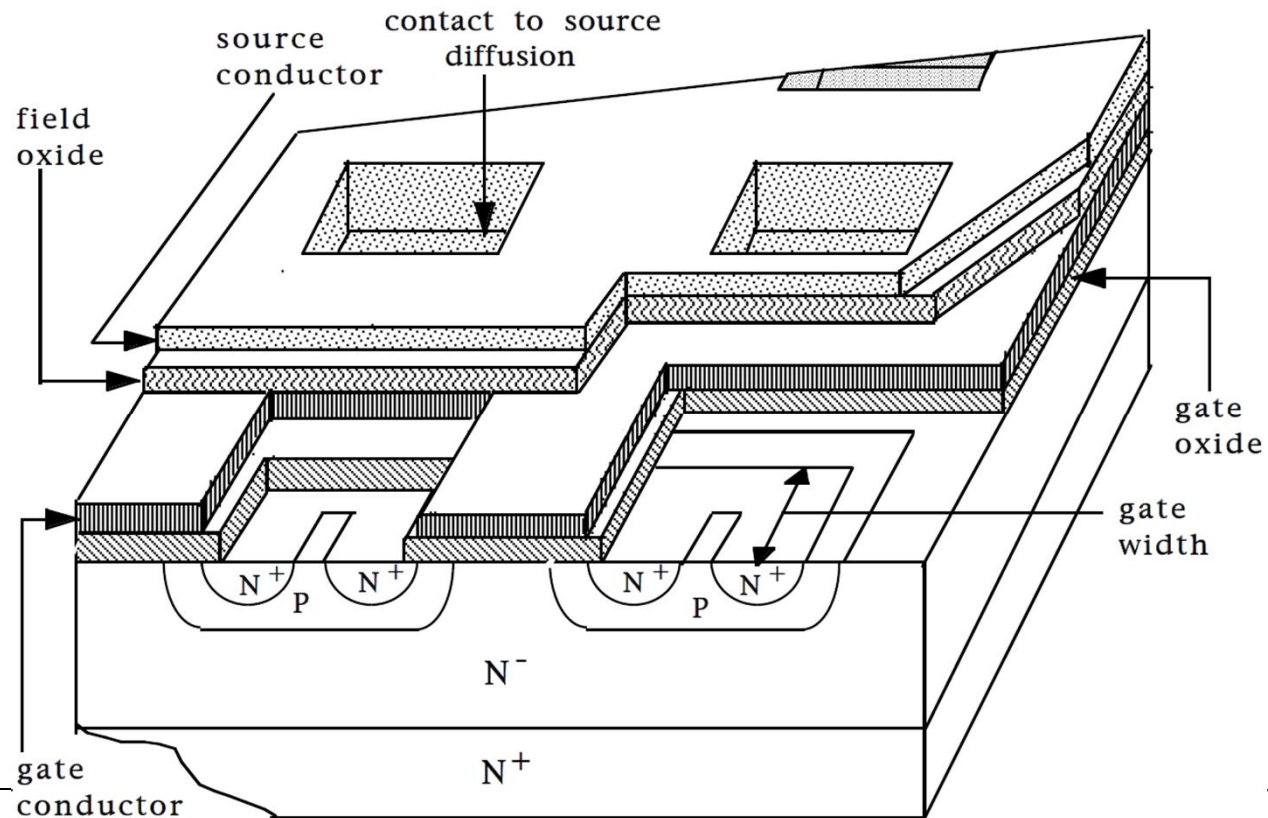


MOSFET channel conduction control

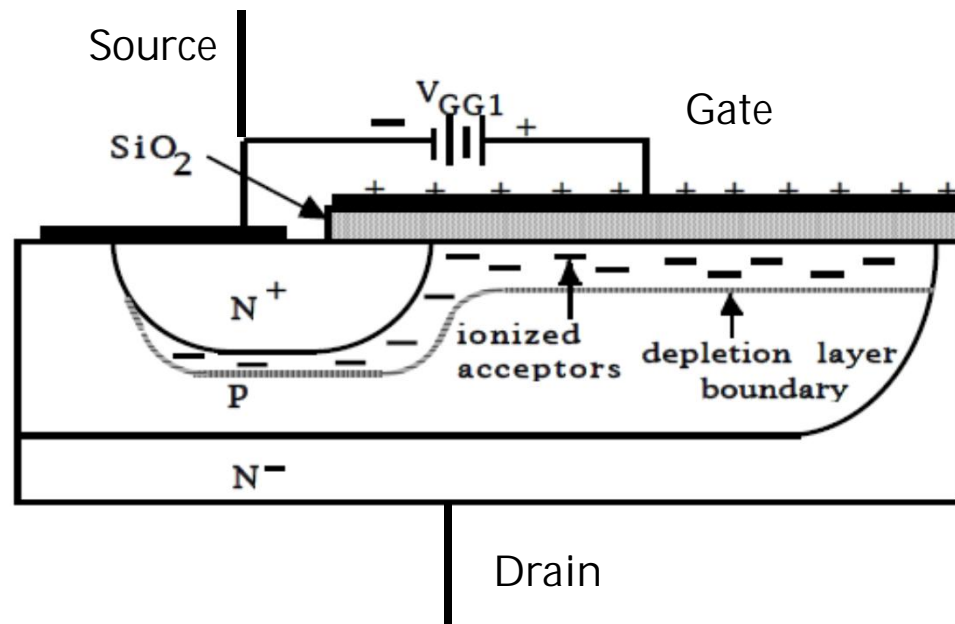- Low gate voltage
- Inversion layer isolating drain N^- from source N^+




MOSFET channel conduction control

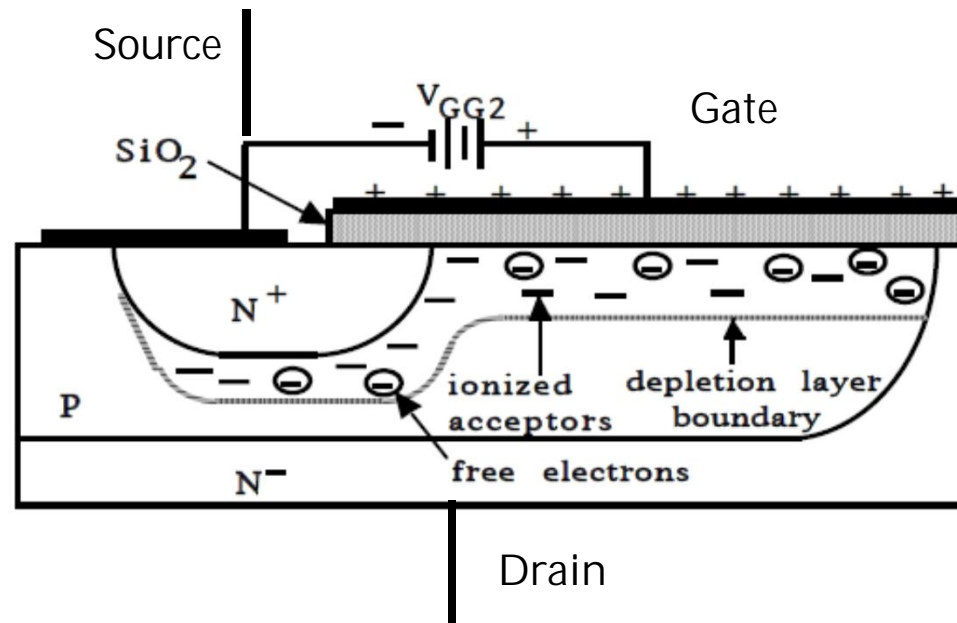- Increasing gate voltage but below threshold
- Inversion layer with some free electrons still isolating drain N^- from source N^+




MOSFET channel conduction control

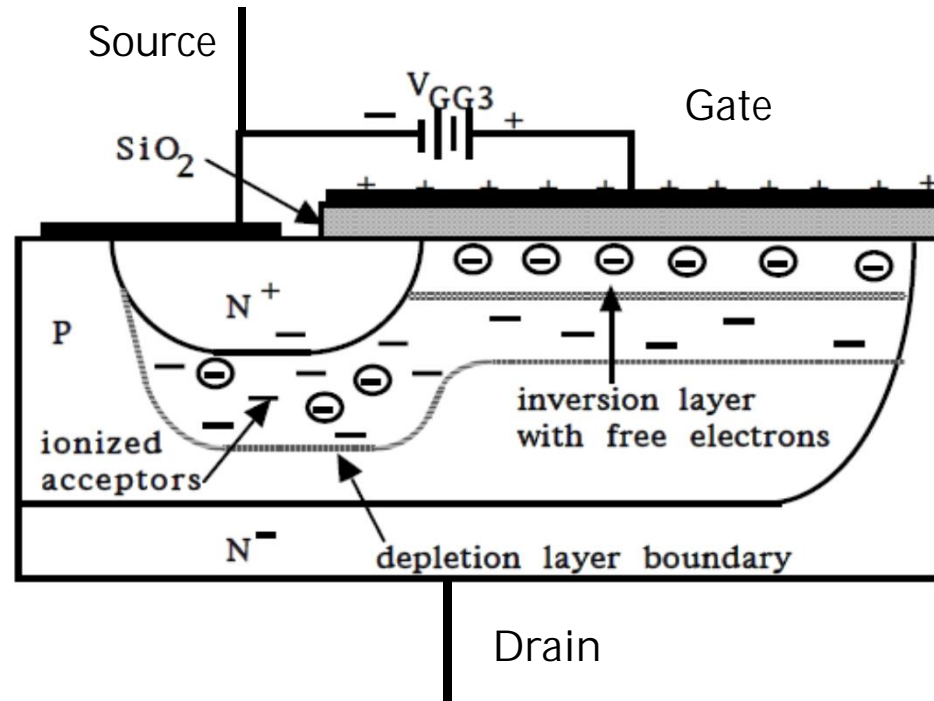- High gate voltage above threshold
- Conductive channel of free electrons formed between drain N^- and source N^+




Switching MOSFET – Diode pair

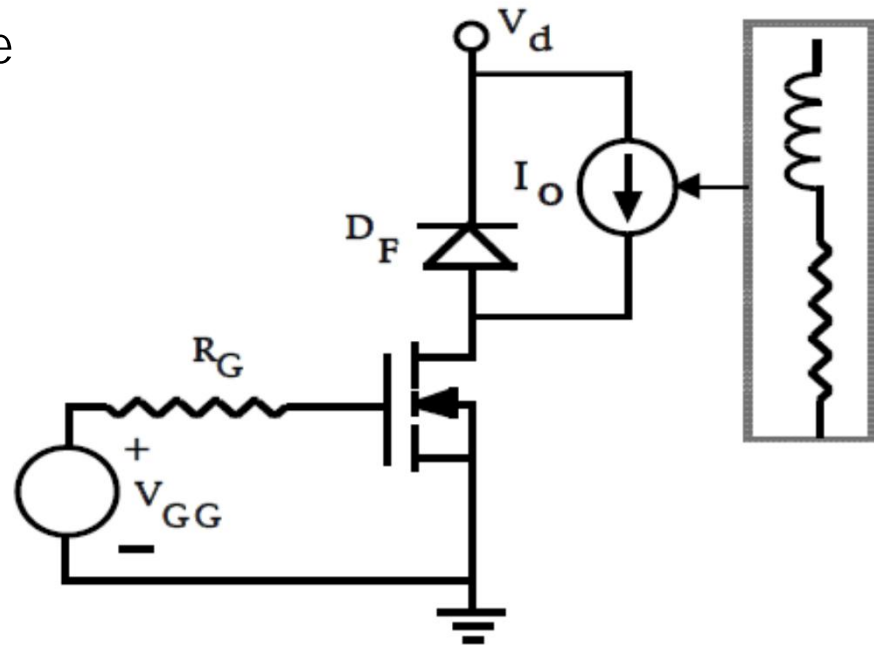- The current I_o is either conducted through the diode (when MOSFET is off) or through the MOSFET
- Turn-on: $V_{GG} \gg V_{th}$
- Turn-off: $V_{GG} = 0$




MOSFET turn-on/turn-off equivalent

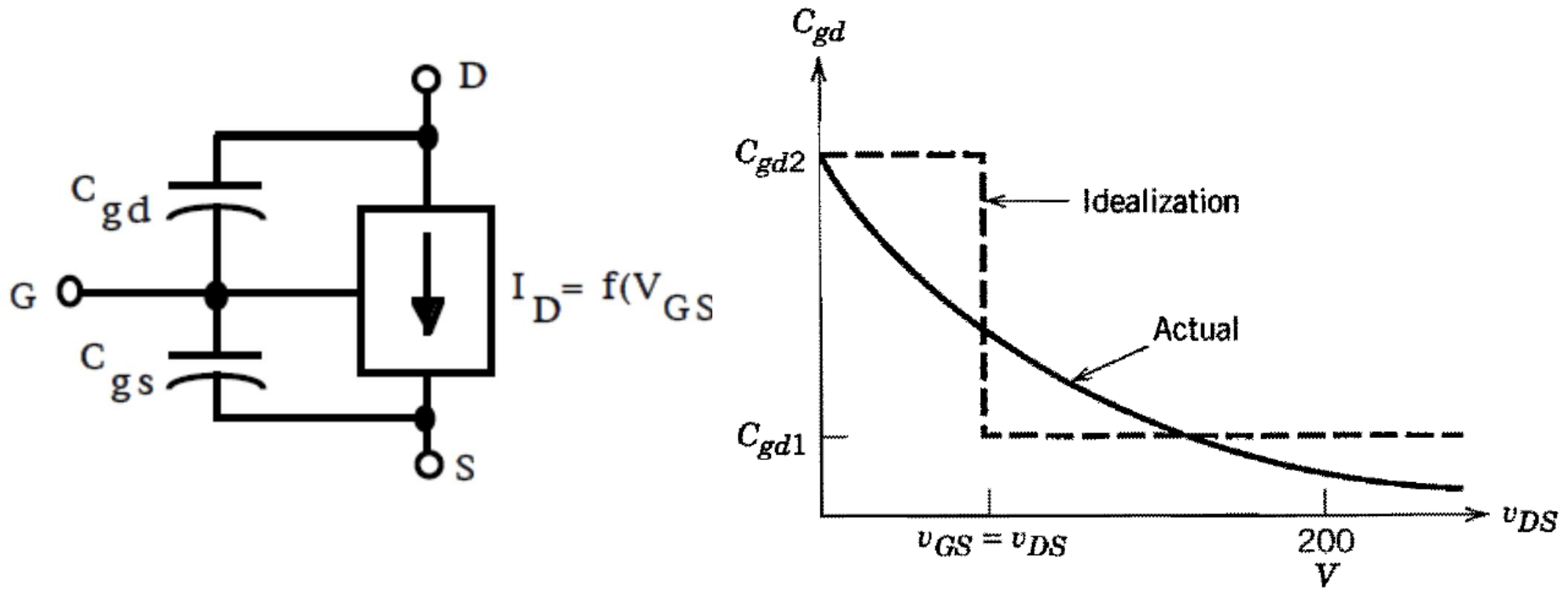


- MOSFET equivalent circuit valid for off-state (cutoff) and active region operation.

MOSFET on-state equivalent

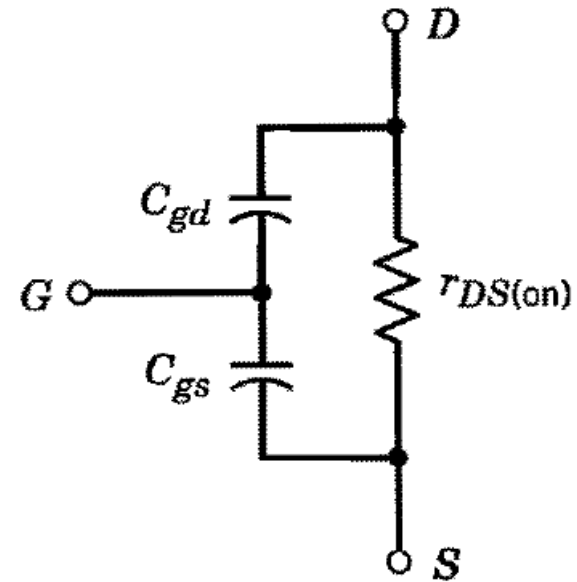


- MOSFET equivalent circuit valid for on-state (triode) region operation.

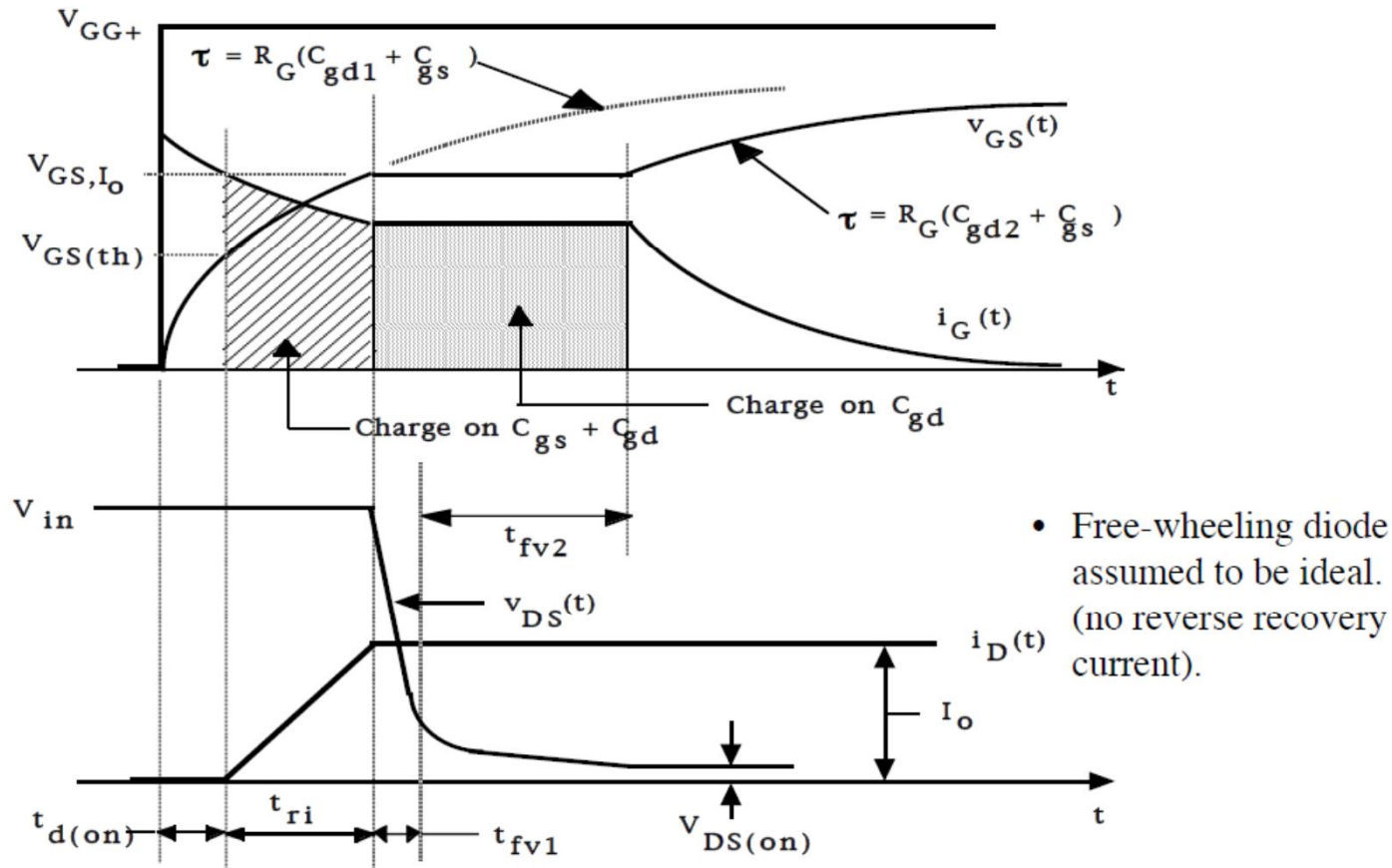MOSFET-based Buck Converter Turn-on Waveforms




Copyright © by John Wiley & Sons 2003

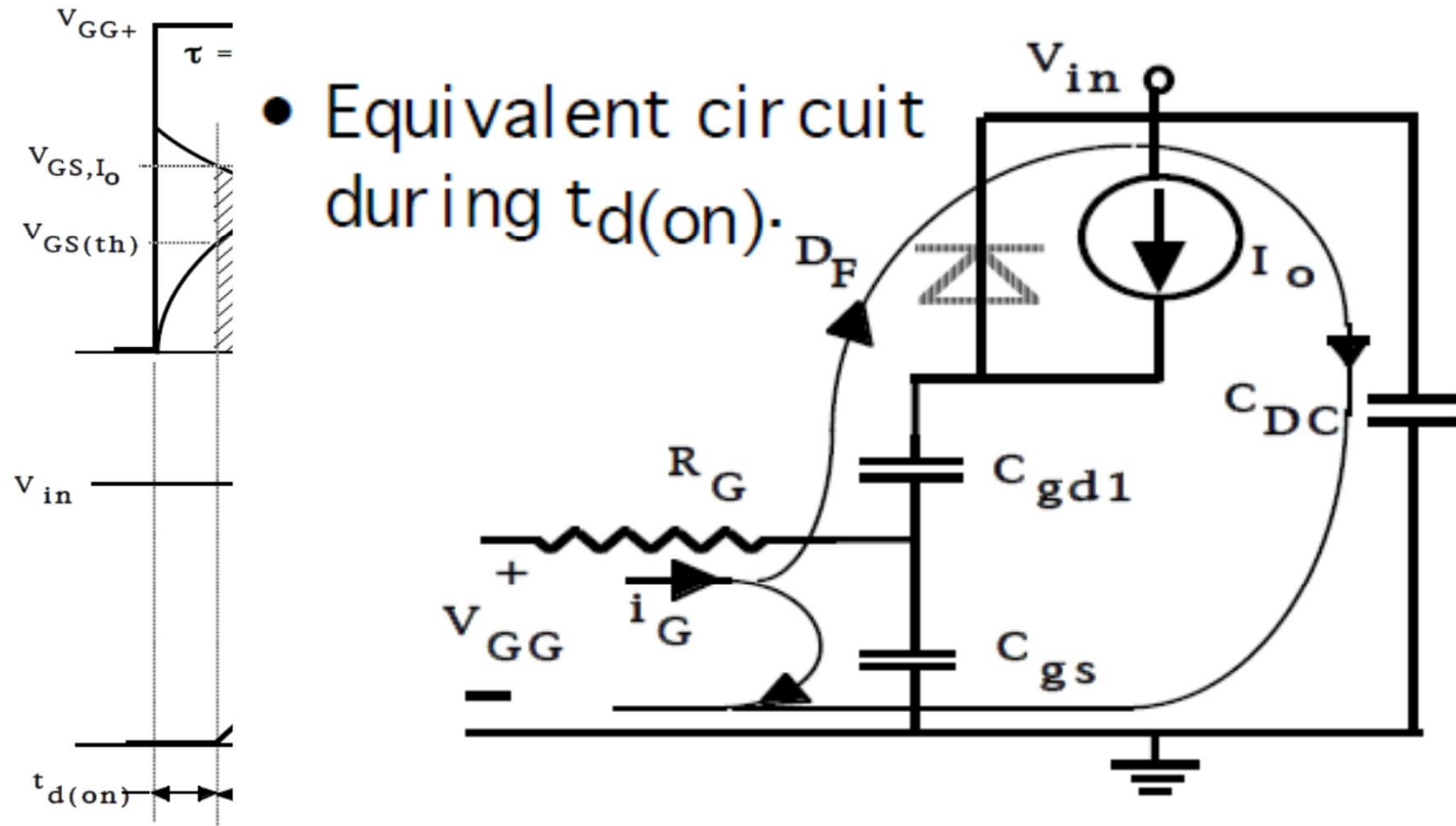MOSFET-based Buck Converter Turn-on Waveforms




Copyright © by John Wiley & Sons 2003

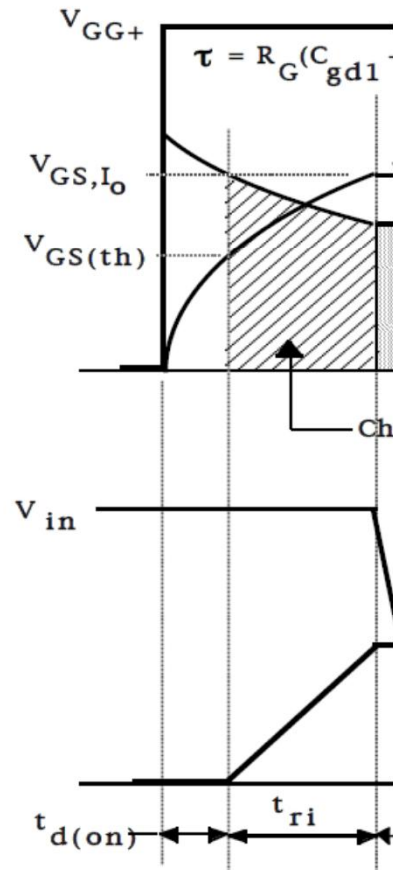MOSFET-based Buck Converter Turn-on Waveforms




- Equivalent circuit during t_{ri} .

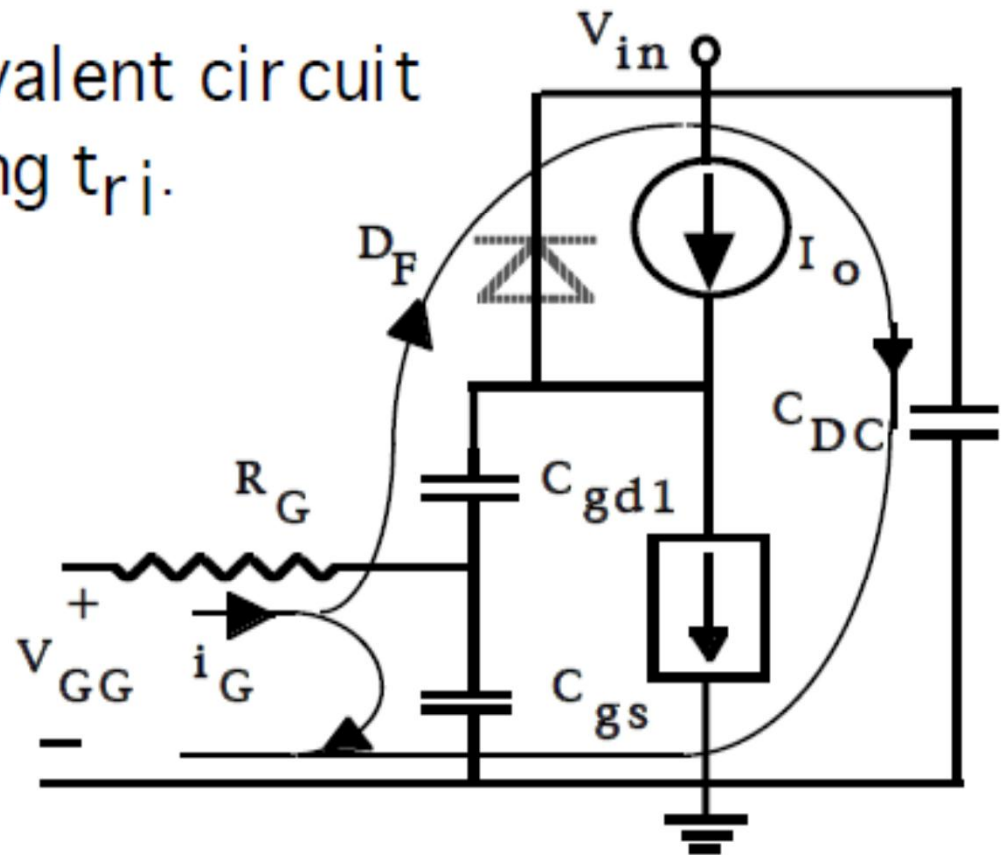


Copyright © by John Wiley & Sons 2003

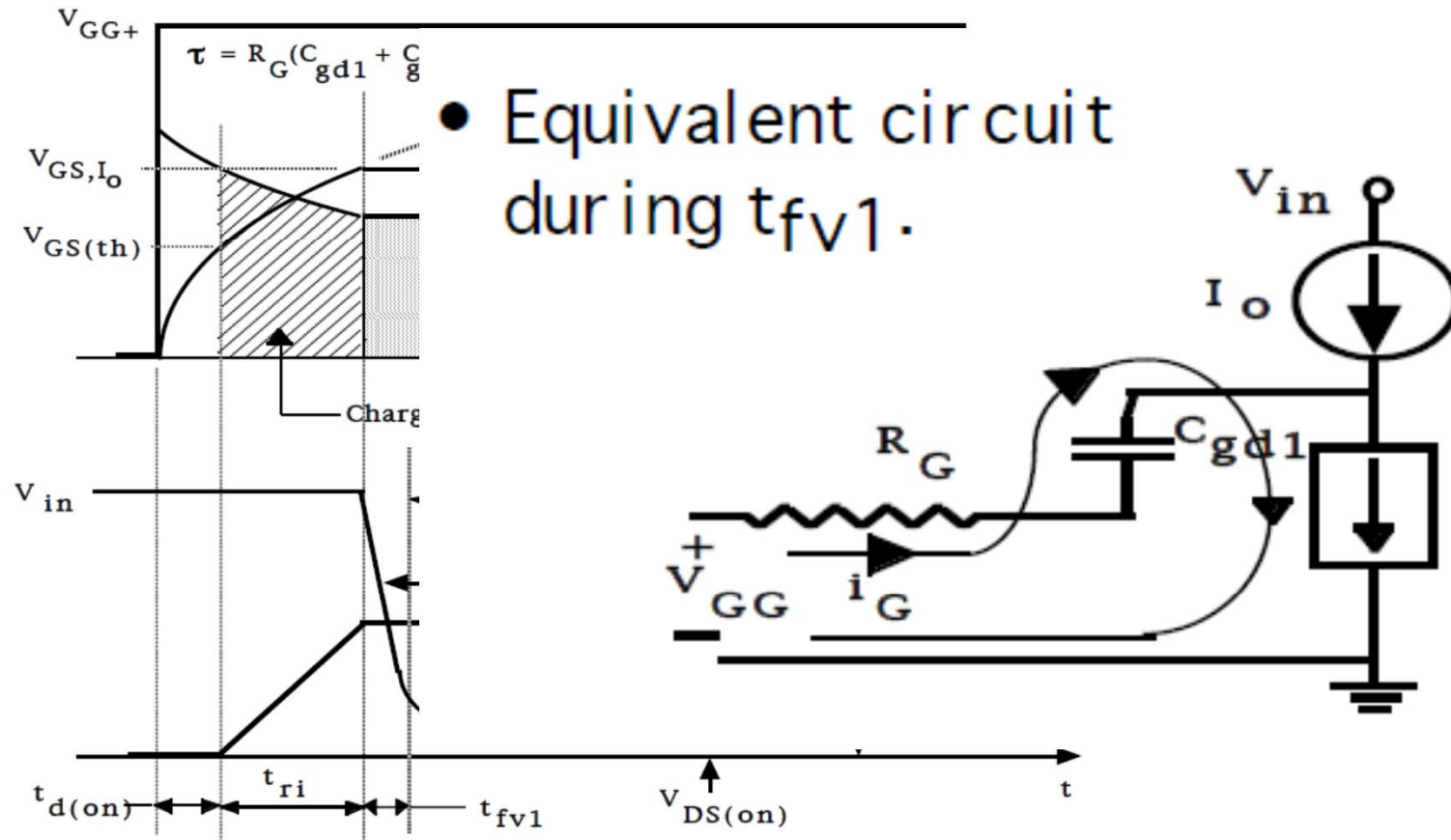MOSFET-based Buck Converter Turn-on Waveforms



Copyright © by John Wiley & Sons 2003

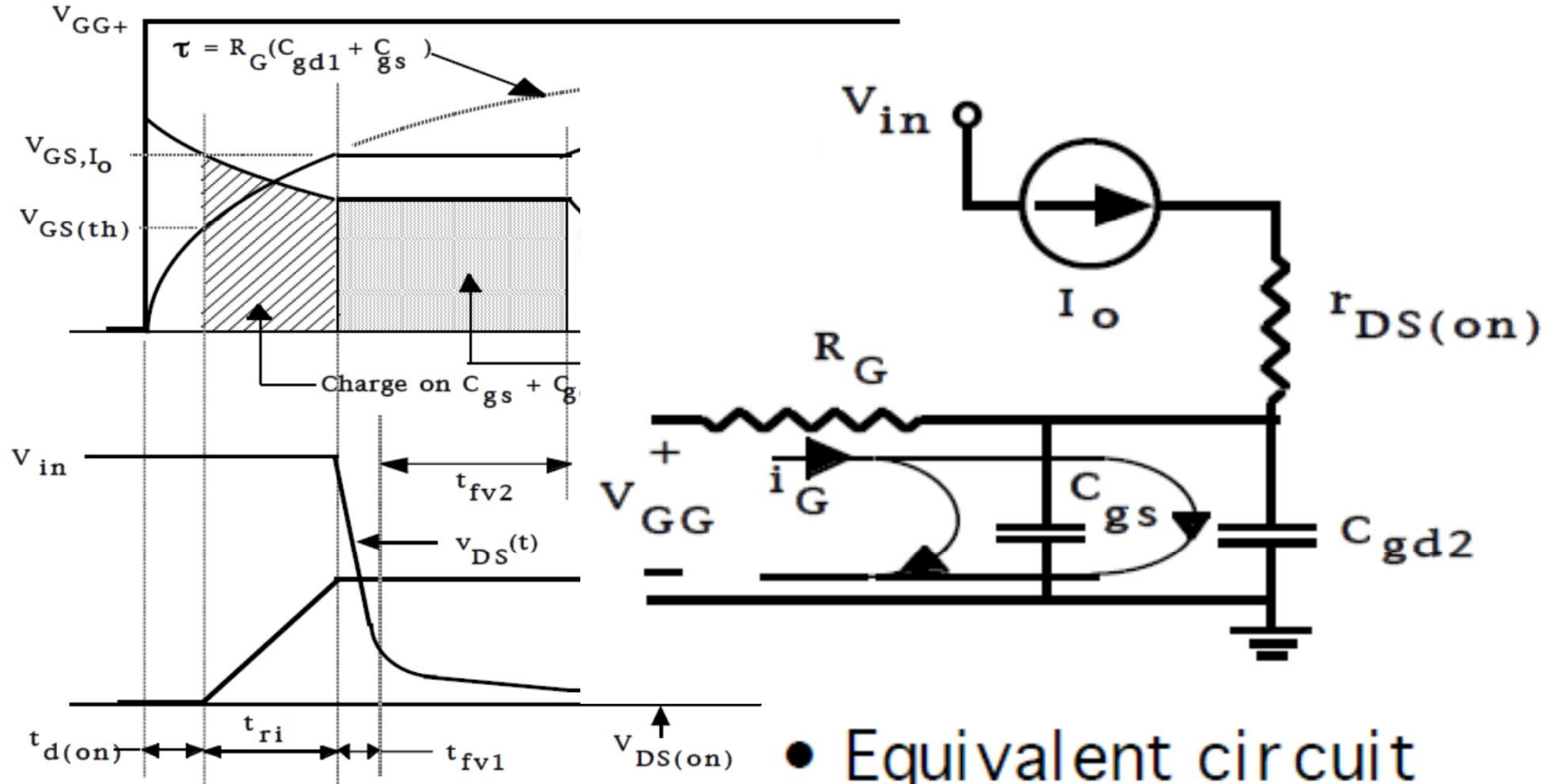
MOSFET-based Buck Converter Turn-on Waveforms



- Equivalent circuit during t_{fv2} .

Copyright © by John Wiley & Sons 2003

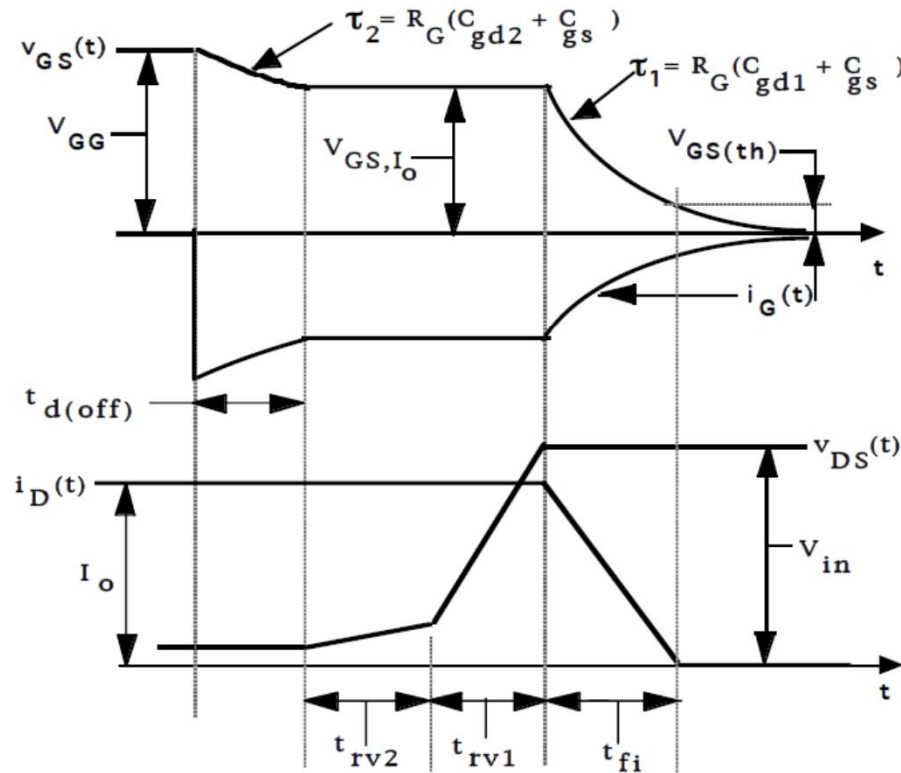MOSFET-based Buck Converter Turn-off Waveforms




- Assume ideal free-wheeling diode.
- Essentially the inverse of the turn-on process.
- Model quantitatively using the same equivalent circuits as for turn-on. Simply use correct driving voltages and initial conditions

Copyright © by John Wiley & Sons 2003

Lecture 5

Exercises



22-13

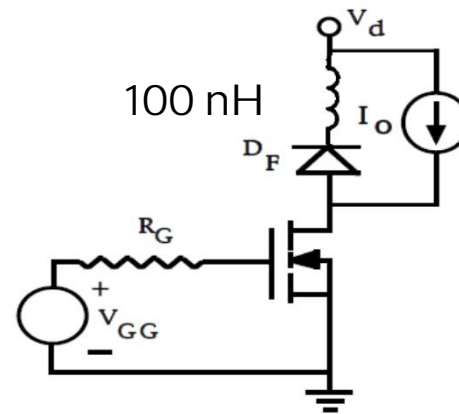

- A MOSFET step-down converter such as shown in Fig. 22-10 operates at a switching frequency of 30 kHz with a 50% duty cycle at an ambient temperature of 50°C.
- The power supply $V_d = 100$ V and the load current $I_o = 100$ A.
- The free-wheeling diode is ideal but a stray inductance of 100 nH is in series with the diode.
- The MOSFET characteristics are listed below:
 $B_{VDSS} = 150$ V; $T_{j,max} = 150$ °C; $R_{th,j-a} = 1$ K/W; $r_{DS(on)} = 0.01$ ohm,
 $t_{ri} = t_{fi} = 50$ ns; $t_{rv} = t_{fv} = 200$ ns; $I_{D,max} = 125$ A
- Is the MOSFET overstressed in this application and if so, how? Be specific and quantitative in your answer.




5-100

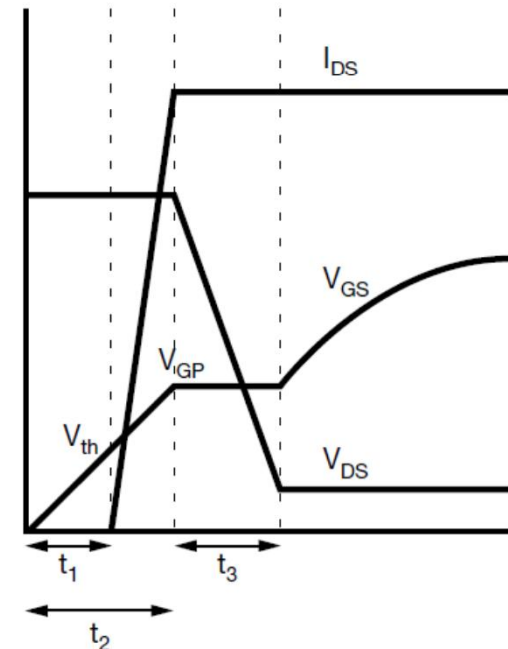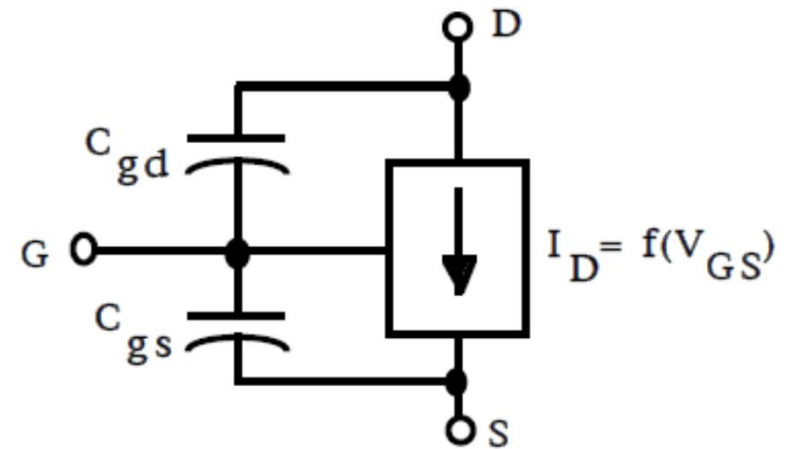- For the step-down converter in 22-13 the dV/dt during turn-on is defined by V_d (assume $V_{dson}=0$) and t_{fv} .
- The gate-drain capacitance, $C_{gd} = 120$ pF. The miller plateau voltage $V_{GP} = 4V$
- Calculate the gate resistance, R_G for a gate drive giving $V_{GG} = 10V$.




Insulated gate bipolar (IGBT)

- High input impedance
- Small on-state voltage
- Large blocking voltage
- Combined with anti-parallel diode

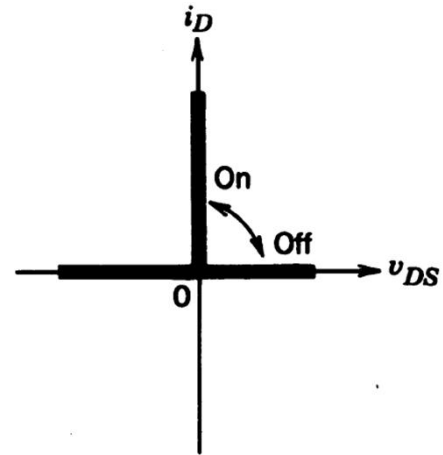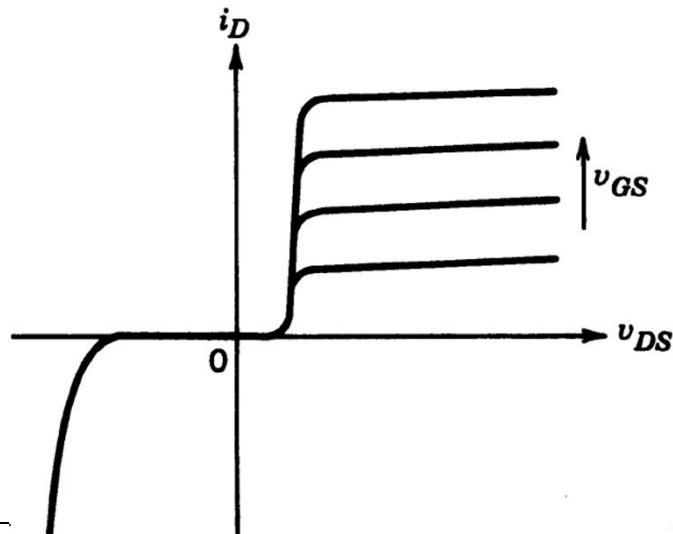
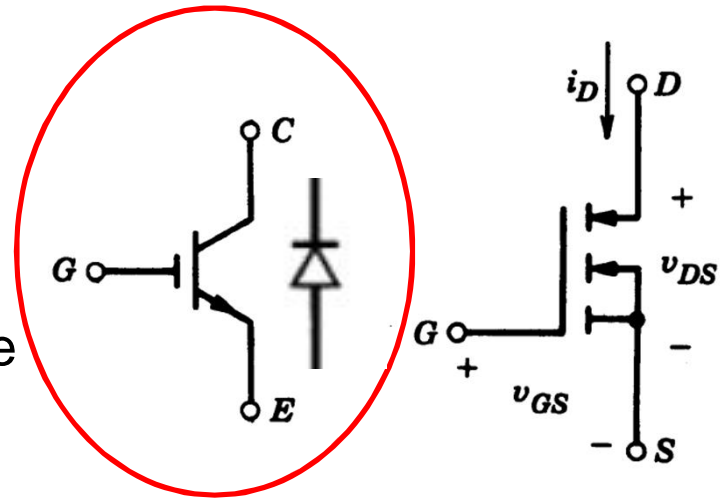


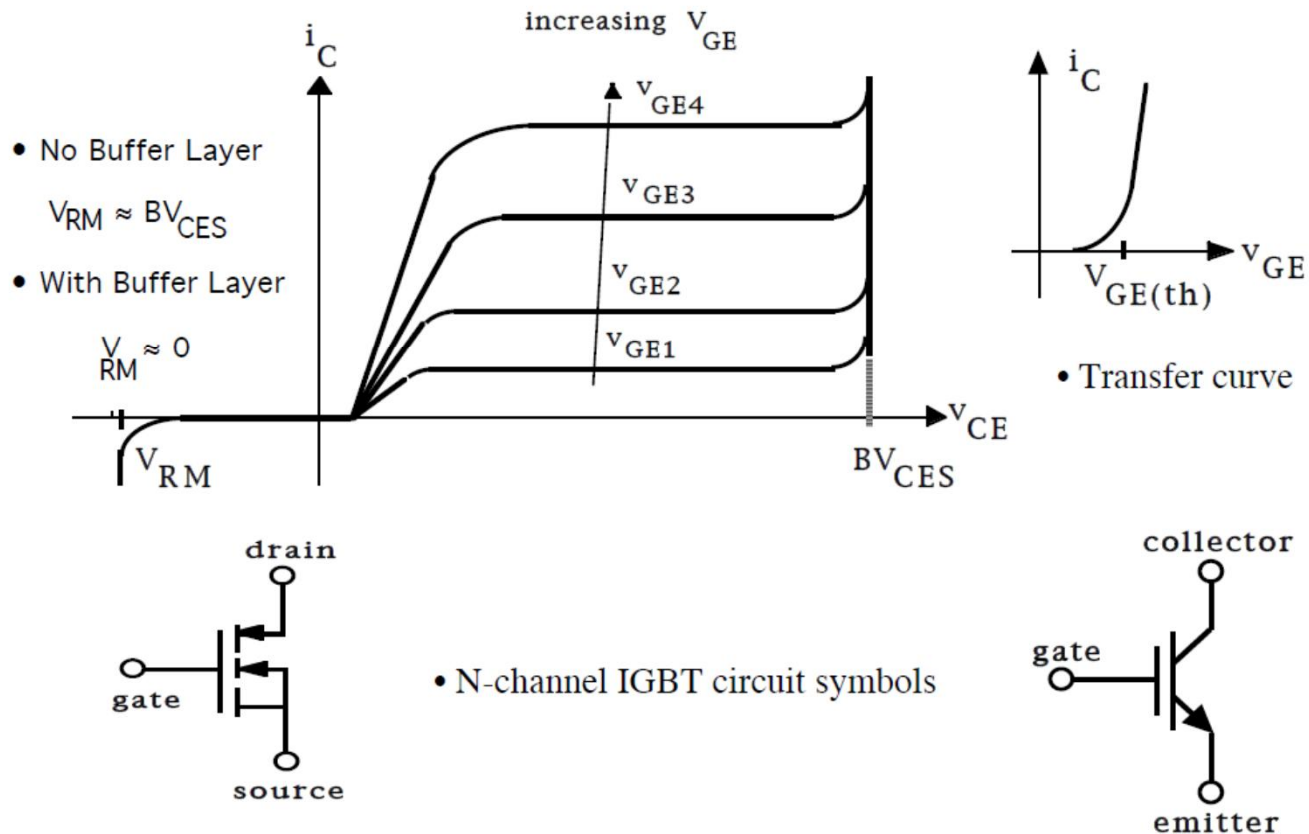IGBT I-V Characteristics and Circuit Symbols





Insulated gate bipolar (IGBT) implementation

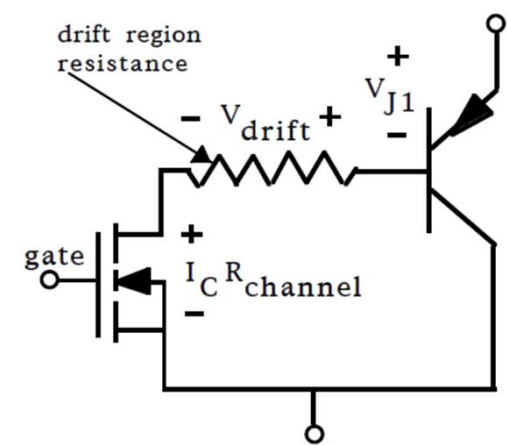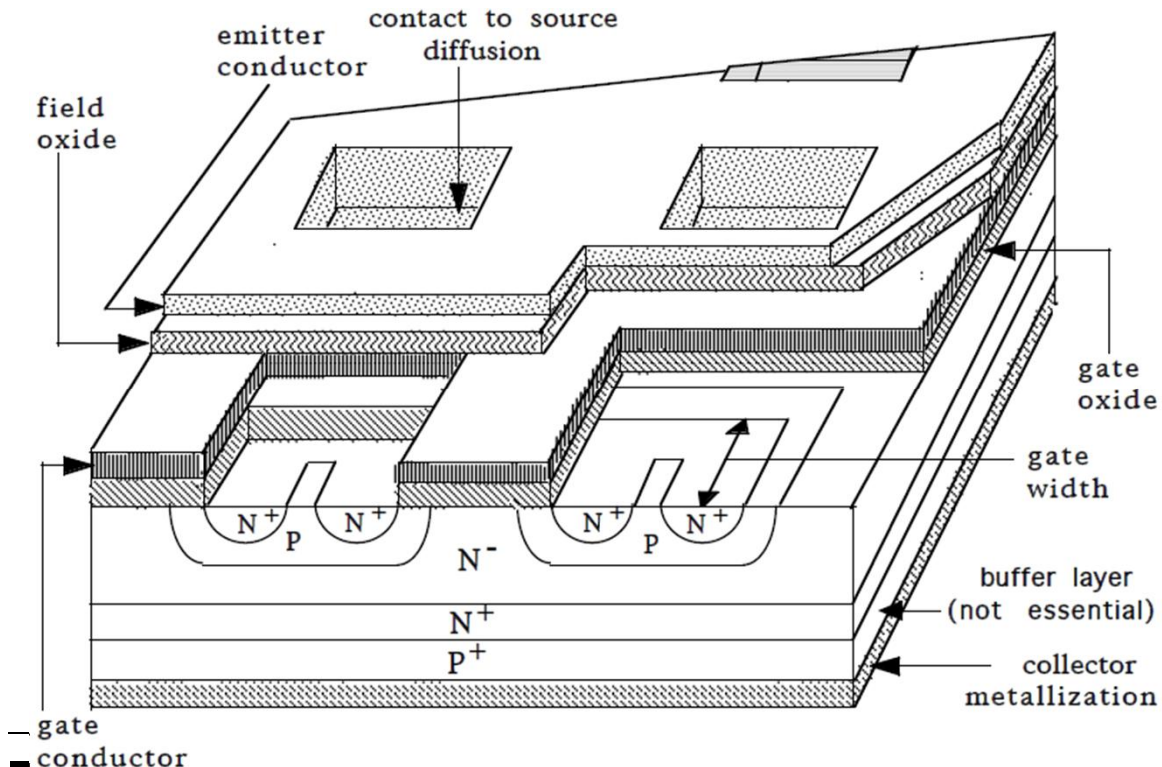- Chip view, and approximate equivalent circuit





Gate-turn-off Thyristor (GTO)

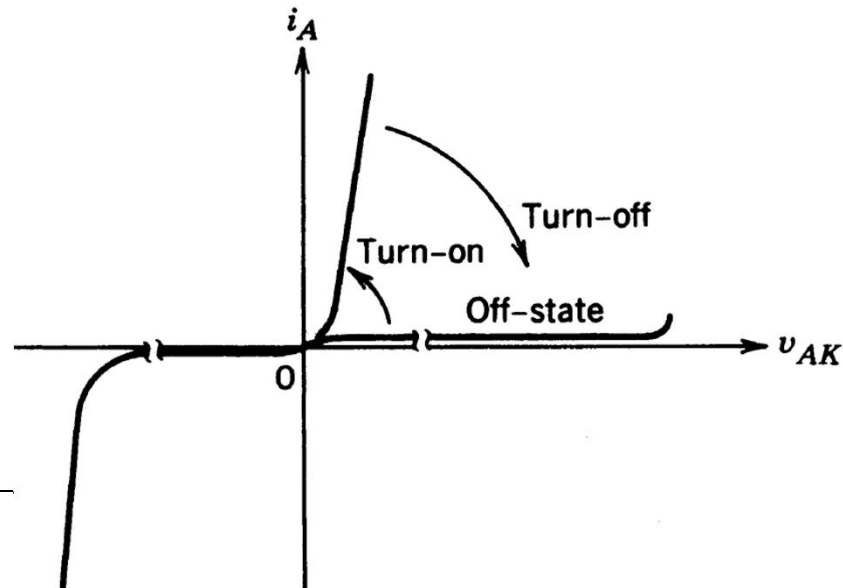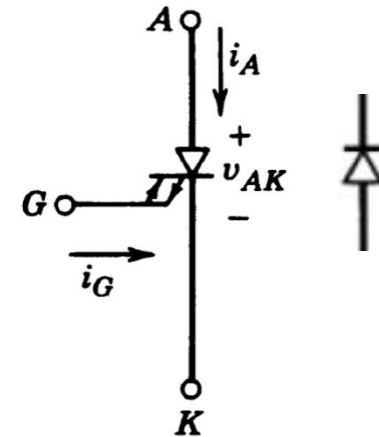- Thyristor possible to turn off
- Slow switch time ($1 \mu\text{s} < t_{\text{off}} < 25 \mu\text{s}$)
- High voltage and currents
 - 4.5 kV, 2-3 kA
- Combined with anti-parallel diode



Gate-turn-off Thyristor

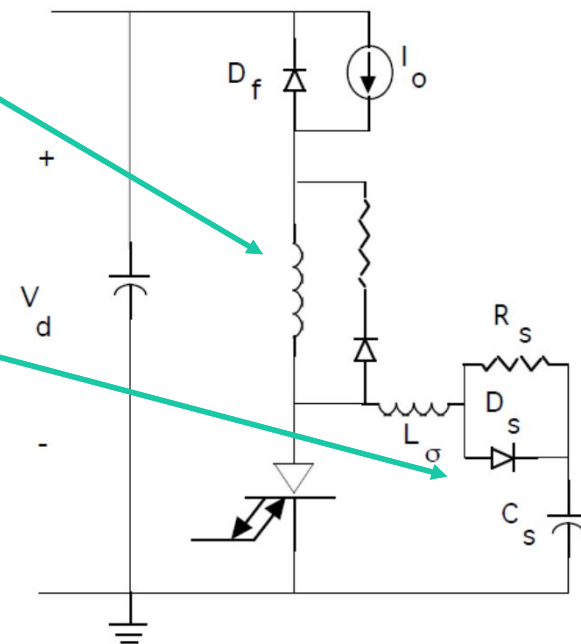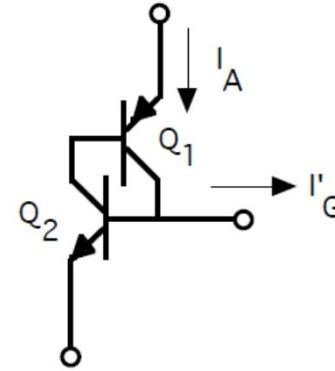
- High gate current required at turn-off. $I_G \approx I_A$.
- Turn-on inductor required to limit di/dt
- Turn-off snubber required to limit over-voltage related to stored energy in the turn-on inductor



Controllable switch comparison

<i>Device</i>	<i>Power Capability</i>	<i>Switching Speed</i>
BJT/MD	Medium	Medium
MOSFET	Low	Fast
GTO	High	Slow
IGBT	Medium	Medium

Controllable switch comparison, cont.

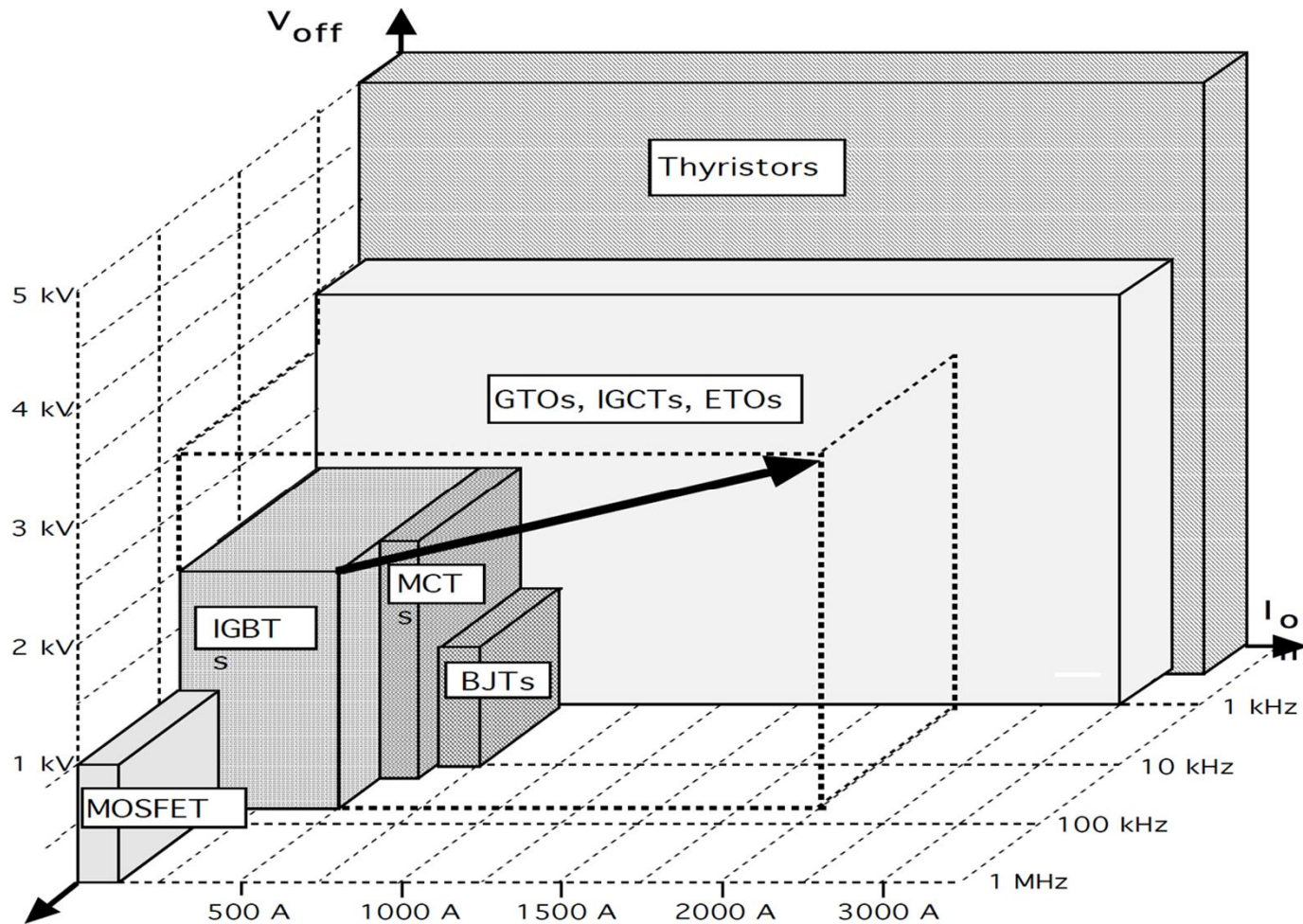

Cooling requirement motivation

- Component failure rate increase with temperature increase
- Components degrade/fail rate increase due to high temperature
- Capacitors
 - Electrolyte evaporate reate increase with temperature
- Magnetic components
 - Losses in magnetic components increase when $T > 100$ degrees
 - Winding insulation degrades when $T > 100$ degrees
- Semiconductors
 - Breakdown voltage decrease
 - Leakage current and switching time increases
 - Power sharing problems when parallel or serial devices



Electric analogy model

- Voltage corresponds to temperature, current corresponds to power, R_{Θ} (or R_{th}) corresponds to power conductivity resistance

$$R_{\Theta,cond} = \frac{\Delta T}{P_{cond}} [K/W]$$

Multiple layer structure model

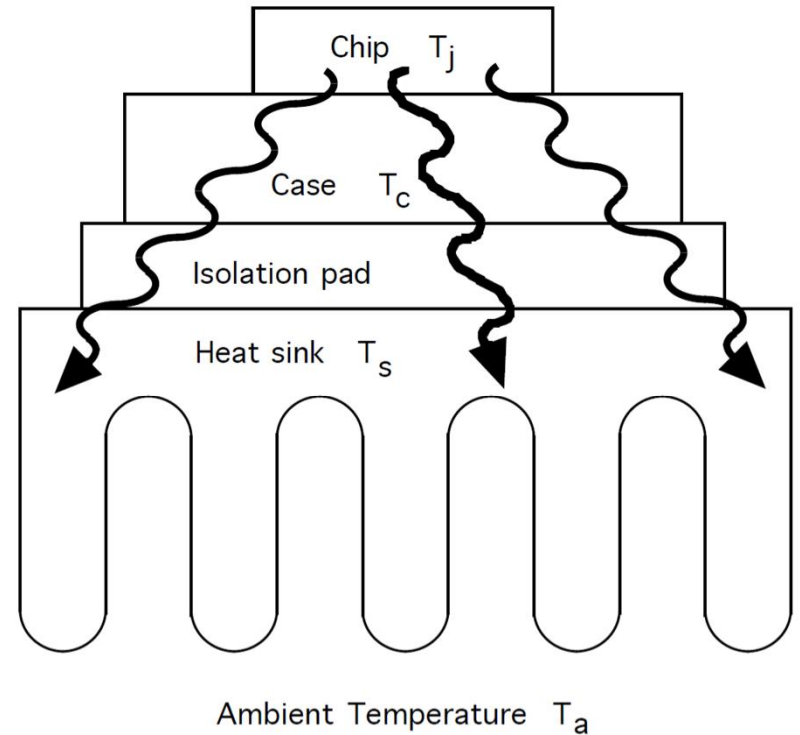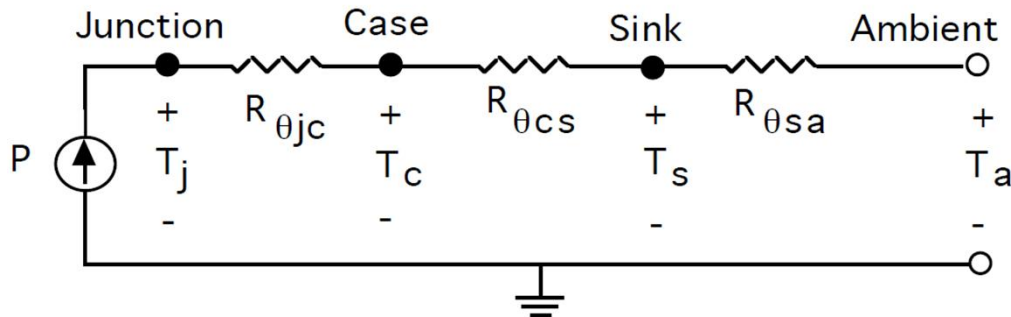- Typical cooling setup
 - Different sizes and materials
- Electric model of the power transfer from power source to the environment



Transient thermal impedance

- Short increase in power dissipation may not lead to overtemperature...

- Heat capacity per unit volume C_v

- Heat energy density Q




$$C_v = \partial Q / \partial T$$

- Volume V

$$C_s = C_v V$$

- Corresponding electric model

$$Z_\theta(t) = [T_j(t) - T_a] / P(t)$$

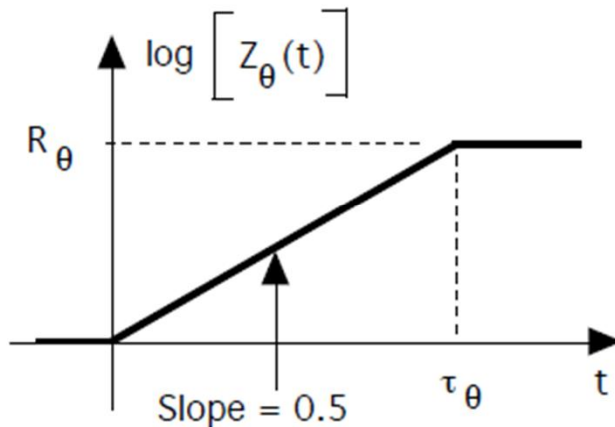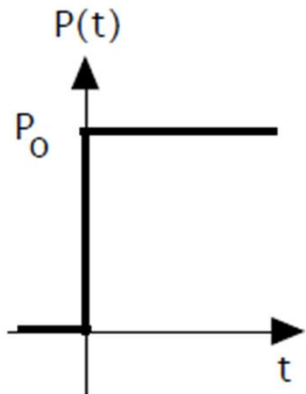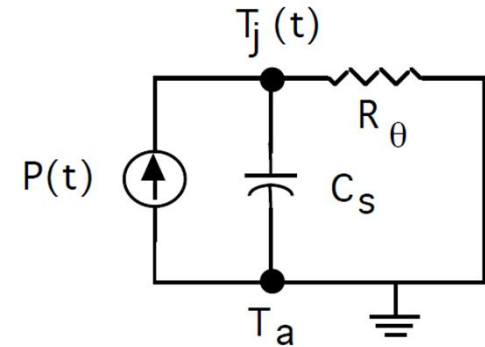


- $\tau_\theta = \pi R_\theta C_s / 4$ = thermal time constant

- $T_j(t = \tau_\theta) = 0.833 P_o R_\theta$

Transient thermal example

- Short pulse, power increase by P_0

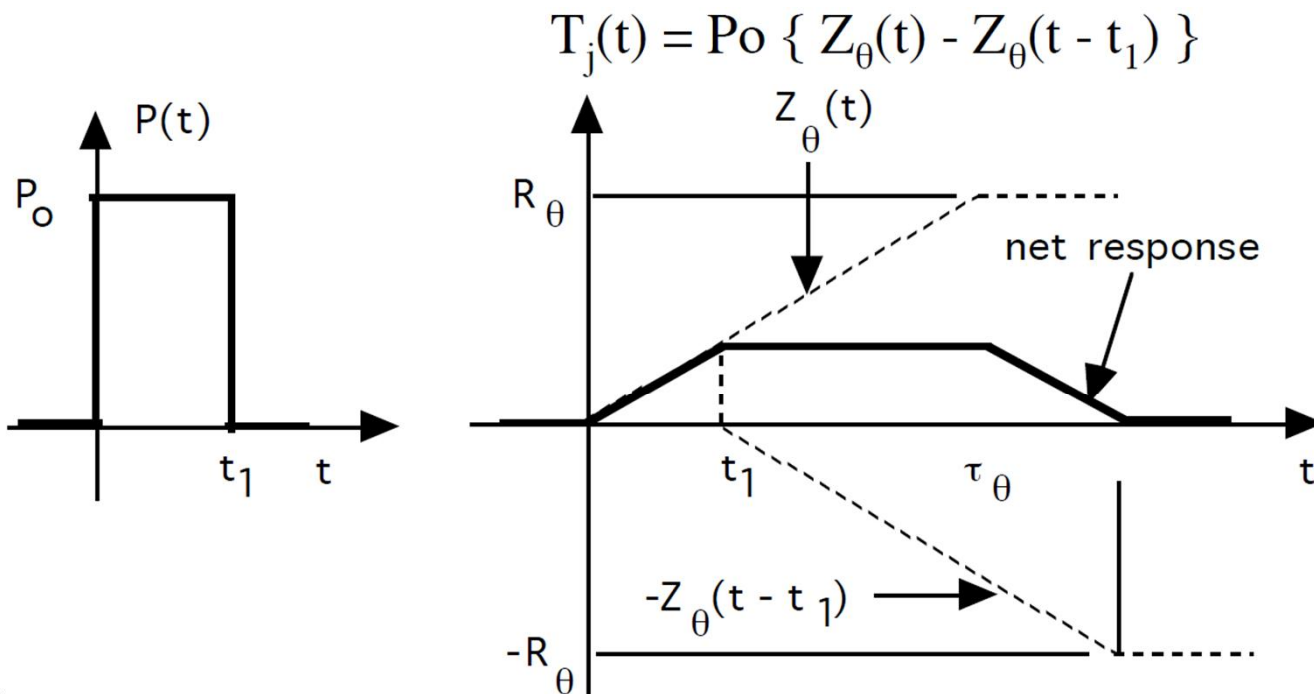


Heat sinks

- Different shapes and material
- Based on convection and radiation
 - Natural convection
 - Forced-air convection
- Examples: Computers, trains,



Other cooling approaches

- Liquid cooling
 - Allow larger heatsinks, placed away from power source
- Thermal towers, heatpipes
 - Similar principle as in a refrigerator (phase shifting)
 - Connect a larger heatsink without large thermal resistance
- Liquid nitrogen
 - Force temperature down below T_a
 - Expensive
 - Water condensation problems
 - Material stress problems

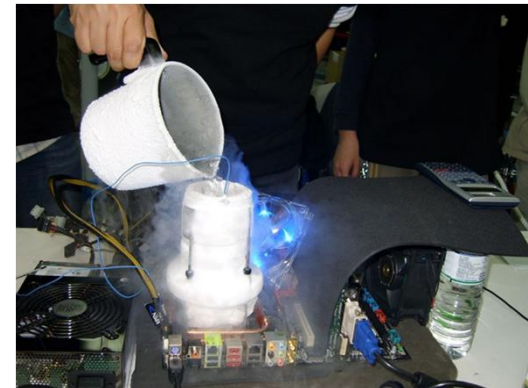

Lecture 5

Exercises

29-6

- A MOSFET used in a step-down converter has an on-state loss of 50 W and a switching loss given by $10^{-3} f_s$ (in watts) where f_s is the switching frequency in hertz.
- The junction-to-case thermal resistance $R_{th,jc}$ is 1 K/W and the maximum junction temperature $T_{j,max}$ is 150°C.
- Assuming the case temperature is 50°C, estimate the maximum allowable switching frequency.

29-7

- The MOSFET of Problem 29-6 is mounted on a heat sink and the ambient temperature $T_a = 35^\circ\text{C}$.
- If the switching frequency is 25 kHz, what is the maximum allowable value of the case-to-ambient thermal resistance $R_{th,ca}$ of the heat sink.
- Assume all other parameters given in Problem 29-6 remain the same except the case temperature which can change.

www.liu.se