


TSTE19

Power Electronics

Examination (TEN1)


Time:	Thursday 12 April 2012 at 8.00 - 12.00
Place:	U10
Responsible teacher:	Kent Palmkvist, ISY, 28 13 47, 0705 23 31 59 (kentp@isy.liu.se) Will visit exam location at 9 and 11.
Number of tasks:	5
Number of pages:	4
Allowed aids:	Calculator
Notes:	A pass on the exam requires approximately 30 points. Remember to indicate the steps taken when solving problems.
Exam presentation:	Thursday 26 April 2012 11.00-13.00 (Kent Palmkvist's office)

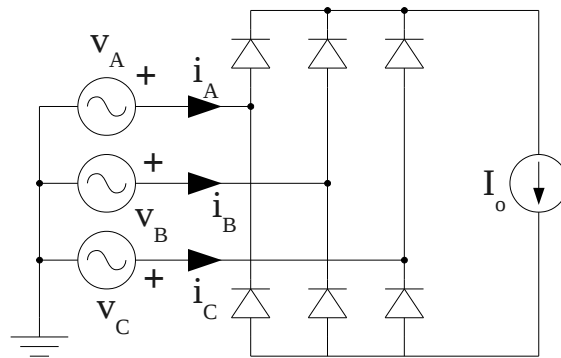1. a) Why do an increase of the switching frequency in a step-down converter make it possible to use an inductor with smaller physical size? (2)
- b) Is the speed of the synchronous motor dependent on the voltage or frequency of the driving voltage? (2)
- c) Can the fundamental component of a signal be larger than the peak value? Motivate your answer. (2)
- d) What does the acronym IGBT stand for? (2)
- e) Does the Cúk dc-dc converter produce a positive or negative voltage? (2)




2. The 3-phase AC->DC converter above have load I_o of 10 A. Assume the diodes are ideal. The AC input voltages v_A , v_B and v_C are 240V rms, with a 50 Hz fundamental frequency.
 - a) Draw the waveforms of $v_A(t)$ and $i_A(t)$. Indicate angles/time and voltages/currents. (6)
 - b) Calculate the amplitude of the 1st and 2nd harmonic of the current $i_A(t)$. (6)

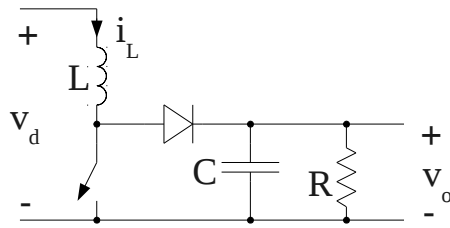3. An AC-DC converter consists of 4 thyristors. These are mounted onto one common heat sink. The input voltage is 400V rms, input current 4 A rms, output voltage is 250V, output current 6 A. The ambient temperature can reach a maximum of 50 degrees. The thermal resistance between junction and case is 2 °C/W, and the case to ambient thermal resistance is 0.8 °C/W. Assume all power loss occur in the thyristors and are equally distributed between them.
 - a) What is the efficiency of the converter? (4)
 - b) What is the switch utilization ratio? (6)
 - c) What is the maximum temperature in the junction of the thyristors? (6)



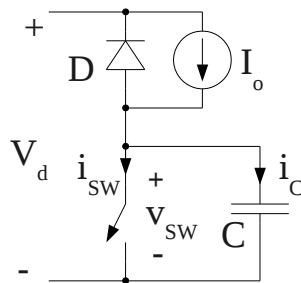4. The step-up (boost) converter above is working in the continuous conduction mode. The switching rate $D = 0.75$, input voltage $V_d = 12 \text{ V}$. C is large, $R = 80 \Omega$, and $L = 50 \mu\text{H}$. The switching frequency is 50 kHz .

- Calculate the output voltage v_o . (6)
- Draw the waveform for $i_L(t)$ and indicate when the switch is on and off. (6)
- Calculate the maximum current through the inductor L . (4)



5. The circuit above describes a turn-off snubber consisting of the capacitance C . The flywheel diode D have a reverse recovery time of $0.2 \mu\text{s}$, The input voltage V_d is 380V , and the current I_o is 10 A . The switch have a turn-off time of $0.5 \mu\text{s}$ (linear current decrease), and a turn-on time of $0.5 \mu\text{s}$ (linear current increase). The voltage across the snubber capacitance should reach the input voltage after the same time as the switch current reaches zero.


- Draw the waveforms of i_c , i_{sw} , and v_{sw} at the switch turn-off. (4)
- Draw the waveforms of i_c , i_{sw} , and v_{sw} at the switch turn-on. (6)
- Compute the peak value of i_{sw} at switch turn-on. (6)

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry, Table 3.1

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	
		$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h	
		$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$a_h = 0$ for even h	
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	
		$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
		$b_h = 0$ for even h	

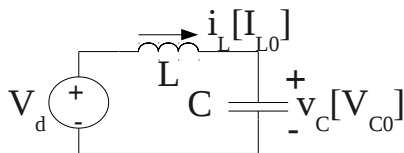
Undamped series resonant circuit, equations 9-3, 9-4



$$i_L(t) = I_{L0} \cos \omega_0(t - t_0) + \frac{V_d - V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-3)$$

$$v_C(t) = V_d - (V_d - V_{C0}) \cos \omega(t - t_0) + Z_0 I_{L0} \sin \omega_0(t - t_0) \quad (9-4)$$

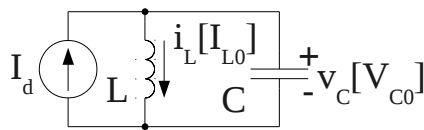Undamped parallel resonant circuit, equations 9-20, 9-21



$$i_L(t) = I_d + (I_{L0} - I_d) \cos \omega_0(t - t_0) + \frac{V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-20)$$

$$v_C(t) = Z_0 (I_d - I_{L0}) \sin \omega(t - t_0) + V_{C0} \cos \omega_0(t - t_0) \quad (9-21)$$

Integration rules

$$\int_a^b f(ax) dx = \int_A^B f(g(t)) g'(t) dt \quad \text{if } a = g(A) \text{ and } b = g(B)$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$