

Today's topic


Application Specific Integrated Circuits for Digital Signal Processing Lecture 5

Oscar Gustafsson

- ▶ Computation graphs
- ▶ Latency and execution time
- ▶ Iteration period bound and critical path
- ▶ Pipelining and retiming
- ▶ Algorithm transformations
- ▶ Unfolding


Computation graphs

 - ▶ Precedence graphs only consider the order of operations, not the actual time it takes to finish an operation



Computation graphs

 
- ▶ Introduce time to get a *computation graph*



- ▶ The time may be different for different operations

Shimming delay

 - ▶ When input data to an operation is available at different times *shimming delays* are needed



- ▶ Note that we want to reuse the operators, so keeping the value at the output is not an option

Relation latency and execution time?

- ▶ Is it possible to say anything about the relation between latency and execution time?


$T_L > T_{\text{exe}}$	$T_L = T_{\text{exe}}$	$T_L < T_{\text{exe}}$
Pipelined combinatorial	Combinatorial	Serial
Several clock cycles	No clock cycle	No or a few clock cycles

Latency and execution time

- ▶ Two time measures of interest
 - ▶ Time from input of sample to output of sample
 - ▶ Time between input sample and input of next sample
- ▶ Latency
 - ▶ Time to produce an output from the corresponding input
 - ▶ Denoted T_L
 - ▶ Of interest when determining the timing between operations
- ▶ Execution time
 - ▶ Time between successive input samples
 - ▶ Denoted T_{exe}
 - ▶ Of interest when we determine how many operators are required
- ▶ Often convenient to express the latency and execution time in number of clock cycles
- ▶ Combinatorial latency adds to the clock period


Serial arithmetic

 - ▶ LSB first
- ▶ Latency of addition: 0 clock cycles ($T_{L,FA}$)



Serial arithmetic

- ▶ Latency of multiplication: W_f clock cycles
 - ▶ Data: $X = \sum_{i=0}^{W_d-1} x_i 2^{-i}$
 - ▶ Coefficient: $\alpha = \sum_{j=0}^{W_f} a_j 2^{-j}$
 - ▶ Result: $Y = X\alpha = \sum_{i=0}^{W_d-1} x_i 2^{-i} \sum_{j=0}^{W_f} a_j 2^{-j} = \sum_{k=0}^{W_f+W_d-1} y_k 2^{-k}$
 - ▶ First bit at the output of multiplier has weight $W_f + W_d - 1$
 - ▶ First bit of interest is of weight $W_d - 1$
 - ▶ Have to wait for W_f clock cycles (bits)

 

Iteration period bound


- ▶ Time for one iteration limited by recursive parts
- ▶ All computations in a loop must finish before the next iteration can start
- ▶ Iteration period bound, T_{∞} , (minimum sample period, T_{min})

$$T_{\infty} = \max_i \frac{\sum_{\text{Op. in loop } i} T_{L,k}}{N_i} = \frac{1}{f_{\max}} \quad (2)$$

- where N_i is the number of delay elements in loop i
- ▶ Processing K samples per iteration, the minimum sample period is $T_{min} = T_{\infty}/K$
- ▶ The loop that determines the sample period is called *critical loop*
- ▶ Theoretical bound that puts a limit on how fast the algorithm can be run
- ▶ Not always straightforward to find an implementation that runs as fast

Critical path

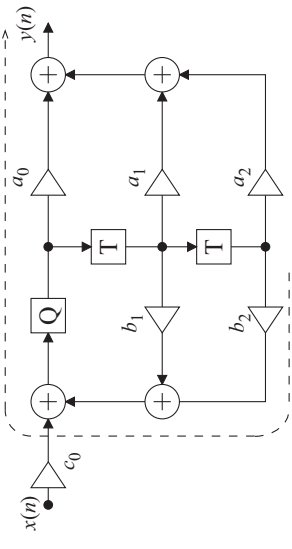
- ▶ Longest time directed path is critical path
- ▶ T_{cp} = time of critical path




$$T_{cp} = 3T_{L,add} + T_{L,Q} + T_{L,mult_{b_2}} + T_{L,mult_{a_0}} \quad (1)$$

Maximum sample rate – example

- ▶ SFG below has two loops

 

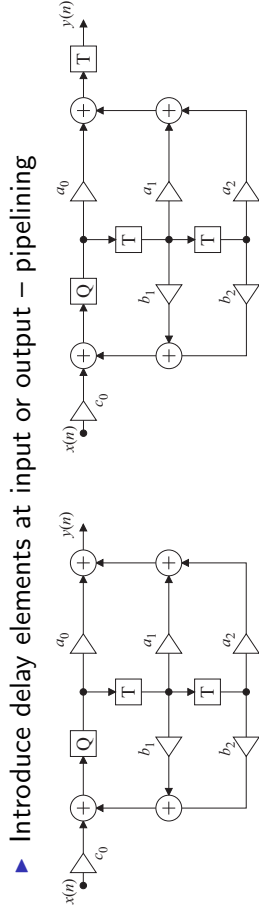
$$T_{min} = \max \left\{ \underbrace{T_{L,add} + T_{L,Q} + T_{L,mult_{b_1}}}_{1 \text{ Loop}_1}, \underbrace{2T_{L,add} + T_{L,Q} + T_{L,mult_{b_2}}}_{2 \text{ Loop}_2} \right\} \quad (3)$$



- ▶ Introduce delay elements at input or output – pipelining


- ▶ Changes the latency of the algorithm

 


- ▶ Move delay elements – retiming

- ▶ Must have delay elements on all inputs (outputs) to move to outputs (inputs)

- ▶ May change critical path

 

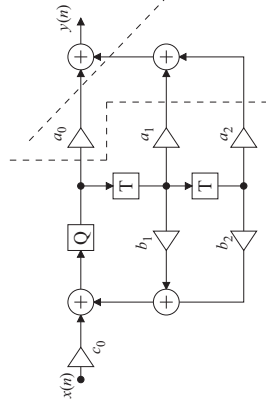- ▶ Find a cut such that all signals go in the same direction




- ▶ May NOT change the iteration period bound
- ▶ Never possible to move delay elements into/out of a loop

- ▶ Possible to add an arbitrary number of delay elements at the cut

Cut-set retiming

 
- ▶ A cut where signals go in opposite directions



- ▶ Possible to move an arbitrary number of delay elements from one direction to the other
- ▶ Must move the same number of delay elements from all signals going in one direction

Cut-set retiming

 - ▶ May accidentally introduce pipelining (delay elements between the input and the output)





Maximum sample rate – some important notes

- ▶ Recursive algorithms have a bound on achievable sample rate caused by the loops
- ▶ Loops can never be pipelined
- ▶ Non-recursive (parts of) algorithms can always be pipelined
- ▶ No upper bound on achievable sample rate for non-recursive algorithms

Algorithm transformations

  - ▶ Still some opportunities to modify the algorithm to, e.g., possibly reduce the sample period
- ▶ Associativity: $(x + y) + z = x + (y + z)$
- ▶ Commutativity: $ab = ba$
- ▶ Distributivity: $a(x + y) = ax + ay$




Algorithm transformations


- ▶ Possible to obtain one loop with one multiplication and one addition
- ▶ May increase operations in other loops
- ▶ Ignores finite-wordlength effects
 - ▶ Merging multiplications leads to longer coefficient wordlength
 - ▶ Re-quantizing the coefficient may lead to an incorrect algorithm

Algorithm transformations – example

- ▶ Initial algorithm

 


- ▶ Move addition out of loop

 


Algorithm transformations – example

- ▶ Propagate multiplication with b

 


- ▶ Merge multiplications

 

Timing in non-time-multiplexed architectures

 
- ▶ For architectures where no time-multiplexing of operators is used, it is still important to introduce shimming delays when the operators have a non-zero clock cycle latency
- ▶ Introduce registers/flip-flops to synchronize the signals taking the latency of the operations into consideration
- ▶ Example – bit-serial second-order birectiprocal LWDF allpass section



- ▶ Use pipelining register after each operation to increase clock frequency
 - ▶ $T_{L,add} = 1$ clock cycle
 - ▶ $T_{L,mult} = 9$ clock cycles
- ▶ Sample time of 21 clock cycles

Timing in non-time-multiplexed architectures

 
- ▶ Replace delay elements with 21 registers/flip-flops




- ▶ Each operation needs a number of registers corresponding to the latency
- ▶ Move negation to avoid an additional operator

Timing in non-time-multiplexed architectures

 - ▶ Move one register into the first adder (marked with white)




 - ▶ Move nine registers into the multiplier



Timing in non-time-multiplexed architectures

 
- ▶ Replace delay elements with 21 registers/flip-flops




- ▶ Each operation needs a number of registers corresponding to the latency
- ▶ Move negation to avoid an additional operator

Timing in non-time-multiplexed architectures

 - ▶ Move one register into the final adders




- ▶ Final realization

 

- ▶ All loops should have a latency that is an integer multiple of the sample period
- ▶ All paths from input to output should have a latency that is an integer multiple of the sample period (plus some constant)

Unfolding

 
- ▶ Express algorithm over several sample periods



- ▶ Increase probability of applying algorithm transformations
- ▶ Express multi-rate algorithms as single-rate


Unfolding – motivational example 1

- ▶ Consider a simple accumulator

 

$$T_{min} = \frac{T_{L,add}}{1} \quad (4)$$

 - ▶ Express accumulator over two sample periods




$$T_{min} = \frac{2T_{L,add}}{1} \quad (5)$$

but computing two samples per iteration

Unfolding – motivational example 1


- ▶ Re-order additions

 

$$T_{min} = \frac{T_{L,add}}{1} \quad (6)$$


still computing two samples per iteration

- ▶ Non-recursive parts can be pipelined

 


Unfolding – motivational example 2

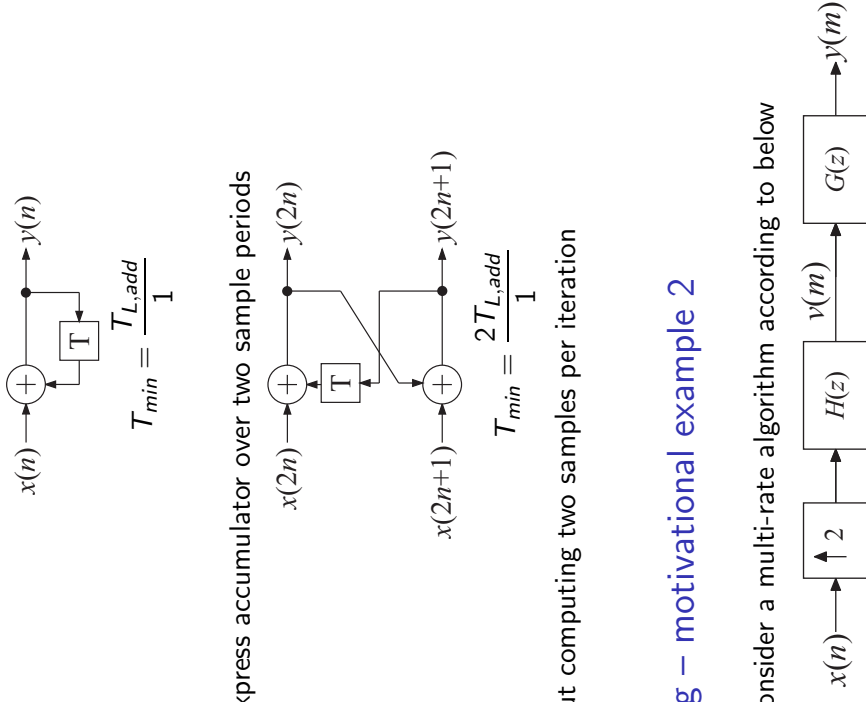
- ▶ Consider a multi-rate algorithm according to below



 - ▶ $H(z)$ can be poly-phase decomposed but $G(z)$ can not




 - ▶ Unfold $G(z)$ and obtain a single-rate formulation




Unfolding – derivation

 
- ▶ Consider an algorithm separated in operations, N , and delay element




 - ▶ In the next iteration the sample indices are as follows



Unfolding – derivation

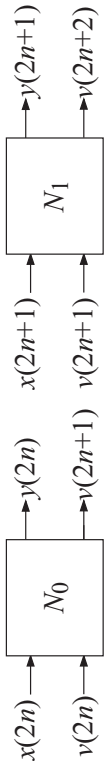 - ▶ Looking at two iterations, the following samples are used
 
- ▶ One iteration updates the indices a factor of two
- ▶ Connect according to indices



Unfolding – systematic equations


- ▶ Unfolding with aq factor M can be performed systematically as follows
 - ▶ There are M computational blocks, denoted $N_i, i = 0, 1, 2, \dots, M - 1$
 - ▶ The input and output to block N_i are $x(Mn + i)$ and $y(Mn + i)$, respectively
 - ▶ An internal state from block N_i with L delay elements is connected to block N_j with K delay elements where

$$j = (i + L) \bmod M \quad (7)$$

and

$$K = \left\lfloor \frac{i + L}{M} \right\rfloor \quad (8)$$

Unfolding – example 1

 


Unfolding – example 1

- ▶ Compute connections


i	L	j	K
0	1	$(0 + 1) \bmod 3 = 1$	$\frac{0+1}{3} = 0$
0	2	$(0 + 2) \bmod 3 = 2$	$\frac{0+2}{3} = 0$
0	4	$(0 + 4) \bmod 3 = 1$	$\frac{0+4}{3} = 1$
1	1	2	0
1	2	0	1
1	4	2	1
2	1	0	1
2	2	1	1
2	4	0	2

Unfolding – example 1

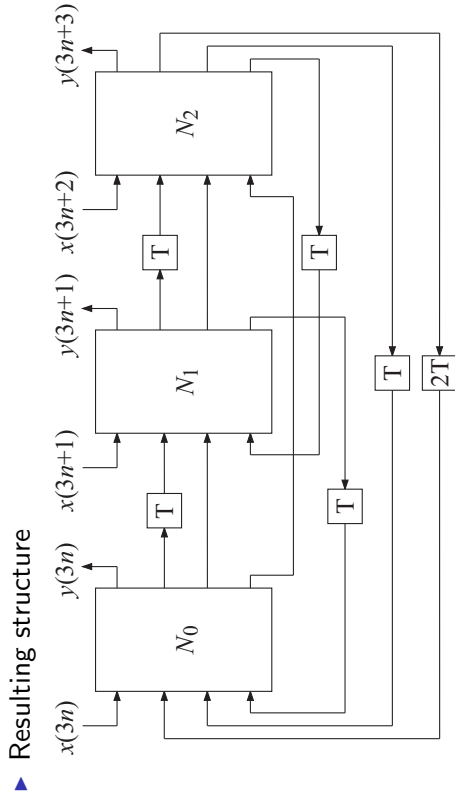


Unfolding – example 2

 - ▶ Unfold first-order WDF allpass structure a factor $M = 2$
- ▶ Two copies



Unfolding – example 2

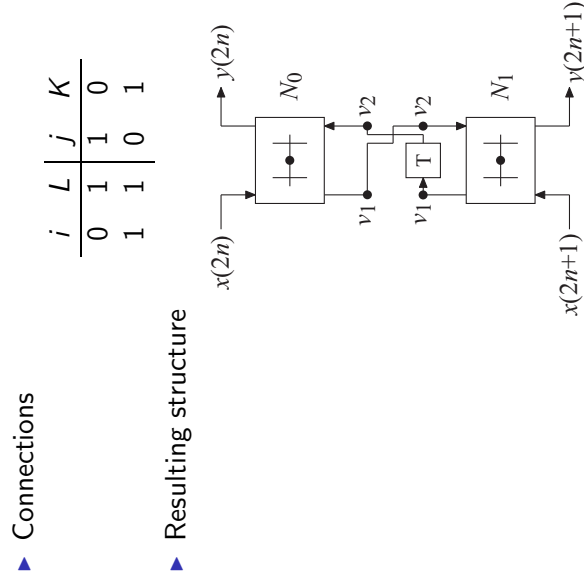

Unfolding and iteration period bound

- ▶ What happens to the iteration period bound?
- ▶ Every loop have M times more operations or M times fewer delay elements \rightarrow iteration period bound increases a factor of M
- ▶ Process M samples per iteration
- ▶ Resulting minimal sample rate is the same
- ▶ Unfolding does not affect the parallelism of a recursive algorithms
 - ▶ More operations may lead to better algorithm transformations
 - ▶ May increase the resource utilization (next lectures)