

## Today's topics

### Application Specific Integrated Circuits for Digital Signal Processing Lecture 9

Oscar Gustafsson

- ▶ Number representations
- ▶ Addition

(If you enjoy this lecture and the next,  
take the TSTE18 Digital Arithmetic course)

## Number representations

- ▶ The number representation defines both the arithmetic operations and numerical properties
- ▶ Fixed-point arithmetic has been dominating for a long time because of the less complex operations
- ▶ Floating-point arithmetic is gaining ground, especially for numerically troublesome applications such as MIMO detection
- ▶ Non-traditional number representations such as logarithmic number systems and residue number systems are advantageous in certain applications (more on next lecture)
- ▶ We will primarily focus on fractional numbers, but most of the time this is just a matter of indexes

## Number representations

- ▶ A  $W$  fractional digits radix- $r$  positive fractional number,  $0 \leq X < 1$ , is written as

$$X = \sum_{i=1}^W x_i r^{-i} \quad (1)$$

where  $x_i \in \{0, 1, \dots, r-1\}$

- ▶ For most cases we assume  $r = 2$ , i. e., a binary representation, which gives

$$X = \sum_{i=1}^W x_i 2^{-i} \quad (2)$$

where  $x_i \in \{0, 1\}$  are binary digits, i. e., bits

- ▶ Define the weight of the least significant bit as  $Q = 2^{-W}$

## Binary addition

- ▶ Add the two binary numbers

$$X = \sum_{i=1}^W x_i 2^{-i} \text{ and } Y = \sum_{i=1}^W y_i 2^{-i} \quad (3)$$

- ▶ The result can be written as

$$S = c_0 + \sum_{i=1}^W s_i 2^{-i} \quad (4)$$

where

$$s_i = x_i \oplus y_i \oplus c_i$$


and

$$c_{i-1} = \text{majority}(x_i, y_i, c_i) = x_i y_i + y_i c_i + x_i c_i$$


with  $c_W = 0$
 
## Binary addition

- ▶ These equations are often realized with a *full adder* cell employing three inputs,  $x_i$ ,  $y_i$ , and  $c_i$ , and two outputs,  $s_i$  and  $c_{i-1}$



 - ▶ Several full adders are connected to form a ripple carry adder



- ▶ Gate delay proportional to the number of bits

## Negative numbers

- ▶ Easy to represent positive numbers, but what about negative?
- ▶ Representing negative numbers are required for typical DSP applications, although sometimes one can just offset the signals
- ▶ Subtraction can be written and computed as  $X - Y = X + (-Y)$
- ▶ To illustrate the different number representations we will consider the following properties and operations
  - ▶ Representation and numerical range
  - ▶ Increasing the number of bits on the least significant side (left shift) and on the most significant side (right shift/sign-extension)
  - ▶ Negation
  - ▶ Addition/subtraction
  - ▶ Multiplication
- ▶ Assume one more bit compared to before to represent the sign

## Sign-magnitude

- ▶ Use one bit to represent the sign and the rest of the bits for the magnitude

$$X = (1 - 2x_0) \sum_{i=1}^W x_i 2^{-i} = (-1)^{x_0} \sum_{i=1}^W x_i 2^{-i} \quad (5)$$

- ▶ Numerical range  $-1 + Q \leq X \leq 1 - Q$
- ▶ Examples
  - ▶  $0 = 0.000$  or  $1.000$
  - ▶  $\frac{5}{8} = 0.101$
  - ▶  $-\frac{5}{8} = 1.101$
- ▶ Increasing wordlength on MSB side (sign extend)/right shift
  - ▶ Add zeros after sign bit
  - ▶  $\frac{5}{8} = 00.101$
  - ▶  $-\frac{5}{8} = 10.101$
  - ▶  $\frac{5}{16} = 0.0101$
  - ▶  $-\frac{5}{16} = 1.0101$

## Sign-magnitude

- ▶ Increasing wordlength on LSB side/left shift
  - ▶ Add zeros after the LSB
  - ▶  $\frac{5}{8} = 0.1010$
  - ▶  $\frac{5}{8} = 1.1010$
  - ▶  $\frac{5}{4} = 01.010$
  - ▶  $-\frac{5}{4} = 11.010$
- ▶ Negation
  - ▶ Invert sign-bit
- ▶ Addition/subtraction
  - ▶ Complicated, must determine which one is the largest in relation to the sign and operation to be performed
- ▶ Multiplication
  - ▶ Unsigned multiplication of magnitudes, xor of sign-bits

## One's complement

- ▶ Negate by inverting all bits

$$X = -x_0(1 - 2^{-W}) + \sum_{i=1}^W x_i 2^{-i} \quad (6)$$

- ▶ Numerical range  $-1 + Q \leq X \leq 1 - Q$
- ▶ Examples
  - ▶  $0 = 0.000$  or  $1.111$
  - ▶  $\frac{5}{8} = 0.101$
  - ▶  $-\frac{5}{8} = 1.010$
- ▶ Increasing wordlength on MSB side (sign extend)/right shift
  - ▶ Add sign-bit before the MSB
  - ▶  $\frac{5}{2} = 00.101$
  - ▶  $-\frac{5}{2} = 11.010$
  - ▶  $\frac{5}{10} = 0.0101$
  - ▶  $-\frac{5}{10} = 1.1010$

## One's complement

- ▶ Increasing wordlength on LSB side/left shift
  - ▶ Add sign-bit after the LSB
  - ▶  $\frac{5}{8} = 0.1010$
  - ▶  $-\frac{5}{8} = 1.0101$
  - ▶  $\frac{5}{4} = 01.010$
  - ▶  $-\frac{5}{4} = 10.101$
- ▶ Negation
  - ▶ Invert all bits
- ▶ Addition/subtraction
  - ▶ Perform normal binary addition, then add the carry output  $c_{-1}$  to the carry input  $c_W$
  - ▶ End-around carry
  - ▶ Example:
 
$$\underbrace{0.10}_{\frac{1}{2}} + \underbrace{1.10}_{-\frac{1}{2}} = \underbrace{1}_{c_{-1}} \underbrace{0.00}_{c_W=c_{-1}} + \underbrace{0.01}_{\frac{1}{4}} = \underbrace{0.01}_{\frac{1}{4}} \quad (7)$$

- ▶ Multiplication
  - ▶ Complicated handling of sign-bits on both LSB and MSB side

## Two's complement

$$X = -x_0 + \sum_{i=1}^W x_i 2^{-i} \quad (8)$$

- ▶ Numerical range  $-1 \leq X \leq 1 - Q$
- ▶ Examples
  - ▶  $0 = 0.000$
  - ▶  $\frac{5}{8} = 0.101$
  - ▶  $-\frac{5}{8} = 1.011$
- ▶ Increasing wordlength on MSB side (sign extend)/right shift
  - ▶ Add sign-bit before the MSB
  - ▶  $\frac{5}{2} = 00.101$
  - ▶  $-\frac{5}{2} = 11.011$
  - ▶  $\frac{5}{10} = 0.0101$
  - ▶  $-\frac{5}{10} = 1.1011$

## Two's complement

- ▶ Increasing wordlength on LSB side/left shift
- ▶ Add zeros after the LSB
- ▶  $\frac{5}{8} = 0.1010$
- ▶  $-\frac{5}{8} = 1.0110$
- ▶  $\frac{5}{4} = 01.010$
- ▶  $-\frac{5}{4} = 10.110$
- ▶ Negation
  - ▶ Invert all bits and add one at the LSB position
- ▶ Addition/subtraction
  - ▶ Normal binary addition
  - ▶ Example:

$$\underbrace{0.10}_{\frac{1}{2}} + \underbrace{1.11}_{-\frac{1}{4}} = \underbrace{1.01}_{\frac{1}{4}} \quad (9)$$

- ▶ For subtraction there is no need to evaluate the negation explicitly, instead the additional one can be added at the  $c_W$  input of the adder
- ▶ Multiplication
  - ▶ Complicated handling of sign-bits on MSB side

## Signed-digit (SD) representation

- ▶ Allow each “bit” to be signed, i.e.,  $x_i \in \{-1, 0, 1\}$

$$X = \sum_{i=1}^W x_i r^{-i} \quad (10)$$

- ▶ Numerical range  $-1 + Q \leq X \leq 1 - Q$
- ▶ The “bit” is a ternary digit, sometimes called trit
- ▶ Require two bits to represent but there are other advantages
- ▶ Several representations of many numbers (denote  $-1$  as  $\bar{1}$ )
  - ▶ Example:  $\frac{5}{8} = 0.101 = 1.\bar{1}01 = 1.\bar{1}\bar{1}\bar{1} = 1.0\bar{1}\bar{1}$
  - ▶ Redundant number system
- ▶ Main benefit: addition/subtraction can be made without carry-propagation

## Number representations

- ▶ Two's complement is the commonly used representation
  - ▶ Also has the benefit of adding numbers in arbitrary order as discussed earlier
- ▶ Two's complement has one “major” issue to consider
  - ▶ Multiplying  $-1$  with  $-1$  leads to  $1$  which is out of range
  - ▶ Will have to decide if an additional integer bit should be added for this specific case or if one detects it and use saturation to  $1 - Q$
- ▶ Sign-magnitude has benefits in terms of switching activity
  - ▶ Consider a value changing from  $Q$  to  $0$  to  $-Q$ 
    - ▶ Sign-magnitude:  $0.000 \dots 001 \rightarrow 0.000 \dots 000 \rightarrow 1.000 \dots 001$
    - ▶ Two's complement:  $0.000 \dots 001 \rightarrow 0.000 \dots 000 \rightarrow 1.111 \dots 111$
  - ▶ This is the typical case for many “silent” signals, only some noise
  - ▶ Can be utilized e.g. by having one accumulator for negative numbers and one for positive

## Signed-digit number systems

- ▶ Conversion from two's complement to signed-digit
  - ▶ Only the sign-bit must be considered
  - ▶ Examples:
    - ▶  $\frac{5}{8} = 0.101_{2C} = 0.101_{SD}$
    - ▶  $-\frac{5}{8} = 1.011_{2C} = \bar{1}.011_{SD}$
- ▶ Conversion from signed-digit to two's complement
  - ▶ Subtract the number formed by the negative digits from that formed by the positive digits
  - ▶ Example:
    - ▶  $\frac{5}{8} = 1.\bar{1}\bar{1}\bar{1}_{SD} = 1.010_2 - 0.101_2 = 1.010 + \underbrace{1.010 + 0.001}_{2C \text{ negation}} = \bar{1}.010_{2C}$

## Minimum signed-digit representation

- ▶ A signed-digit representation with minimum number of non-zero digits is called a minimum signed-digit (MSD) representation
- ▶ In general there are several MSD representations
- ▶ One particular MSD representation can be obtained if we constraint two adjacent digits to not both be non-zero

$$x_i x_{i+1} = 0 \quad (11)$$

- ▶ This particular representation is called canonic signed digit (CSD) representation
- ▶ The CSD representation is unique and therefore not redundant
- ▶ This is useful as a SD representation without adjacent non-zero digits are then known to be minimum

## Minimum signed-digit representation

- ▶ Properties of CSD vs binary

	Binary	CSD
Average non-zero digits	$W/2$	$W/3$
Maximum non-zero digits	$W$	$W/2$

- ▶ Conversion to CSD

- ▶ Convert strings of ones:  $011 \dots 11 \Rightarrow 100 \dots 0\bar{1}$
- ▶ Merge adjacent digits of opposite signs:  $1\bar{1} \Rightarrow 01, \bar{1}1 \Rightarrow 0\bar{1}$

## Minimum signed-digit representation

- ▶ A signed-digit representation with minimum number of non-zero digits is called a minimum signed-digit (MSD) representation
- ▶ In general there are several MSD representations
- ▶ One particular MSD representation can be obtained if we constraint two adjacent digits to not both be non-zero

$$x_i x_{i+1} = 0 \quad (11)$$

- ▶ This particular representation is called canonic signed digit (CSD) representation
- ▶ The CSD representation is unique and therefore not redundant
- ▶ This is useful as a SD representation without adjacent non-zero digits are then known to be minimum

## Carry-save representation


- ▶ Consider a ripple carry adder where the carries are not connected to the next stage
- ▶ Three words can be added and the result is represented using two outputs (carry and sum)
- ▶ Assuming two's complement representation

$$X = S + C = -s_0 + \sum_{i=1}^W s_i 2^{-i} - c_0 + \sum_{i=1}^W c_i 2^{-i} \quad (12)$$

- ▶ Suitable for high-speed realizations as no carry is propagated
- ▶ To detect sign (i.e. hard to compare and detect overflows) a carry propagation is required
- ▶ Can be seen as a signed-digit representation with  $x_i \in \{0, 1, 2, 3\}$  and  $x_i = 2c_i + s_i$
 
## Redundant binary representation

- ▶ An alternative sometimes usable is the redundant binary representation
- ▶ Generalization of carry-save by writing  $x_i = 2c_i + s_i$  as  $x_i = 2c_i - s_i$  or  $x_i = -2c_i + s_i$
- ▶ The first equation can represent  $x_i \in \{-1, 0, 1, 2\}$  so it can add one negative and two positive inputs, while the other can represent  $x_i \in \{-2, -1, 0, 1\}$  and add two negative and one positive
- ▶ Compare with a radix-2 signed digit, which can represent  $x_i \in \{-1, 0, 1\}$ , still two bits are needed for the three values
- ▶ Redundant binary adder with one negative and two positive inputs



## Addition

- ▶ Ripple carry adders are the base line adders
- ▶ Gate delay linear in the word length
- ▶ Example

Value	0	1	2	3	4	5	6	7	Signal
-53/256	1	1	0	0	1	0	1	1	$x_i$
94/256	0	1	0	1	1	1	1	0	$y_i$
41/256	1	1	0	1	1	1	1	0	$c_i$
	0	0	1	0	1	0	0	1	$s_j$

- ▶ Becomes problematic for high-speed implementations
- ▶ Several methods to speed addition up will be covered
- ▶ Focus on parallel prefix addition

## Carry-look ahead addition

- ▶ The carry can either take on a value independent on the carry input or the exact value of the carry input
- ▶ These cases are

$a_i$	$b_i$	$c_{i-1}$	Case
0	0	0	No carry-propagation (kill)
0	1	$c_i$	Carry-propagation (propagate)
1	0	$c_i$	Carry-propagation (propagate)
1	1	1	Carry-generation (generate)

- ▶ We can define propagate,  $p_i$ , and generate,  $g_i$  at bit-level as

$$p_i = a_i \oplus b_i \text{ and } g_i = a_i b_i \quad (13)$$

## Carry-look ahead addition

- ▶ The carry output can then be expressed as

$$c_{i-1} = g_i + p_i c_i \quad (14)$$

- ▶ For the next stage the expression becomes

$$\begin{aligned} c_{i-2} &= g_{i-1} + p_{i-1} c_{i-1} = g_{i-1} + p_{i-1} (g_i + p_i c_i) \\ &= g_{i-1} + p_{i-1} g_i + p_{i-1} p_i c_i \end{aligned} \quad (15)$$

- ▶ For  $N + 1$ :th stage we have

$$\begin{aligned} c_{i-(N+1)} &= g_{i-N} + p_{i-N} g_{i-(N-1)} + p_{i-N} p_{i-N-1} g_{i-(N-2)} + \\ &+ \dots + p_{i-(N-1)} \dots p_{i-1} p_i c_i \end{aligned} \quad (16)$$


## Carry-look ahead addition

- ▶ These terms can be grouped as

$$\begin{aligned} c_{i-(N+1)} &= \underbrace{g_{i-N} + p_{i-N} g_{i-(N-1)} + p_{i-N} p_{i-N-1} g_{i-(N-2)} + \dots +}_{G_{i-N;i}} \\ &+ \underbrace{p_{i-(N-1)} \dots p_{i-1} p_i}_{P_{i-N;i}} c_i \\ &= G_{i-N;i} + P_{i-N;i} c_i \end{aligned}$$

where  $G_{i-N;i}$  is called group generate and  $P_{i-N;i}$  group propagate as they correspond to the generate and propagate signals for the group of bits  $i - N$  to  $i$

 - ▶ The group generate and propagate signals can be computed before the incoming carry is known to speed up the output carry generation



## Parallel prefix addition

- ▶ The carry look-ahead concept can be formalized by introducing the dot operator

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \triangleq \begin{bmatrix} g_i + p_i g_j \\ p_i p_j \end{bmatrix} \quad (17)$$

- ▶ Adders based on dot operators are commonly referred to as parallel prefix adders
- ▶ The group generate and propagate for bits  $k$  to  $l$  can be written as


$$\begin{bmatrix} G_{k:l} \\ P_{k:l} \end{bmatrix} \triangleq \begin{bmatrix} g_k \\ p_k \end{bmatrix} \bullet \begin{bmatrix} g_{k+1} \\ p_{k+1} \end{bmatrix} \bullet \dots \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} \quad (18)$$

## Parallel prefix addition

- ▶ The idempotency leads to the very useful property that overlapping groups do not cause any problems

$$\begin{bmatrix} G_{k:n} \\ P_{k:n} \end{bmatrix} = \begin{bmatrix} G_{k:l} \\ P_{k:l} \end{bmatrix} \bullet \begin{bmatrix} G_{m:n} \\ P_{m:n} \end{bmatrix}, \quad k \leq l, m \leq n, m \leq l - 1. \quad (19)$$

which can be illustrated as below

 

## Parallel prefix addition

- ▶ The dot-operator is associative

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \left( \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \right) \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \left( \begin{bmatrix} g_j \\ p_j \end{bmatrix} \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} \right)$$

- ▶ Idempotent

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_k \\ p_k \end{bmatrix} \bullet \begin{bmatrix} g_k \\ p_k \end{bmatrix}$$

- ▶ But not commutative


$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \neq \begin{bmatrix} g_j \\ p_j \end{bmatrix} \bullet \begin{bmatrix} g_i \\ p_i \end{bmatrix}$$

## Parallel prefix addition

- ▶ The carry signal in position  $k$  can be written as
 
$$c_k = G_{(k+1):l} + P_{(k+1):l}c_l \quad (20)$$
- ▶ Similarly, the sum signal in position  $k$  for an adder using  $W$  fractional bits is then expressed as
 
$$s_k = a_k \oplus b_k \oplus d_k = p_k \oplus (G_{(k+1):W} + P_{(k+1):W}c_{in}) = p_k \oplus c_k \quad (21)$$
- ▶ Of interest to compute all group generate and group propagate originating from the LSB position, i.e.,  $G_{k:W}$  and  $P_{k:W}$  for  $1 \leq k \leq W$ .


## Parallel prefix addition

- ▶ Can be computed sequentially

 
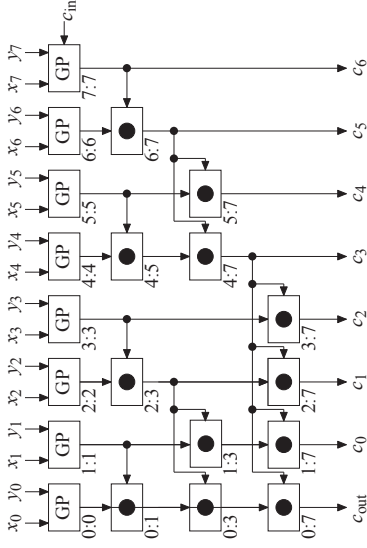
## Parallel prefix addition


- ▶ But we can also use the properties of the dot product and compute it in parallel



- ▶ Many different structures for computing the dot product trees have been proposed trading dot operators, fan-out, wire length, etc.
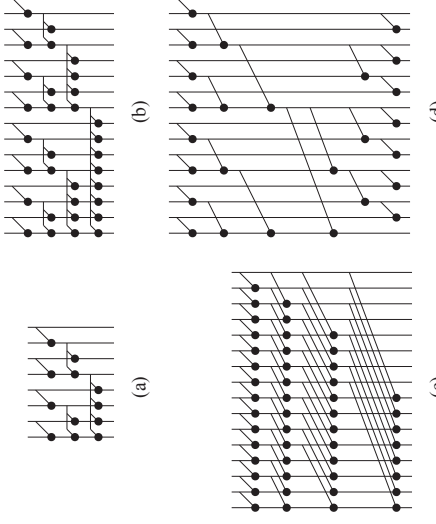
## Parallel prefix addition


- ▶ Often a simplified view is used to represent the dot-products



- ▶ (a) 8-bit Ladner-Fisher (compare previous slide), (b) 16-bit Ladner-Fisher, (c) 16-bit Kogge-Stone, and (d) 16-bit Brent-Kung
 
## Carry-select and conditional sum addition

- ▶ At any stage of the adder, the carry signal is either zero or one(!)
- ▶ Precompute both results and select the correct result once the correct carry arrives
- ▶ Carry-select adder





## Carry-select and conditional sum addition

- ▶ The carry-select adder can of course be separate into several stages
- ▶ Best selection depends on the gate delays of the adders and the multiplexers
- ▶ Each pre-computation adder can in turn be split into a carry-select adder
- ▶ If this is done until the word length of each adder is one a conditional sum adder is obtained

## Summary

- ▶ Binary number representations
  - ▶ Main problem is how to represent negative numbers
  - ▶ Different approaches have different pros and cons
  - ▶ Two's complement mainly used
- ▶ Redundant number representations
  - ▶ Redundant = several possible representations of many numbers
  - ▶ Can avoid carry propagation
  - ▶ Must eventually converted back to non-redundant form which require a carry propagation
  - ▶ Carry-save is easy to use since it relates very much to two's complement
- ▶ Addition
  - ▶ Main problem to mitigate is the lengthy carry propagation
  - ▶ Carry look-ahead/parallel prefix using dot operators
  - ▶ Can reorder and speed up the evaluation at the cost of more dot operators
  - ▶ Carry-select is an intuitive speed giving large speed up at reasonable cost