

Lösningsförslag till tentamen ETE235 Digitalteknik 2013-06-18

1a)

$2013/2$	$=$	1006	REST 1	LSB
$1006/2$	$=$	503	REST 0	
$503/2$	$=$	251	REST 1	
$251/2$	$=$	125	REST 1	
$125/2$	$=$	62	REST 1	
$62/2$	$=$	31	REST 0	
$31/2$	$=$	15	REST 1	
$15/2$	$=$	7	REST 1	
$7/2$	$=$	3	REST 1	
$3/2$	$=$	1	REST 1	↑
$1/2$	$=$	0	REST 1	MSB

$$2013_{10} = 11111011101_2$$

1b)

$$\overbrace{01101010}_2 = 6A_{16}$$

1c)

$$\overbrace{01101010}_2 = 152_8$$

1d)

$$\begin{aligned} 01101010_2 &= 0 \cdot 2^7 + 1 \cdot 2^6 + 1 \cdot 2^5 + 0 \cdot 2^4 + 1 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0 \\ &= 0 + 64 + 32 + 0 + 8 + 0 + 2 + 0 = 106_{10} \end{aligned}$$

1e)

$$106_{10} = 0001\ 0000\ 0110_{NBCD}$$

1f/

$0,71875 \cdot 2$	$=$	$0,4375$	$+ 1$	MSB
$0,4375 \cdot 2$	$=$	$0,875$	$+ 0$	$\downarrow$
$0,875 \cdot 2$	$=$	$0,75$	$+ 1$	
$0,75 \cdot 2$	$=$	$0,5$	$+ 1$	
$0,5 \cdot 2$	$=$	0	$+ 1$	LSB

$$0,71875_{10} = 0,10111_2$$

1g/


10101011	← NEGATIVT TAL ENLIGT TVÅKOMPLEMENT METODEN
- 1	← SUBTRAHERA ETT
10101010	
01010101	← INVERTERA

$$01010101 = +85$$


ALLTSA⁰ 10101011 = -85

ENLIGT TURKOMPLEMENTMETODEN

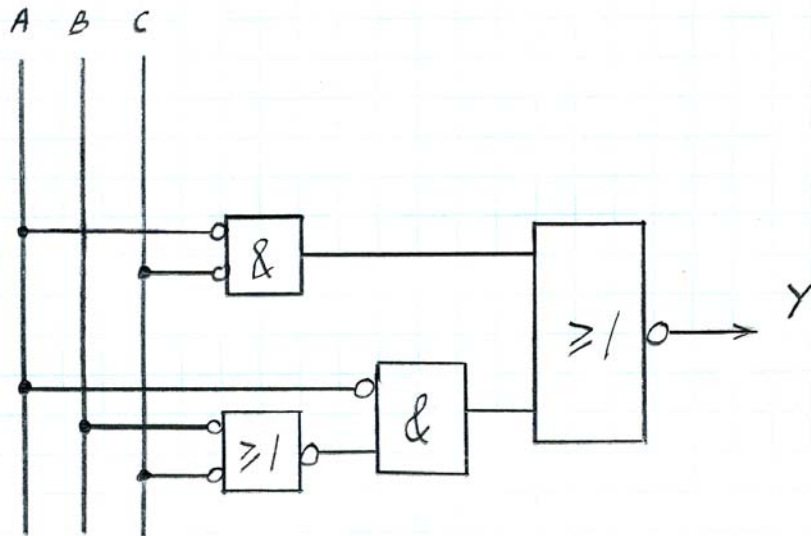2a/ $Y = \overline{\overline{A}\overline{C} + \overline{A}(\overline{B} + \overline{C})}$



2b/
$$\begin{aligned} Y &= \overline{\overline{A}\overline{C} + \overline{A}(\overline{B} + \overline{C})} = \overline{\overline{A}\overline{C} + \overline{A}BC} = \\ &= \overline{\overline{A}\overline{C}} \cdot \overline{\overline{A}BC} = (A + C) \cdot (A + \overline{B} + \overline{C}) = \\ &= AA + A\overline{B} + A\overline{C} + AC + \overline{B}C + C\overline{C} = \\ &= A(1 + \overline{B} + \overline{C} + C) + \overline{B}C = A + \overline{B}C \end{aligned}$$

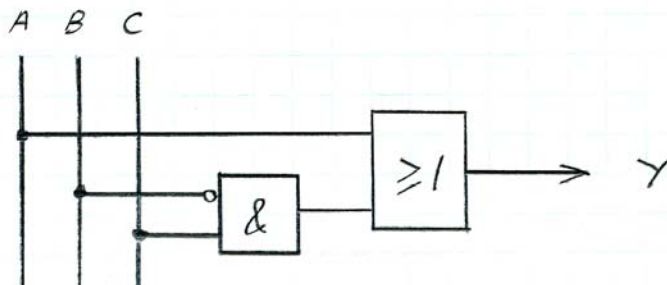


3a/

		DE							
BC		00	01	11	10	00	01	11	10
00	1	1	0	1	1	1	1	0	1
01	0	1	0	0	1	1	1	1	1
11	0	1	0	0	1	1	1	1	1
10	1	1	0	1	1	1	1	0	1

$A = 0$ $A = 1$


$$Y = \bar{C}\bar{E} + \bar{D}E + AC$$

A B C D E

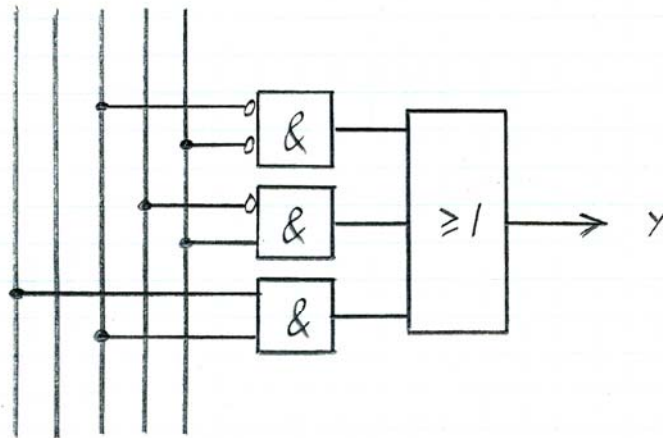

3b/ $Y = \overline{\bar{C}\bar{E} + \bar{D}E + AC} = \overline{\bar{C}\bar{E}} \cdot \overline{\bar{D}E} \cdot \overline{AC}$

A B C D E

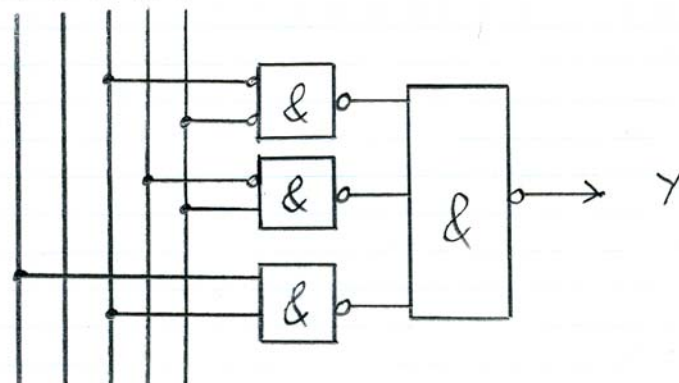

4.


$$T = Q_C Q_B \bar{X} + X \bar{Q}_C \bar{Q}_B$$

$$S = Q_C \bar{X} \bar{Q}_B + X \bar{Q}_C \bar{Q}_B$$

$$R = Q_C Q_B \bar{X} + Q_B X \bar{Q}_C$$

$$D = \bar{Q}_C$$

X	Q_A	Q_B	Q_C	T	S	R	D	Q_A^+	Q_B^+	Q_C^+
0	0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	0	1	0
0	0	1	0	0	0	0	1	0	1	1
0	0	1	1	1	0	1	0	1	0	0
0	1	0	0	0	0	0	1	1	0	1
0	1	0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	0	1	1	1	1
0	1	1	1	1	0	1	0	0	0	0
1	0	0	0	1	1	0	1	1	1	1
1	0	0	1	0	0	0	0	0	0	0
1	0	1	0	0	0	1	1	0	0	1
1	0	1	1	0	0	0	0	0	1	0
1	1	0	0	1	1	0	1	0	1	1
1	1	0	1	0	0	0	0	1	0	0
1	1	1	0	0	0	1	1	1	0	1
1	1	1	1	0	0	0	0	1	1	0

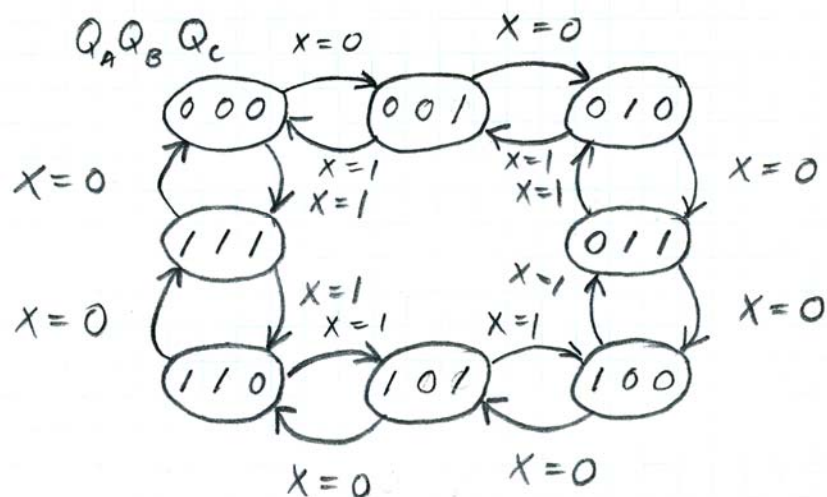

5.

X	Q_A	Q_B	J_A	K_A	J_B	K_B	Q_A^+	Q_B^+
0	0	0	1	-	1	-	1	1
0	0	1	0	-	-	1	0	0
0	1	0	-	1	1	-	0	1
0	1	1	-	0	-	1	1	0
1	0	0	0	-	0	-	0	0
1	0	1	0	-	-	0	0	1
1	1	0	-	0	0	-	1	0
1	1	1	-	0	-	0	1	1

X

$Q_A Q_B$	00	01	11	10
0	1	0	-	-
1	0	0	-	-

$$J_A = \bar{X} \bar{Q}_B = \overline{X + Q_B}$$

X

$Q_A Q_B$	00	01	11	10
0	-	-	0	1
1	-	-	0	0

$$K_A = \bar{X} \bar{Q}_B = \overline{X + Q_B}$$

X


$Q_A Q_B$	00	01	11	10
0	1	-	-	1
1	0	-	-	0

$$J_B = \bar{X}$$



X

$Q_A Q_B$	00	01	11	10
0	-	1	1	-
1	-	0	0	-

$$K_B = \bar{X}$$

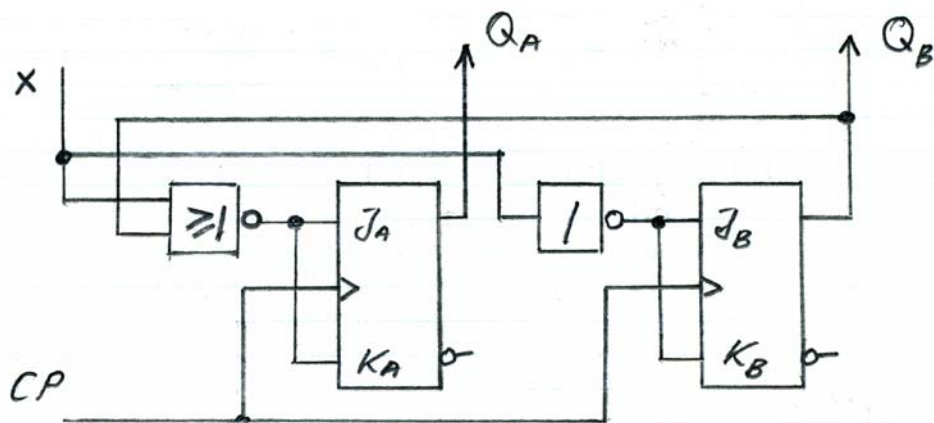

6a)

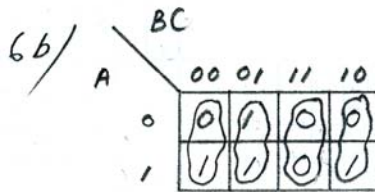
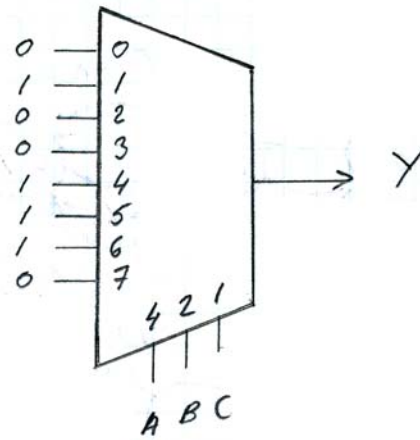


$$BC = 00 \rightarrow Y = A$$

$$BC = 01 \rightarrow Y = 1$$

$$BC = 10 \rightarrow Y = A$$

$$BC = 11 \rightarrow Y = 0$$

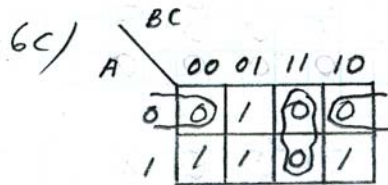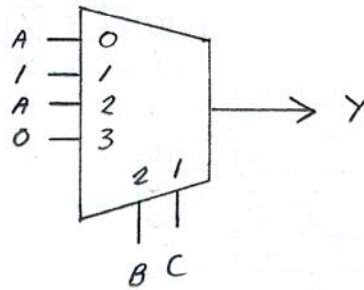

$$\bar{Y} = BC + \bar{A}\bar{C}$$

$$Y = \overline{BC + \bar{A}\bar{C}} = \overline{BC} \cdot \overline{\bar{A}\bar{C}}$$

