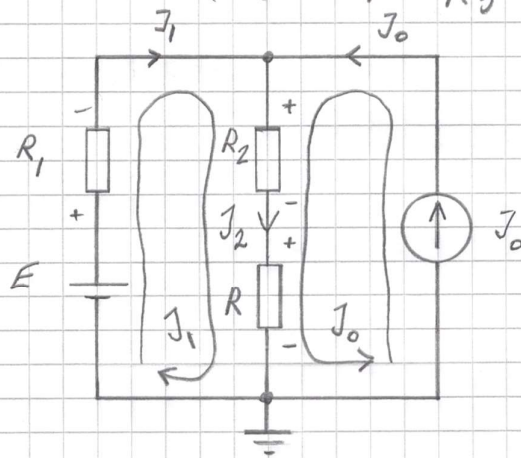


Lösningsförslag till tentamen TMEL08 Eltekniska system 2025-01-07

1. ERSÄTT DE PARALLELLKOPPLADE RESISTORERNA R_3 , R_4 OCH R_5 MED EN RESISTOR

$$R = \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)^{-1} = 2,0 \text{ k}\Omega$$



$$J_2 = J_1 + J_0 \dots (1)$$


$$+E - R_1 J_1 - R_2 (J_1 + J_0) - R (J_1 + J_0) = 0$$

$$+12 - 1000 J_1 - 1000 (J_1 + 0,012) - 2000 (J_1 + 0,012) = 0$$

$$\Rightarrow J_1 = -6,0 \text{ mA}$$

$$(1) \Rightarrow J_2 = -6,0 + 12 \text{ mA} = \underline{\underline{6,0 \text{ mA}}}$$

2. Separatmagnetiserad likströmsmotor

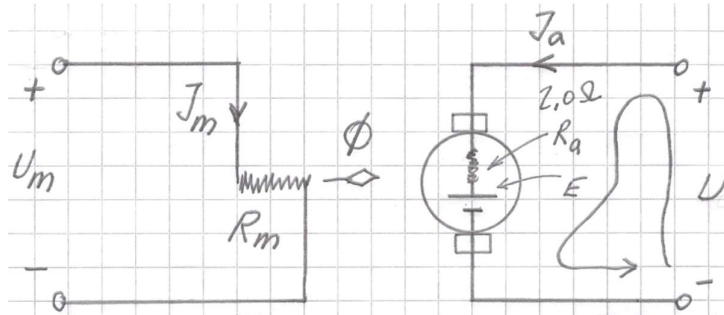

FALL I

$$U_I = 200 \text{ V}$$

$$J_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$J_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

SAMMA MOMENT OCH MAGNETISKT
FLÖDE I DE TVÅ FÄLLEN.

$$\begin{aligned} M &= k_2 \Phi J_{aI} \\ M &= k_2 \Phi J_{aII} \end{aligned} \quad \Rightarrow \quad J_{aII} = J_{aI} = \underline{10 \text{ A}}$$

b) KIRCHHOFFS SPÄNNINGSLAG $\Rightarrow$

$$+U_I - R_a J_{aI} - E_I = 0 \quad \Rightarrow \quad \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a J_{aII} - E_{II} = 0 \quad \Rightarrow \quad \underline{E_{II} = 150 \text{ V}}$$


$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \quad \Rightarrow \quad \underline{n_{II} = 833 \text{ RPM}}$$

3a) $U_{UT} = U_Z - U_{BE}$

OM "ÖVERBELASTNING" EJ SKER, HÅLLER
SIG U_Z KONSTANT $\Rightarrow$

$$U_{UT} = 5,6 - 0,70 = \underline{\underline{4,9 \text{ V}}}$$

3b)

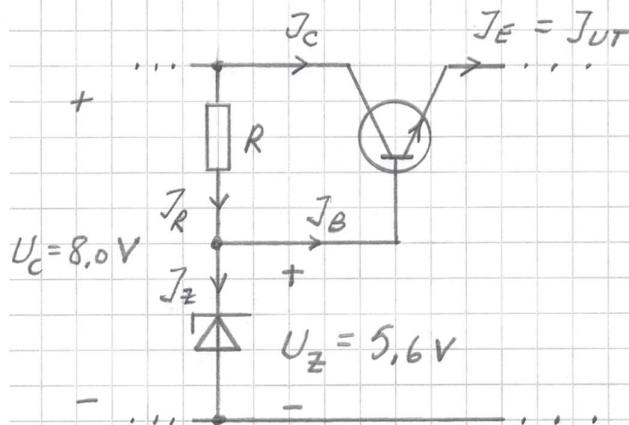

$$I_R = I_Z + I_B \quad \dots, (1)$$

$$I_R = \frac{U_C - U_Z}{R} \Rightarrow I_R = 20 \text{ mA}$$


$$U_Z = 5,6 \text{ V} \text{ om } I_{Z_{\min}} = 10 \text{ mA}$$

$$(1) \Rightarrow I_{B_{\max}} = 10 \text{ mA}$$

$$I_{UT} = I_E = I_B + I_C = I_B + h_{FE} I_B$$

$$\Rightarrow I_{UT_{\max}} = \underline{\underline{1,0 \text{ A}}}$$

3c) LKSTRÖMSSCHEMA

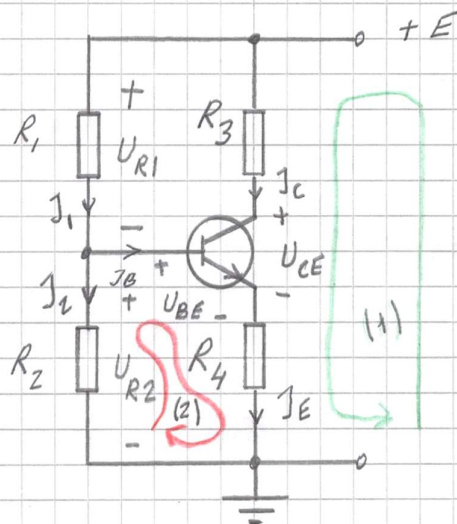

$$+E - R_3 I_C - U_{CE} - R_4 I_E = 0 \quad \dots (1)$$

$$+U_{R2} - U_{BE} - R_4 I_E = 0 \quad \dots (2)$$

$$I_E = I_B + I_C = \frac{I_C}{h_{FE}} + I_C \Rightarrow I_E = 4,04 \text{ mA}$$

$$(1) \rightarrow \underline{\underline{R_4 \approx 2,0 \text{ k}\Omega \text{ (1980 }\Omega\text{)}}}$$

$$(2) \rightarrow U_{R2} = 8,7 \text{ V}$$

$$U_{R2} + U_{R1} = E \Rightarrow U_{R1} = 11,3 \text{ V}$$

$$I_1 = I_2 + I_B = \frac{U_{R2}}{R_2} + \frac{I_C}{h_{FE}} \rightarrow I_1 = 910 \mu\text{A}$$


$$R_1 = \frac{U_{R1}}{I_1} \rightarrow \underline{\underline{R_1 \approx 12 \text{ k}\Omega \text{ (12419 }\Omega\text{)}}}$$

4a)

$$\frac{N_1}{N_2} = \frac{\hat{U}}{\hat{U}_2} = \frac{\hat{U} \leftarrow 230\sqrt{2} \text{ V}}{U_c + 2 \cdot 0,70} \approx \underline{\underline{35}} \quad (34,6)$$

$\uparrow$
 $0,0 \text{ V}$

4b)

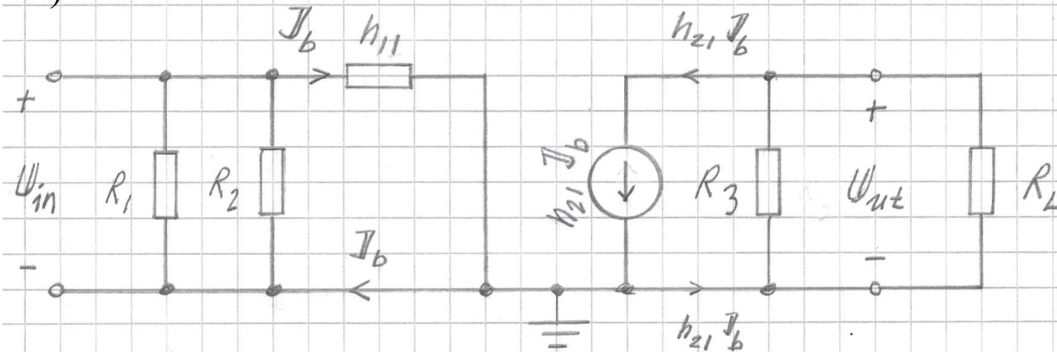

$$F = \frac{U_{out}}{U_{in}} \quad \dots (1)$$

$$U_{out} = - h_{21} I_b \cdot \frac{R_3 \cdot R_L}{R_3 + R_L} \quad \dots (2)$$


$$U_{in} = h_{11} I_b \quad \dots (3)$$

$$(2) \text{ \& } (3) \text{ ins. in } (1) \rightarrow$$

$$F = - \frac{h_{21} \cdot \frac{R_3 \cdot R_L}{R_3 + R_L}}{h_{11}}$$

$$\rightarrow |F| = 267 \text{ GGR}$$

5.

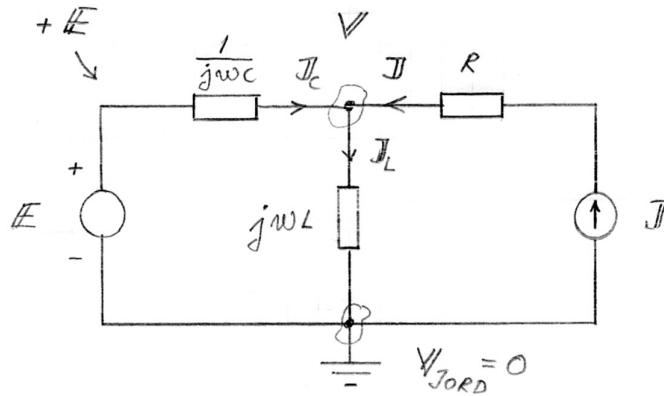

$$I_C + I = I_L \Rightarrow I_C + I - I_L = 0$$

$$\Rightarrow \frac{+E - V}{1/j\omega C} + I - \frac{V - V_{JORD}}{j\omega L} = 0$$

$$\frac{10\sqrt{2} \cdot e^{j0^\circ} - V}{1/j0,020} + 0,20\sqrt{2} \cdot e^{j90^\circ} - \frac{V - 0}{j100} = 0$$

$$j0,20\sqrt{2} - j0,02V + j0,20\sqrt{2} + j0,01V = 0$$

$$j0,01V = j0,40\sqrt{2} \Rightarrow V = +40\sqrt{2} \cdot V$$


$$I_L = \frac{V - V_{JORD}}{j\omega L} \rightarrow I_L = \frac{40\sqrt{2} - 0}{j100} = 0,40\sqrt{2} e^{-90^\circ}$$

$$\leadsto \underline{\underline{i_L(t) = 0,40\sqrt{2} \sin(1000t - 90^\circ) \text{ A}}}$$

$P = R \cdot I^2$ DÄR I ÄR EFFEKTIV-
VÄRDET AV $i(t)$.

$$\underline{\underline{P = 100 \cdot 0,20^2 = 4,0 \text{ W}}}$$

6a)

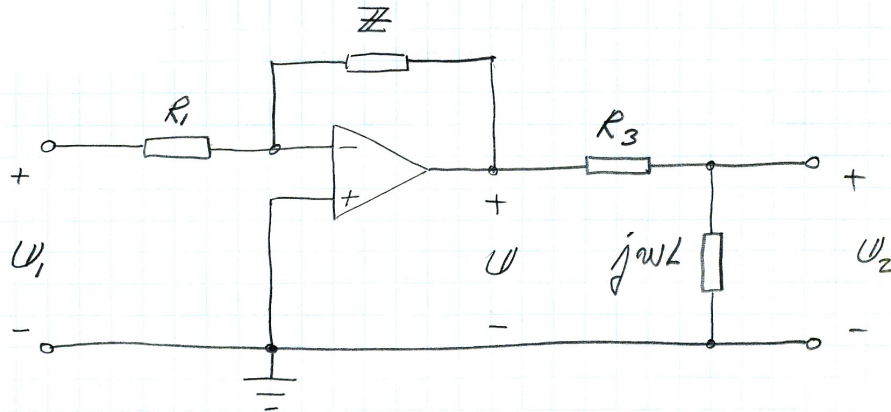

$$\frac{U_2}{U_1} = \frac{U_2}{U} \cdot \frac{U}{U_1} \dots (1)$$

$$U_2 = U \cdot \frac{j\omega L}{R_3 + j\omega L} \Rightarrow \frac{U_2}{U} = \frac{j\omega \cdot \frac{L}{R_3}}{1 + j\omega \cdot \frac{L}{R_3}}$$

$$\Rightarrow \frac{U_2}{U} = \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$

$$\frac{U}{U_1} = - \frac{Z}{R_1} \quad \text{d.h.} \quad Z = \frac{\frac{1}{j\omega C} \cdot R_2}{\frac{1}{j\omega C} + R_2} =$$

$$= \frac{R_2}{1 + j\omega C R_2} \Rightarrow \frac{U}{U_1} = - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega C R_2}$$

$$\Rightarrow \frac{U}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}}$$

$$(1) \Rightarrow \frac{U_2}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}} \cdot \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$

6b)


$$\left| \frac{U_2}{U_1} \right| = 10 \cdot \frac{1}{\sqrt{1^2 + \left(\frac{\omega}{62500} \right)^2}} \cdot \frac{\frac{\omega}{1587}}{\sqrt{1^2 + \left(\frac{\omega}{1587} \right)^2}}$$

$$\text{OM } \omega < 1587 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| \approx \frac{10}{1587} \cdot \omega$$

$$\text{OM } 1587 \frac{\text{RAD}}{\text{s}} < \omega < 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = 10$$

$$\text{OM } \omega > 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = \frac{625000}{\omega}$$

BODE DIAGRAM (AMPLITUDEKURVA)

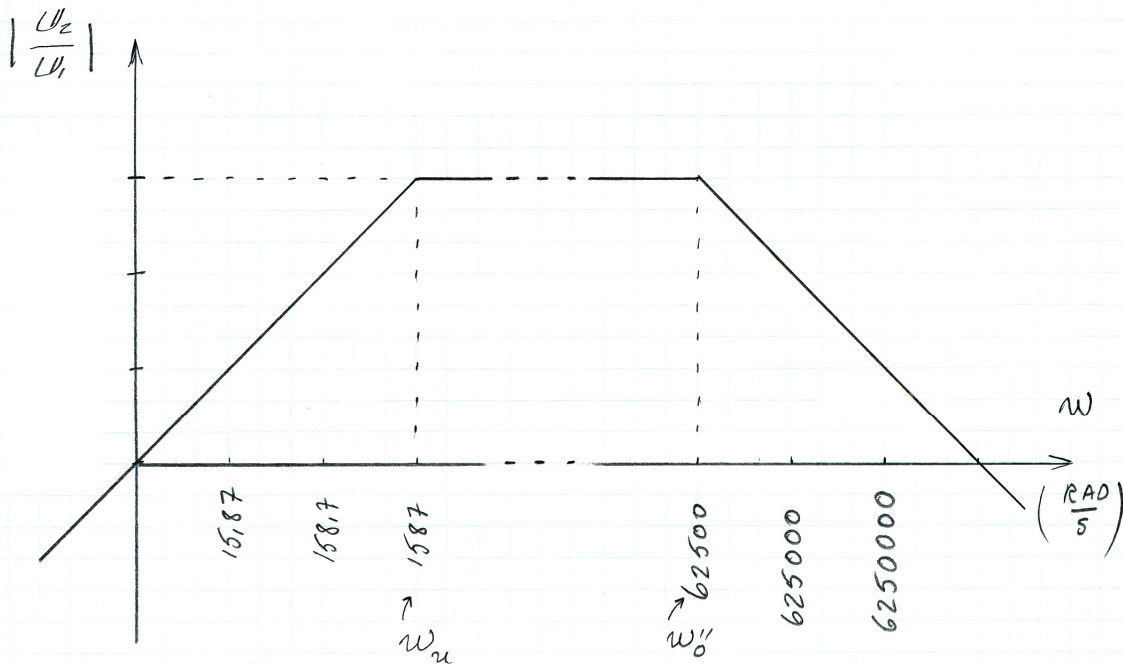

$$\omega_u = 2\pi f_u \Rightarrow \underline{f_u \approx 0,25 \text{ KHz}}$$

$$\omega_o' = 2\pi f_o' \Rightarrow \underline{f_o' \approx 9,9 \text{ KHz}}$$