

TSEA26 Tutorial 3. MAC design

Frans Skarman ¹

November 24, 2021

MAC introduction


- ▶ Most important HW module in DP of any DSP Processor
- ▶ Supports Algorithms like
 - ▶ Convolution (most frequently used in DSP Algorithms)
 - ▶ Filtering, FIR, IIR, Auto-Correlation, Cross-Correlation
 - ▶ Transforms (FFT, DCT etc)
 - ▶ Double Precision Arithmetic Operations

MAC Building blocks

- ▶ Multiplier
- ▶ Long adder
- ▶ Accumulator Registers (ACR)
- ▶ Multiplexers
- ▶ Functions (e.g. Rounding, Scaling, Saturation, Flags etc)

Multipliers

 We only use signed multipliers. Signed values are sign extended, unsigned values are zero extended




MAC Design: A case study

Design a MAC unit with the following operations

- ▶ Integer / Fractional multiplication (16×16)
- ▶ Signed / Unsigned multiplication
- ▶ Convolution with 8 guards and initialization
- ▶ Round
- ▶ Saturation
- ▶ 32 bits Long Plus and Minus
- ▶ 32 bits Long operation: ABS
- ▶ **There are plenty of ways to do this. This is one example**


Basic design

 - ▶ ACR is the accumulation register
- ▶ 0 for clear
- ▶ Feedback for nop




With guard bits

 - ▶ G8 block adds 8 guard bits to input using sign extension




Load to ACR

 - ▶ Load guard, ACRH or ACRL from RF
- ▶ Also allows load of OPA → ACRH, OPB → ACRL
- ▶ Auto-set G when loading ACRH
- ▶ **For clarity these changes are implicit in the rest of the slides**




ACR1 and ACR2 to support long addition

 - ▶ Two or more ACRs allows for long addition



Signed and unsigned multiplication

 - ▶ Add sign extension discussed in the beginning
- ▶ Requires fewer “additional” guard bits




Fractional multiplication

Fractional multiplication “moves” fractional point
16 bit signed fractional multiplication:

$$x \cdot 2^{15} \cdot y \cdot 2^{15} = (x \cdot y) \cdot 2^{15+15} = (x \cdot y) \cdot 2^{30}$$

Normally we assume the fixed point in ACR to be at bit 31
⇒ We need to shift the result


Fractional multiplication

 

Inserted to shift left

We'll build this into a I/F block


Fractional multiplication

 


Rounding

Recall tutorial 1. Using method 2 here


Method 1:

 

Method 2:


 


Rounding

 


Saturation

  
- ▶ From tutorial 1
- ▶ Check guard bits for overflow




min

 

max

 

Rounding

 

Subtraction, absolute value etc.

Same as for ALUs, See tutorial 2 for details.

Exercises

- ▶ Exercise 3.1 and 3.3 for “normal mac design”.
- ▶ Exercise 3.4, 3.2 and 3.5 for complex valued MAC