

# TSEA44 - Design for FPGAs

Andreas Ehliar <ehliar@isy.liu.se>

2014-11-18

- ▶ Did the email regarding no lecture this Wednesday reach you?

- ▶ What can go wrong?
  - ▶ Design mistakes
  - ▶ Synthesis errors
  - ▶ Runtime errors
- ▶ Crossing clock domains
  - ▶ Handshaking
  - ▶ Asynchronous FIFOs
- ▶ FPGA architecture
  - ▶ Adders
  - ▶ Multiplexers
  - ▶ Memories
  - ▶ Multipliers
- ▶ Case study

# A design bug

- ▶ Symptom: The boot sequence of uClinux hangs after a second when the lcache is on.
- ▶ uClinux boots ok with lcache off
- ▶ No problems detected in the monitor when the icache is on

# First try

- ▶ Modify the testbench so uClinux is present in SDRAM models
- ▶ Add interesting signals to the wave window
- ▶ Run the simulation over night

- ▶ In the morning the simulation was not running any longer
- ▶ The log files had filled up all free space on the fileserver...
  - ▶ ...which promptly crashed, causing all sorts of merriment

# Handling long simulation runtimes

- ▶ Use checkpointing to reduce/eliminate the need for logging
  - ▶ Add no signals to wave window (and log for that matter)
  - ▶ Modify UART so printouts are displayed in the transcript window (using `$display()`)
  - ▶ `run 100ms; checkpoint 100ms.chk`
  - ▶ `run 100ms; checkpoint 200ms.chk`
  - ▶ `run 100ms; checkpoint 300ms.chk`
  - ▶ ...


# Handling long simulation runtimes

- ▶ Now you can pinpoint the time interval where the crash happened
  - ▶ Restore the checkpoint in Modelsim that occurred closest before the actual crash
  - ▶ `vsim -restore 600ms.chk`
  - ▶ Debug as usual (by adding signals to wave window/etc)



# So what was the bug?

|                  |      |      |      |      |
|------------------|------|------|------|------|
| Wrong content:   | AAAA | AAAA | CCCC | DDDD |
| Correct content: | AAAA | BBBB | CCCC | DDDD |

 

# What if you can't find a bug during simulation?

- ▶ Very likely you have some undefined behavior in your design
  - ▶ Race condition in RTL code (blocking vs non-blocking assignment)
  - ▶ Incorrect use of “don't cares”
  - ▶ You are not crossing clock domains correctly
  - ▶ etc
- ▶ Not so likely:
  - ▶ You have triggered a bug in the CAD tools (more on this later)

# Clock domain crossings

- ▶ Why do we need synchronous designs?
  - ▶ Race conditions
  - ▶ Metastability
- ▶ Crossing clock domains
  - ▶ (Avoid it if possible)
  - ▶ Using handshakes
  - ▶ Using asynchronous FIFOs
  - ▶ Your own solution
    - ▶ (Only if you like debugging systems where bugs cannot be deterministically reproduced. . . )
- ▶ Don't forget that the reset signal has to be passed to each clock domain!


## An example of a synthesis bug

- ▶ RTL simulation works fine
- ▶ Real hardware doesn't work
- ▶ (There are no clock domain crossings involved)

```
// Work around possible synthesis bug in an
// old version of synthesis tool
logic signed [27:0] foo;
logic signed [27:0] bar;
assign          foo = x2[2] * S6;
assign          bar = x2[3] * C6;
// ***** Third stage *****
always_ff @(posedge clk_i) begin
    if (en) begin
        x3_0 <= x2[0] + x2[1];
        x3_1 <= x2[0] - x2[1];
        x3_2 <= x2[2]*C6 + x2[3]*S6;
        x3_3 <= bar - foo;
```
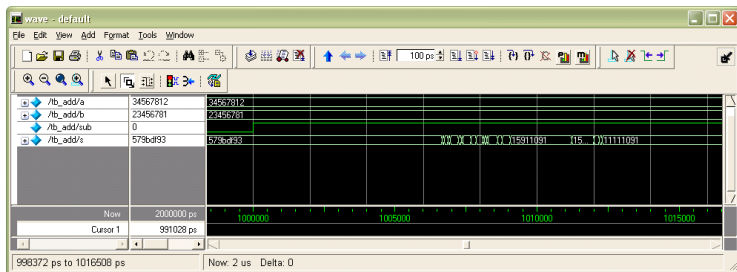
# Post synthesis simulation

- ▶ Synthesize the design
- ▶ Convert the synthesized design back to Verilog (`netgen`)
- ▶ The simulation is done using FPGA components like LUTs instead of at the behavioral level
- ▶ Can even be done after place and route if you want to simulate timing (very useful for power simulations!)



# Writing testbenches for post synthesis netlists 1

```
// Original testbench code

initial begin // Test adder
    @(posedge clk);
    a <= 5;
    b <= 3;
    @(posedge clk);
    if (result !== 8) begin
        $display("Adder has funny ideas of addition");
        $stop;
    end
end

// This code will probably lead to unknown values all over
// the simulation.
```

# Writing testbenches for post synthesis netlists 1

```
// Modified testbench

initial begin // Test adder
    @(posedge clk);
    #4; // (Use an appropriate delay so the setup/hold
        // of flip-flops in the circuit are honored.)
    a <= 5;
    b <= 3;
    @(posedge clk);
    // However, we should still check the result on the
    // clock edge!
    if (result !== 8) begin
        $display("Adder has funny ideas of addition");
        $stop;
    end
end

end
```

# Dealing with bugs that you are unable to reproduce in simulation

- ▶ Add extra debugging logic to the FPGA design
- ▶ Chipscope/SignalTap
  - ▶ Logic analyzer that store samples to built in BlockRAMs
  - ▶ Communicates with the host computer via JTAG
- ▶ Warning!
  - ▶ Many people use ChipScope/SignalTap as a substitute for a comprehensive self-checking testbench.
  - ▶ Don't! You will most likely waste time better spent writing high quality testbenches.



# Single event upset - SEU


- ▶ Very important in aerospace applications
- ▶ Can be important for ground based safety critical applications.
- ▶ (Fortunately not a problem in this course)
- ▶ Some (partial) solutions:
  - ▶ Triplicate logic
  - ▶ Reprogram FPGA often

# Now for something else...

- ▶ Adapting designs to FPGAs
- ▶ Why?
  - ▶ Clock frequency
  - ▶ Area
  - ▶ Power
- ▶ Target FPGA architecture: Xilinx FPGAs with 4 input LUTs (such as Virtex-II)
 
# Determining the maximum frequency of a design


Comparison of actual performance versus requested performance for various timing constraints




- ▶ Knowing the FPGA architecture makes it much easier to optimize your code
- ▶ FPGA editor, floorplanner, PlanAhead, datasheets, timing reports, XDL

- ▶ Slices
- ▶ CLBs
- ▶ Hard blocks (memories, multipliers, I/O, etc)

 
# Combinatorics using a Lookup Table (LUT)



# Adders and carrychains in Xilinx FPGAs

 

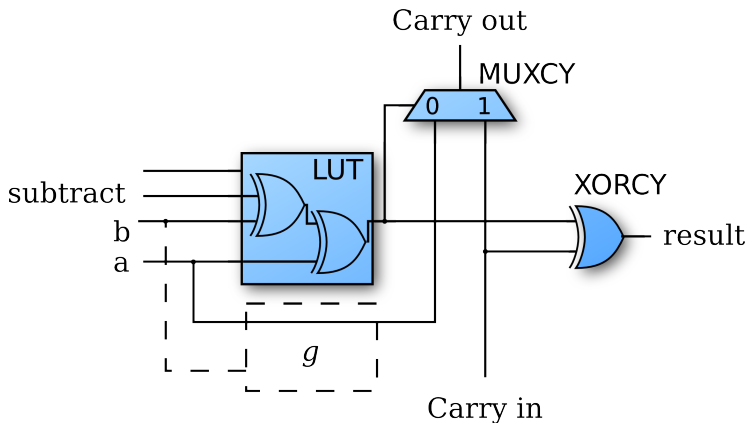
# Add/subtract using one LUT/bit in Xilinx FPGAs




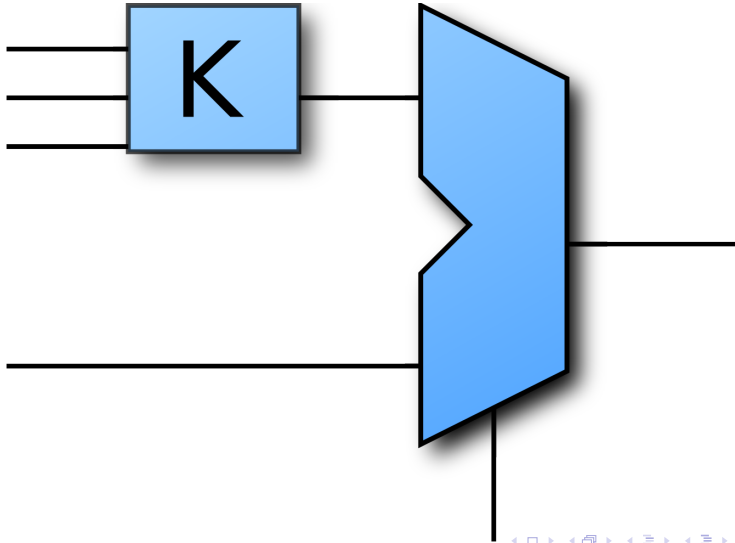
# Rule of thumb for efficient adders in 4 input LUT based FPGAs




# Summary: Adders in 4-input LUT based architectures


- ▶ Plain adder
- ▶ Adder/subtracter
- ▶ 2-to-1 mux and adder
- ▶ Some more esoteric versions:
  - ▶ `result = (opa | opb | opc) + opd;`
  - ▶ `result = (opa & opb) + (opc & opd);` (Using MULT\_AND)
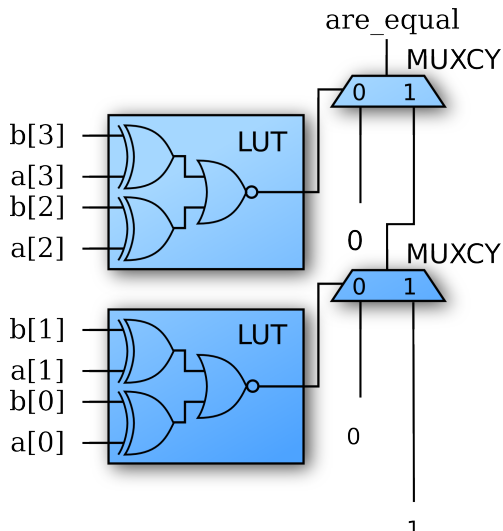
# Using the carry chain for other purposes: Comparators


- ▶ Comparing 2 bits per LUT
- ▶ Comparing 4 bits per LUT if one value is constant!



# Carry chain drawbacks

 

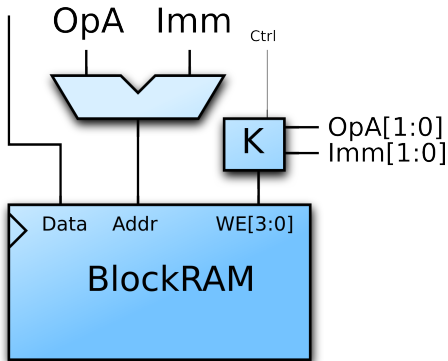WE signal delayed by going through carry-chain




2 bit adder implemented in K using one level LUT logic leads to a faster implementation

- ▶ The carry chain itself is extremely fast
- ▶ Getting on the carry chain is not very fast

# Multiplexers in FPGAs


- ▶ A big difference between ASIC and FPGAs: Multiplexers are cheap in ASIC and expensive in FPGAs
- ▶ 4-input LUT: One 2-to-1 mux
- ▶ Specialized multiplexers in the slices are used to combine LUTs into larger multiplexers

# Multiplexers in Xilinx FPGAs

 

- ▶ Possible uses for spare input:
  - ▶ Invert output, set output to one or zero
  - ▶ Tricky variants based on  $a$ ,  $b$ , and  $s[0]$
- ▶ Trivia question: How many 4-input LUTs do you need to create a 4-to-1 mux (without MUXF $x$  components)?
 
# Avoiding multiplexers in pipelined designs



- ▶ Multiplexers are costly in FPGAs
- ▶ Alternative 1: Use or gates and make sure unused inputs are set to 0 using reset input of flip-flops
- ▶ Alternative 2: Use and gates and make sure unused inputs are set to 1. (See MULT\_AND as well!)

# Types of memories

- ▶ Flip-flops
- ▶ Distributed memories
- ▶ BlockRAMs



- ▶ A LUT (or a combination of LUTs) can be used for small memories
  - ▶ Synchronous write
  - ▶ Asynchronous read
- ▶ Possible configurations
  - ▶ 16x1 bit wide, 1 read/write port: 1 LUT
  - ▶ 32x1 bit wide, 1 read/write port: 2 LUT
  - ▶ 16x1 bit wide, 1 read port, 1 write port: 2 LUTs
- ▶ Other combinations of note:
  - ▶ 16x1 bit wide, 2 read ports, 1 write port: 4 LUTs
  - ▶ A LUT can also be used as a shift register with (up to) 16 bits


- ▶ Features:
  - ▶ 18 kbit memory
  - ▶ True dual port memory with independent clock domains for each port
  - ▶ Configurable bit width (1, 2, 4, 9, 18, or 36 bits)
  - ▶ Read before write, read after write
- ▶ Requirements:
  - ▶ **Synchronous read and write**
- ▶ For an example: See `mon_prog_bram.sv`

- ▶ The Virtex-II FPGA also contains numerous multipliers
- ▶ Features:
  - ▶ Combinational 18x18 bit two's complement multiplier
- ▶ (Newer FPGAs have more advanced “*DSP blocks*” where the multiplier is combined with adders and registers)


- ▶ Standard rule: Large memories should be synchronous
- ▶ For high frequency designs you want to register the output of the memory as well.
- ▶ For power reasons you shouldn't enable the memory unless necessary
  - ▶ Double check that your enables work when inferring a memory!
- ▶ Smaller memories may be asynchronous if necessary
- ▶ You shouldn't have a reset signal for your memory array
  - ▶ Easy to forget for shift registers!
 
# Memories larger than one BlockRAM

72 Kilobits using 4 BlockRAMs  
that are 9 bit wide



 
72 Kilobits using 4 BlockRAMs  
that are 36 bit wide




- ▶ Why use the right variant? Reduced power consumption!
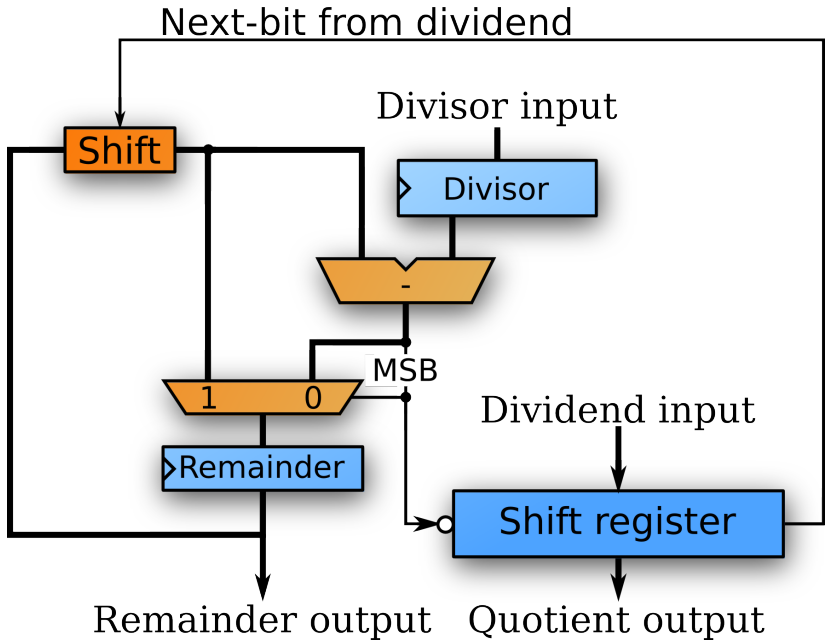
# A case study: A divider for a RISC processor


- ▶ Used in a 32 bit RISC processor
- ▶ Target frequency: Over 320 MHz in a Virtex-4 (speedgrade -12)
- ▶ Uses restoring division algorithm (basic operations are shift, subtract, and select)



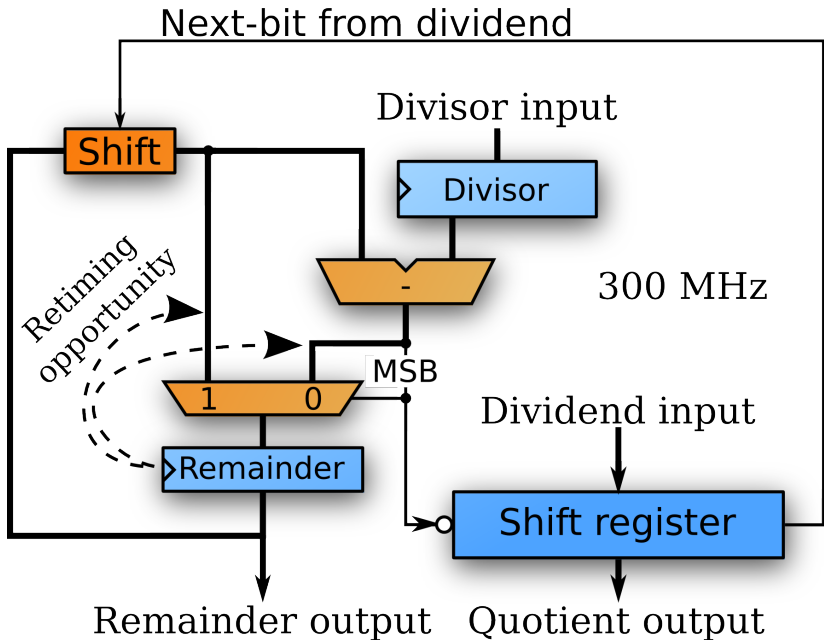



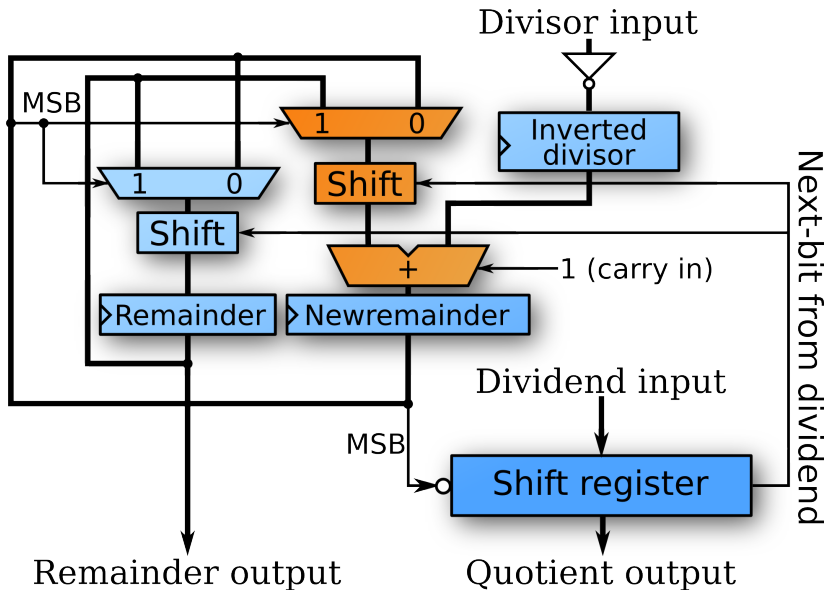- ▶ Can't combine subtracter and 2-to-1 mux!
- ▶ Solution: Preprocess divisor and use an adder instead.




- ▶ Synthesis tool was too clever
- ▶ Manually instantiating the components worked
- ▶ Alternatively a complete rewrite of the module worked as well
- ▶ Improves clock frequency to 377 MHz (from 300 MHz)


# Dealing with negative numbers

- ▶ Idea: Take absolute value of dividend and divisor
- ▶ Negate quotient and remainder if necessary
- ▶ For a 32 bit divider this seems to require around 128 extra LUTs...


# Absolute value for divisor

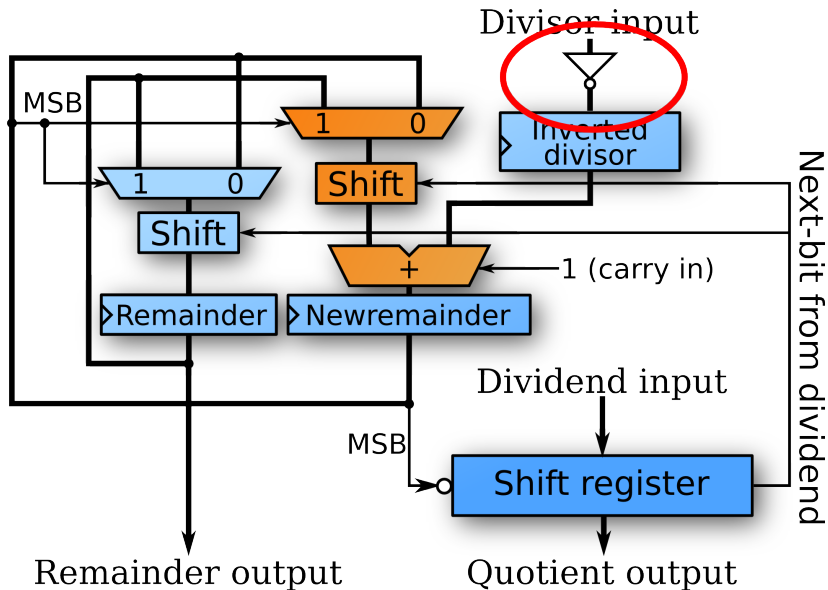


# Absolute value for dividend

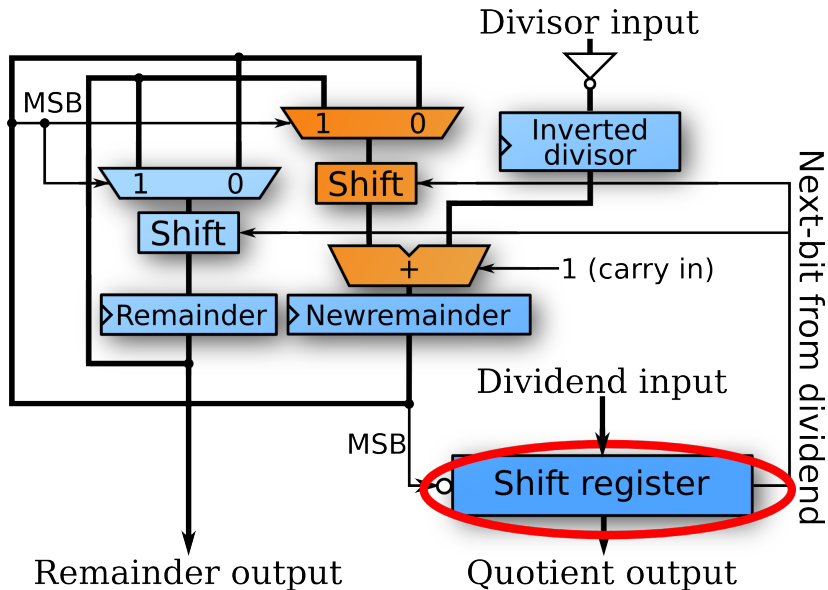
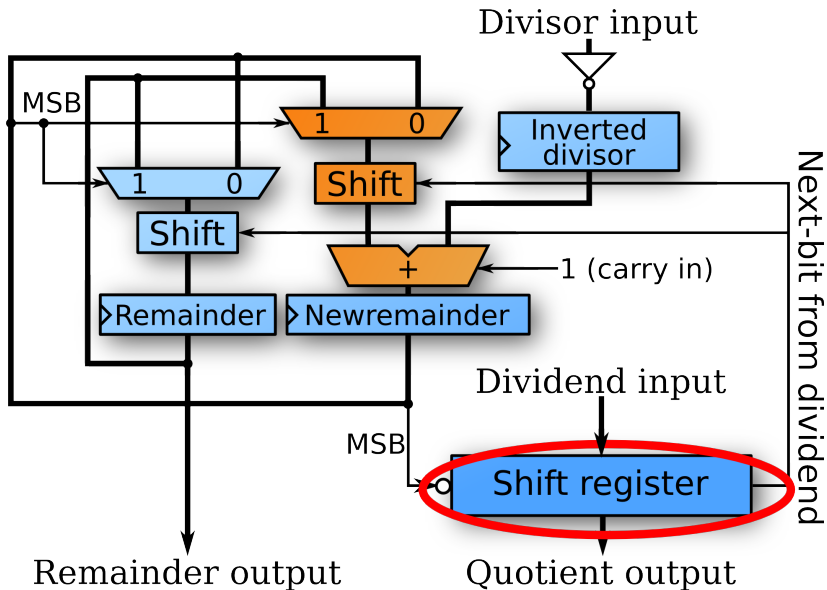
# Quotient negator - Reuse negator for dividend



# Remainder negator

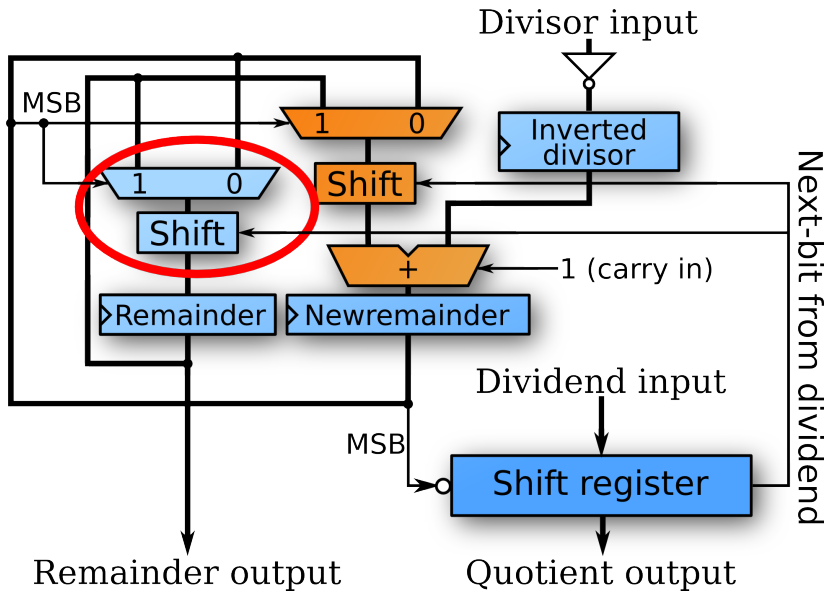



# Tricky to do in practice

- ▶ Required signals for shift register:
  - ▶ 1. Load enable/shift enable
  - ▶ 2. Invert enable
  - ▶ 3. Input data of new dividend
  - ▶ 4. Input data of new dividend (MSB bit)
  - ▶ 5. Current value of register
- ▶ 5 inputs to a 4 input LUT?

# Tricky to do in practice - Solution


- ▶ Solution: Skip MSB of dividend input for ABS operation
- ▶ Always invert the dividend, only add 1 as a carry in if appropriate
  - ▶ This can be implemented by adding a few extra LSB bits
  - ▶ If we had a positive value we can compensate for the inversion at shift out
  - ▶ We can even add a control bit to select between signed/unsigned division
- ▶ Manual instantiation was necessary to actually implement this

# Results for Virtex-4, speedgrade 12

- ▶ Unoptimized, unsigned: 300 MHz, 107 LUTs
- ▶ Retimed, unsigned: 377 MHz, 140 LUTs
- ▶ Retimed, signed: 361 MHz, 151 LUTs
- ▶ Retimed, signed or unsigned: 363 MHz, 153 LUTs
- ▶ Interested? Download the code at  
[http://www.da.isy.liu.se/~ehliar/ae\\_instlib/](http://www.da.isy.liu.se/~ehliar/ae_instlib/)

- ▶ Last resort when synthesis attributes and rewriting the RTL code doesn't work
- ▶ Not portable between FPGA vendors
  - ▶ Surprisingly portable to ASIC however

# 4-to-1 mux with two LUT4

 

# Manual instantiation of flip-flops

- ▶ Allows you to ensure that the correct signals are connected to the D, CE, and SR inputs
  - ▶ XST often seem to select the wrong input for SR
  - ▶ Background: SR input is quite slow compared to D input
- ▶ Can sometimes be avoided by rewriting the code or using synthesis attributes
- ▶ Often easier to just instantiate flip-flop primitives directly

# Manual instantiation of LUTs

- ▶ Often much harder than to rewrite the code or using synthesis attributes
- ▶ A good idea to hide instantiation details in a library if possible
  - ▶ Carry chain instantiation (MUXCY, XORCY, generate loop, etc)
  - ▶ Large multiplexers (MUXF5, MUXF6, MUXF7, etc)
- ▶ See [http://www.da.isy.liu.se/~ehliar/ae\\_instlib/](http://www.da.isy.liu.se/~ehliar/ae_instlib/) for the library I'm using.

# Manual instantiation of Memories and DSP blocks

- ▶ Well documented in various app-notes



# Synthesis attributes

- ▶ A convenient way to force the synthesis tool to do what you mean
- ▶ In VHDL:
  - ▶ `attribute keep : string;`
  - ▶ `attribute keep of mysignal: signal is "TRUE"`
- ▶ In Verilog:
  - ▶ `(* KEEP = "TRUE" *) wire mysignal;`
- ▶ Note: Synthesis attributes discussed here are for XST, not Precision!
  - ▶ (Read the Precision manual)

# Synthesis attribute KEEP

- ▶ Preserves the selected signal
- ▶ Use case:
  - ▶ The synthesis tool makes a bad optimization decision.
  - ▶ By using KEEP you can ensure that a certain signal is not hidden inside a LUT and hence guide the optimization process.

## KEEP example from a display controller

```
wire inimagey = (yctr > 31) && (yctr < 192);
wire inimagex = (xctr > 15) && (xctr < 26);
...
always @(posedge clk) begin
if (inimagey && (xctr == 15) ) begin
    ...
end else if(inimagey && (xctr == 26)) begin
    ...
if (inimagey && (xctr == 15) ) begin
    ...
end else if(inimagey && (yctr[2:0] == 7)) begin
    ...

```

- ▶ Problem: Synthesis tool merged inimagey test with other tests in suboptimal way


## Solution: force inimagey and inimagex to be separate signals

```
(* KEEP = "TRUE" *) wire inimagey;  
(* KEEP = "TRUE" *) wire inimagex;  
  
assign inimagey = (yctr > 31) && (yctr < 192);  
assign inimagex = (xctr > 15) && (xctr < 26);
```

- ▶ Allowed me to save area in an area constrained situation
  - ▶ Especially important when targetting both CPLD and FPGAs with a single IP core


- ▶ Allows you to select encoding for state machines
- ▶ Useful when synthesis tool make suboptimal state machine encoding choices
- ▶ (Alternatively: You can disable FSM optimization if you *really* want to)
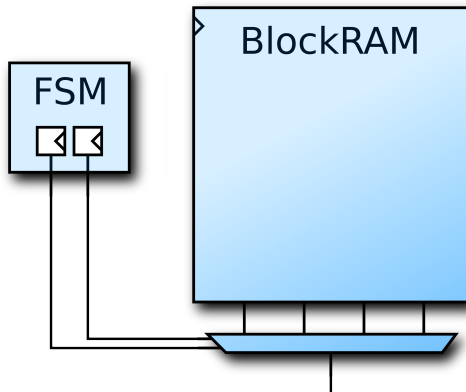
## Example: Memory byte select in a processor



- ▶ Signal encoding specified 2 FF, 4 states.
- ▶ Two signals into mux control signal
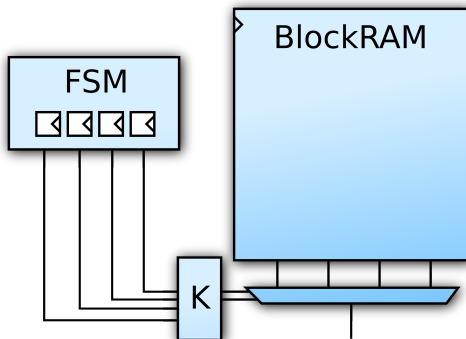
## Example: Memory byte select in a processor




- ▶ Heuristics in synthesis tool selected one-hot coding for FSM...

# EQUIVALENT\_REGISTER\_REMOVAL attribute

- ▶ Allows you to specify that certain registers should *not* be optimized away.
- ▶ Perfect when you don't want the synthesis tool to touch your carefully optimized (duplicated) flip-flops



## Example: Operand bus in a processor

 

- ▶ Problem: Manual register duplication in read operand stage is removed by synthesis tool
- ▶ Solution: Disable optimization locally by setting `EQUIVALENT_REGISTER_REMOVAL` to "no"

# Conclusions

- ▶ By mapping your design to the FPGA in an efficient manner you can significantly improve the performance of your design
- ▶ Keep this in mind early in the design phase.
- ▶ (However, don't optimize unless you really need to.)
- ▶ Looking for master's thesis projects?
  - ▶ Talk to me if you are interested in for example FPGA related projects