


A short introduction to SystemVerilog

- For those who know VHDL
- We aim for synthesis

Verilog & SystemVerilog

- 1984 - Verilog invented, C-like syntax
 - First standard - Verilog 95
 - Extra features - Verilog 2001
 - A super set - SystemVerilog
- VHDL

 [www.vhdl.org/sv/SystemVerilog_3.1a.
pdf](http://www.vhdl.org/sv/SystemVerilog_3.1a.pdf)




Verilog vs VHDL

Verilog-2001 adds a lot of VHDL functionality but still lacks advanced data structures


VHDL

2001

95

 

SystemVerilog

 

SystemVerilog constructs


- Flip-flop
- Register
- Adder
- Multiplier (signed, unsigned)
- Concatenation
- Priority decoder
- Memory (sync and async)

Synch and Single Pulse

```
reg x,y;      // variable type (0,1,Z,X)
wire button; // net type (0,1,Z,X)

// SSP
always @(posedge clk)          // procedural block
begin
    x <= stb;
    y <= x;
end

 assign button = x & ~y;          //continuous assignment
```




Is this the same thing?

```
reg x,y;      // variable type (0,1,Z,X)
wire button; // net type (0,1,Z,X)

// SSP
always @(posedge clk)          // procedural block
begin
    x <= stb;
end

always @(posedge clk)          // procedural block
begin
    y <= x;
end

assign button = x & ~y;
```

 

One more thing


```
// This is OK
always @(posedge clk)
begin
    x <= stb;
    if (rst)
        x <= 0;
end

// same as
always @(posedge clk)
begin
    if (rst)
        x <= 0;
    else
        x <= stb;
end
```

```
// This is not OK (synth)
// multiple assignment
always @(posedge clk)
begin
    x <= stb;
end

always @(posedge clk)
begin
    if (rst)
        x <= 0;
end
```

SV: always_{comb, ff, latch}

 

- always blocks do not guarantee capture of intent
- If not edge-sensitive then only a warning if latch inferred
- always_comb, always_latch and always_ff are explicit
- Compiler Now Knows User Intent and can flag errors accordingly

// forgot else branch
// a synthesis warning
always @(a or b)
if (b) c = a;

// compilation warning
always_comb
if (b)
c = a;

// yes
always_comb
if (b)
c = a;
else
c = d;

reg or wire in Verilog

1) **always** ...

a <= b & c;

reg both

2) **assign** a = b & c;
wire both

3) both wire
wire both
module

SV relaxes variable use

A variable can receive a value from one of these :

- any number of always/initial-blocks
- one always_ff/always_comb-block
- one continuous assignment
- one module instance

We can skip wire

If you don't like reg, use logic instead

Signed/unsigned

Numbers in verilog (95) are unsigned. If you write

```
assign d3 = s + d2;
```

s and d2 get zero-extended

```
wire signed [4:0] d3;  
reg signed [3:0] s;  
wire signed [3:0] d2;
```

```
assign d3 = s + d2;
```

s and d2 get sign-extended

Blocking vs Non-Blocking

- Blocking assignment (=)
- Assignments are blocked when executing
- The statements will be executed in sequence, one after one

```
always_ff @(posedge clk) begin
    B = A;
    C = B;
end
```

- Non-blocking assignment (<=)
- Assignments are not blocked
- The statements will be executed concurrently

```
always_ff @(posedge clk) begin
    B <= A;
    C <= B;
end
```

Use <= for sequential logic

Blocking vs Non-Blocking

```
always_comb begin  
    C = A & B;  
    E = C | D;  
end
```

```
always_comb begin  
    C <= A & B;  
    E <= C | D;  
end
```

Same result

Use = for combinatorial logic

Verilog constructs for synthesis

Construct type	Keyword	Notes
ports	input, inout, output	
parameters	parameter	
module definition	module	
signals and variables	wire, reg	Vectors are allowed
instantiation	module instances	E.g., mymux m1(out, iO, il, s);
Functions and tasks	function, task	Timing constructs ignored
procedural	always, if, then, else, case	initial is not supported
data flow	assign	Delay information is ignored
loops	for, while, forever	
procedural blocks	begin, end, named blocks, disable	Disabling of named blocks allowed

Operators

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+*	Unary plus
	-*	Unary minus
Logical	!	Logical negation
	&&	Logical and
		Logical or
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	Inequality
Reduction	~	Bitwise negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
Shift	>>	Right shift
	<<	Left shift
Concatenation	{ }	Concatenation
Conditional	?	conditional

Replication
 $\{3\{a\}\}$
 same as
 $\{a,a,a\}$

Parameters



```
module w(x,y);  
input x;  
output y;  
parameter z=16;  
localparam s=3'h1;  
...  
  
endmodule
```

```
w w0(a,b);  
w #(8) w1(a,b);  
w #( .z(32) ) w2( .x(a), .y(b));
```

Constants ...

```
`include "myconstants.v"  
  
`define PKMC  
  
`define S0 1'b0  
  
`define S1 1'b1  
  
  
  
`ifdef PKMC  
  
...  
  
`else  
  
...  
  
`endif
```

Comment: FSM1

  

```


//NEXT
always_ff @(posedge clk) begin
  if (rst)
    s <= `S0;
  else
    case (s)
      `S0:
        if (x)
          s <= `S1;
      default:
        if (x)
          s <= `S0;
    end
  
```

```


//OUT
always_comb begin
  case (s)
    `S0: if (x)
      u = 1'b1;
    else
      u = 1'b0;
    default: if (x)
      u = 1'b0;
    else
      u = 1'b1;
  end

```

Comment: FSM2

 
 
```
// COMB ◻
always_comb begin
    ns = `S0; // defaults
    u = 1'b0;
    case (s)
        `S0: if (x) begin
            ns = `S1;
            u = 1'b1;
        end
        default:
            if (~x) begin
                u = 1'b1;
                ns = `S1;
            end
    end
end
```



```
// state register
always_ff @(posedge clk) begin
    if (rst)
        s <= `S0;
    else
        s <= ns;
end
```

Good to have

```
typedef logic [3:0] nibble;  
nibble nibbleA, nibbleB;
```

```
typedef enum {WAIT, LOAD, STORE} state_t;  
state_t state, next_state;
```

```
typedef struct {  
    logic [4:0] alu_ctrl;  
    logic stb,ack;  
    state_t state } control_t;  
control_t control;
```

```
assign control.ack = 1'b0;
```

System tasks


Initialize memory from file

```
module test;  
  
reg [31:0] mem[0:511]; // 512x32 memory  
integer i;  
  
initial begin  
    $readmemh("init.dat", mem);  
    for (i=0; i<512; i=i+1)  
        $display("mem %0d: %h", i, mem[i]); // with CR  
end  
...  
endmodule
```

Do you want a nicer test bench?

=> Try a task or
two!
`my_test_bench`
 
```
initial begin
  uart1.putstr("s 0");
end
```



Tasks

```
module uart_tasks(input clk, uart_tx,
                  output logic uart_rx);

initial begin
    uart_rx = 1'b1;
end

task getch();
    reg [7:0] char;

    begin
        @(negedge uart_tx);
#4340;
#8680;
        for (int i=0; i<8; i++) begin
            char[i] = uart_tx;
#8680;
        end
        $fwrite(32'h1,"%c", char);
    end
endtask // getch

```

```
task putch(input byte char);
begin
    uart_rx = 1'b0;
    for (int i=0; i<8; i++)
#8680 uart_rx = char[i];
#8680 uart_rx = 1'b1;
#8680;
    end
endtask // putch

task putstr(input string str);
byte ch;
begin
    for (int i=0; i<str.len; i++)
        begin
            ch = str[i];
            if (ch)
                putch(ch);
        end
        putch(8'h0d);
    end
endtask // putstr


endmodule // uart_tb

```

In the testbench

```
wire tx, rx;  
...  
// send a command  
initial begin  
    #100000 // wait 100 us  
    uart1.putstr("s 0");  
end  
  
// instantiate the test UART  
uart_tasks uart1(.*);  
  
// instantiate the computer  
computer computer1(.*);
```


Lab 0 : Build a UART in Verilog

 

clk = 40 MHz

baud rate = 115200

full duplex

 

UCF = User constraint file

```
CONFIG PART = XC2V4000-FF1152-4 ;  
  
NET "clk" LOC = "AK19";  
  
# SWx buttons  
NET "stb" LOC = "B3" ;  
NET "rst" LOC = "C2" ;  
  
# LEDs  
NET "u<0>" LOC = "N9"; //leftmost  
NET "u<1>" LOC = "P8";  
NET "u<2>" LOC = "N8";  
NET "u<3>" LOC = "N7";  
...  
# DIP switches  
NET "kb<0>" LOC = "AL3"; //leftmost  
NET "kb<1>" LOC = "AK3";  
NET "kb<2>" LOC = "AJ5";  
NET "kb<3>" LOC = "AH6";  
...
```

Lab0: Testbench


 
 


Figure 2.1: The letter A (0x41). Time per bit is $8.68 \mu\text{s}$.

Arrays-packed/unpacked



```
wire [31:0] bus;           // a packed array
reg [3:0][7:0] mem;        // so is this
                           // both are contiguous

 assign bus = mem;
assign bus[31:16] = mem[3:2];
```



Arrays-packed/unpacked
  
```
wire [31:0] bus;  
reg [7:0] mem [0:3]; // 4 bytes  
...  
assign bus[31:24] = mem[3];
```



Case study

- Two square wave generators driven by an FSM reading from an 8 bit wide ROM
- The 8 bit wide ROM is divided into 8 word “packets”
 - Addr 0: LSB of number of clock cycles for this “packet”
 - Addr 1: MSB of number of clock cycles for this “packet”
 - Addr 2,3: LSB, MSB of square wave period, channel 1
 - Addr 4,5: LSB, MSB of square wave period, channel 2
 - Addr 6,7: Unused