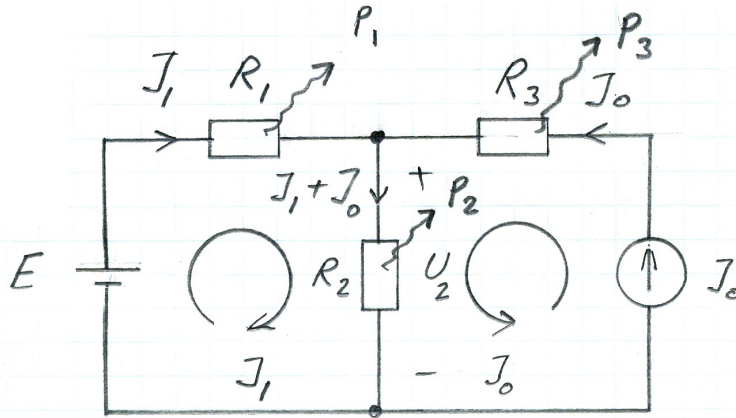


1. *Lösning med slinganalys*



a)

$$+E - R_1 J_1 - R_2 (J_1 + J_0) = 0 \Rightarrow$$

$$+15 - 3,0 J_1 - 3,0 (J_1 + 1,0) = 0 \Rightarrow J_1 = 2,0 \text{ A}$$

$$U_2 = R_2 (J_1 + J_0) \Rightarrow \underline{\underline{U_2 = 9,0 \text{ V}}}$$


b)

$$P_1 = R_1 \cdot J_1^2 \Rightarrow \underline{\underline{P_1 = 12 \text{ W}}}$$

$$P_2 = R_2 \cdot (J_1 + J_0)^2 \Rightarrow \underline{\underline{P_2 = 27 \text{ W}}}$$

$$P_3 = R_3 J_0^2 \Rightarrow \underline{\underline{P_3 = 3,0 \text{ W}}}$$

2a)

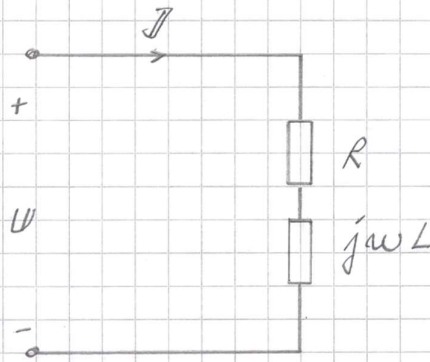

$$u(t) = 230\sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightsquigarrow U = 230\sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230\sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0573} =$$

$$= \frac{230\sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} e^{j \arctan \frac{18}{24}}} = 7,67\sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightsquigarrow i(t) = 7,67\sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}$$

2b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R \cdot I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

$$Q = X_L I^2 = \omega L I^2 \Rightarrow \underline{Q = 1,06 \text{ kVAR}}$$

($Q = Q_L$, DÄ C ÄR BORTKOPPLAD)

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = UI \cos \varphi$$

$$\varphi = \arg U - \arg I = 37^\circ$$


$$Q = UI \sin \varphi$$

$$\begin{array}{cc} \uparrow & \uparrow \\ 0^\circ & -37^\circ \end{array}$$

$$S = UI$$

$$\begin{array}{cc} \uparrow & \uparrow \\ 230V & 7,67A \end{array}$$

2c)

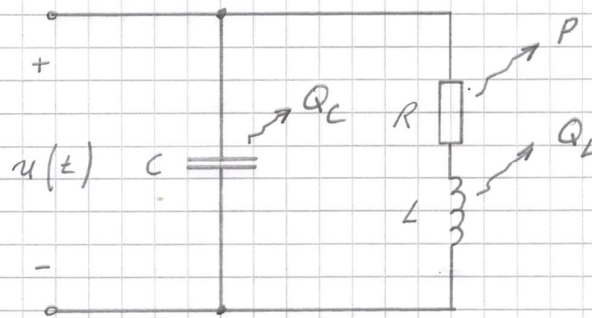

$$Q = Q_L - Q_C$$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = \frac{1}{X_C} = \frac{1}{\omega C} = U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu F}$$

2d)

$$Q = 0 \Rightarrow S = P \text{ och } \cos \varphi = 1 \rightarrow \varphi = 0^\circ (\arg I = \arg U)$$

$$S = UI \rightarrow 1,41 \cdot 10^3 = 230 \cdot I \rightarrow I = 6,13A$$

$$\Rightarrow i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}$$

$$3a) \quad U_{ut} = U_Z - U_{BE} \Rightarrow \underline{U_{ut} = 4,9 \text{ V}}$$

$$U_{CE} = U_{in} - U_{ut} \Rightarrow \underline{U_{CE} = 7,1 \text{ V}}$$

3b) Spänningsfallet mellan plus- och minusingången på OP:n är noll.

$$\Rightarrow U_{R2} = U_Z$$

$$U_{R2} = U_{ut} \cdot \frac{R_2}{R_1 + R_p + R_2}$$

$$R_p = 0 \Rightarrow$$

$$5,6 = U_{ut} \cdot \frac{2400}{7500 + 0 + 2400} \Rightarrow U_{ut} \approx 23 \text{ V}$$


$$R_p = 10 \text{ k}\Omega \Rightarrow$$

$$5,6 = U_{ut} \cdot \frac{2400}{7500 + 10000 + 2400} \Rightarrow U_{ut} \approx 46 \text{ V}$$

$$\underline{\underline{\text{ALLTSA } 23 \text{ V} \lesssim U_{ut} \lesssim 46 \text{ V}}}$$

$$3c) \quad U_{ref} = U_{ut} \cdot \frac{R_1}{R_1 + R_2} \Rightarrow \underline{\underline{R_2 \approx 2,7 \text{ k}\Omega}}$$


4a)

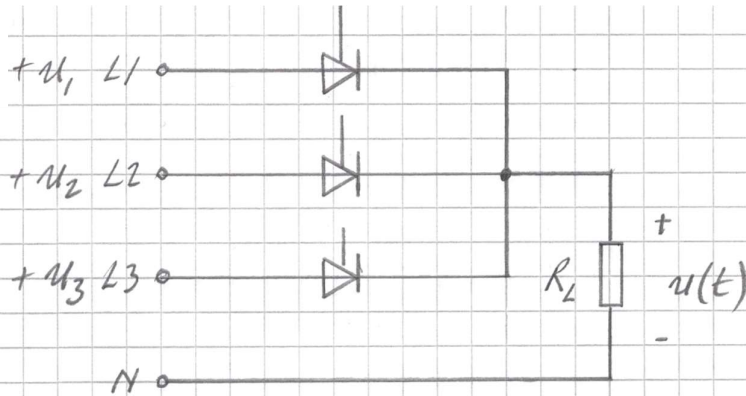

$$T = \frac{1}{f}$$


$$f = 50 \text{ Hz}$$

$$\Rightarrow T = 20 \text{ ms}$$

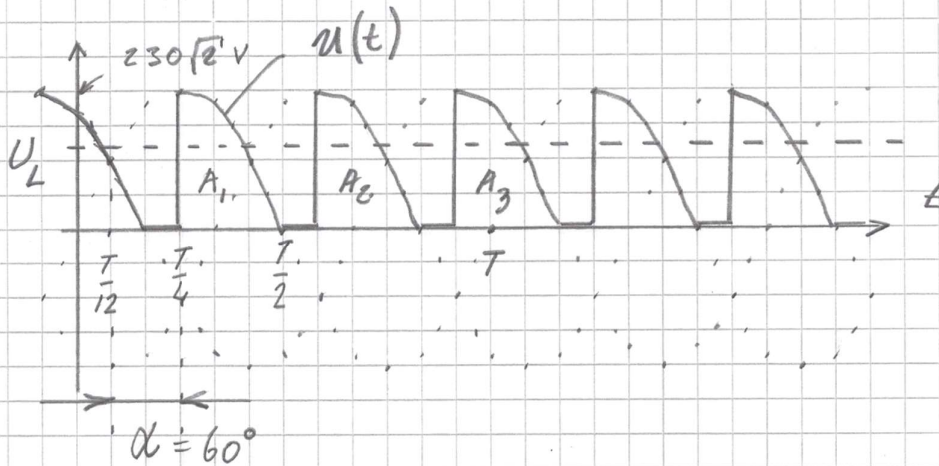

$$\begin{aligned}
 \underline{U_L} &= \frac{1}{T} \int_0^T u(t) dt = \left| A_1 = A_2 = A_3 \right| = \\
 &= \frac{3}{T} \int_{T/4}^{T/2} u(t) dt = \frac{3}{T} \int_{T/4}^{T/2} 230\sqrt{2} \sin(\omega t) dt = \\
 &= \left| T = \frac{2\pi}{\omega} \right| = \frac{3\omega}{2\pi} \cdot 230\sqrt{2} \left[\frac{-\cos(\omega t)}{\omega} \right]_{\frac{\pi}{2\omega}}^{\frac{\pi}{\omega}} = \\
 &= 155,3 \left[-\cos \pi + \cos \frac{\pi}{2} \right] = \underline{155 \text{ V}} \quad (155,3)
 \end{aligned}$$


4b)

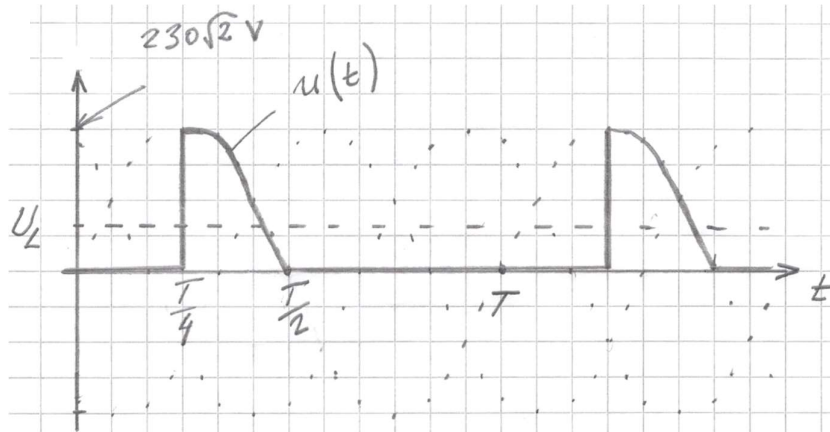

$$U_L = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \int_{T/4}^{T/2} 230\sqrt{2} \sin(\omega t) dt =$$

$$= \dots \approx 52 \text{ V } (51,8)$$

5. SERIEMOTOR

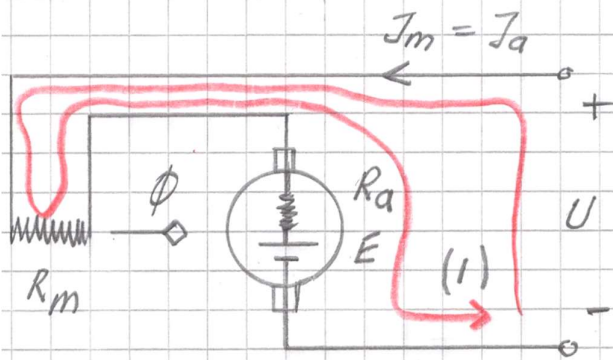

MAGNETISKT OMÄTTAD $\rightarrow \Phi = k_3 I_m = k_3 I_a$

FALL I

$$U_I = 220 \text{ V}$$

$$M_I = M$$

$$n_I = 1000 \text{ RPM}$$

$$I_{aI} = 100 \text{ A}$$

FALL II

$$U_{II} = 220 \text{ V}$$

$$M_{II} = 4M$$

$$n_{II} = ?$$

$$I_{aII} = ?$$

$$\frac{M_I}{M_{II}} = \frac{k_2 I_{aI} \Phi_I}{k_2 I_{aII} \Phi_{II}}$$

$$\frac{M_I}{M_{II}} = \frac{k_2 I_{aI} \cdot k_3 I_{aI}}{k_2 I_{aII} \cdot k_3 I_{aII}}$$

$$\frac{M}{4M} = \frac{k_2 k_3 I_{aI}^2}{k_2 k_3 I_{aII}^2} \Rightarrow \underline{\underline{I_{aII} = 200 \text{ A}}}$$

$$+ U - R_m J_a - R_a J_a - E = 0 \dots (1)$$

$$\text{FALL I} \Rightarrow +220 - 0,050 \cdot 100 - 0,050 \cdot 100 - E_I = 0$$

$$\text{FALL II} \Rightarrow +220 - 0,050 \cdot 200 - 0,050 \cdot 200 - E_{II} = 0$$

$$\Rightarrow E_I = 210 \text{ V} \quad E_{II} = 200 \text{ V}$$

$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi_I n_I}{k_1 \Phi_{II} n_{II}}$$

$$\frac{E_I}{E_{II}} = \frac{\cancel{k_1} \cancel{k_3} J_{aI} n_I}{\cancel{k_1} \cancel{k_3} J_{aII} n_{II}} \Rightarrow \underline{\underline{n_{II} = 476 \text{ RPM}}}$$