

# TSTE12 Design of Digital Systems Lecture 4

Kent Palmkvist

## Agenda

- Practical issues
- Short tool overview
- Introduction to VHDL, continued
  - Timing
  - Testbench

## TSTE12 Deadlines Y,D,ED

- First meeting with supervisor should happen no later than today!
  - Determine project manager (contact person)
  - Questions (short meeting)
- Lab 1 deadline Wednesday 6 September at 21.00
  - Require pass to continue project!
- Tuesday 5 September: First version of requirement specification
  - We use LIPS "light", want to capture expected behavior of final result in requirement specification

## TSTE12 Deadlines MELE, erasmus

- Group definition Wednesday 6 September (afternoon)
  - On web, include supervisor assignment
- Friday 8 September: First meeting with supervisor
  - Determine project manager (contact person)
  - Question (short meeting)
- Tuesday 12 September: First version of requirement specification

# MUX lab access

- LiU-card should now give access to MUX2 lab
  - Email me if you can not get into the lab
- Lab available 5-23 every day
  - Make sure to verify in schedule server if lab is available outside course schedule
  - MUX2 mostly used only for TSTE12
  - MUX1 also sometimes available (used more by other courses)
- Remote login: use thinlinc

# Project issues

- Expected project participation conduct
  - Do not be late to meetings
  - Inform the rest of the group if you have a problem attending a meeting (in advance if possible)
  - Keep track of your project work, noting amount and type of task
- Documents should be discussed and approved by supervisor
- Possible to fail project even if design works
- Possible for individual to fail project even if rest of group get a pass!

# Project hints

- Hints about Requirement specification
  - Possible subsystem: control, display, audio processing
  - Add plenty of features
  - Set priority (low, medium, high)
  - Avoid multiple requirements in one requirement statement
- Hints about design specification
  - Should indicate idea about general building blocks
    - Interfaces (signals/data to communicate)
    - Behavior

# Design flow and tools


- Three types of examined activities in the course
  - Handin
  - Lab
  - Project
- For handins (start next week): use simple text editor + modelsim
  - Start the TSTE12handin shell
  - Write code, compile, simulate, finally upload code
- Chapter 2 tutorial notes shows how to use modelsim  
<http://www.isy.liu.se/edu/kurs/TSTE12/kursmaterial/>

# HDL Designer tool

- Design entry tool, main entry tool to the project
  - Tutorial chapter 3 introduce this [www.isy.liu.se/edu/kurs/TSTE12/kursmaterial](http://www.isy.liu.se/edu/kurs/TSTE12/kursmaterial)
- Tools used to manage libraries, design, and other tools for use by larger designer groups
  - Graphic and text design entry
  - Tool startup configurations
  - Support many different languages and tools
  - Version control, team management....
- Highly configurable


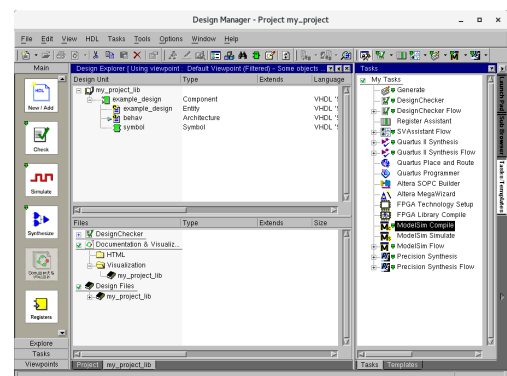
# HDL Designer tool, cont.

- Top level: The project
  - Defined by xxx.hdp file
  - Contains list of libraries, (1 or more)
- Each library contains design units
  - Described as components (green and blue boxes)
  - Each unit have different view
    - Graphic and/or textual
    - Various forms of architectures (text, block, FSM, ...)
    - A default architecture view is indicated by a blue arrow
- Interfaces with simulation and synthesis tools


 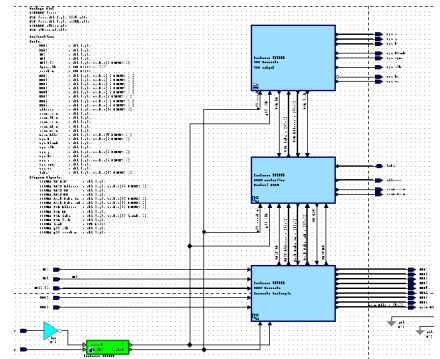
# HDL Designer tool, cont.

- Green boxes (components)
  - Fixed interface (does not automatically update)
  - Possible to reuse in multiple designs
- Blue boxes (subsystems)
  - Updates interface when adding/removing inputs/outputs in block diagram (remember to save schematic to update VHDL)
- Tools can generate valid VHDL from graphical representation (schematics, state machines, etc.)
- State machine example in lab3 lab material



# File I/O

- Possible to read or write a file (1993 allow both on same file)
- Formatted IO
  - Not generally human readable (platform dependent)
- TEXT IO
  - Human readable
- Special package includes definitions
  - STD.TEXTIO
  - Functions for open file, read a complete line, and read individual data from the line

# Later revisions

- Mostly simplifications and additional function support
  - 1993:
    - 8-bit ASCII, identifier restrictions relaxed, declarations simplifications
    - Shared variables (global variables outside processes).
    - Improved reporting in assert statements
  - 2008:
    - Simplified sensitivity lists (keyword all to include all signals used)
    - Simplified conditions, allow bit and std\_logic values as result of condition
    - Read of output ports on entity
  - Tools does not always support latest revision!
- 

# VHDL timing and concurrency

- Simulation of concurrent events (hardware) on a sequential computer
- Must have the same result from simulation independent of execution order of individual event
- Delay is an important property of hardware that must be simulated

## Signals vs Variables

- Electronic signals can not change values in 0 seconds
  - Always slopes on voltages going from 0 to 1
- Common sequential code assumes variables are updated before next statement is executed
- Expect different result depending on if variables or signals are used
- Both variables and signals can be used in synthesized code

## Signal vs Variable example

- Inputs with changing value at different times

X:	1	4	5	5	3
Y:	2	2	2	3	2
Z:	0	3	2	2	2
	initial	t1	t1+2	t1+4	t1+6

- Result depends on if signals or variables as assigned

AS <= X\*Y after 2 ns;

BS <= AS+Z after 2 ns;

AS:	2	2	8	10	15
BS:	2	2	5	10	12
	initial	t1	t1+2	t1+4	t1+6

AV := X\*Y;

BV := AV + Z;

AV:	2	8	10	15	6
BV:	2	11	12	17	8
	initial	t1	t1+2	t1+4	t1+6



## Signal assignment with delta delay

- Minimum delay is a delta delay
- Delta delay is  $> 0$  s but much smaller than the minimum timestep of the simulator

X:	1	4	4	4
Y:	2	2	2	2
Z:	0	3	3	3
initial		t1	t1+delta	t1+2*delta
AS	$\leq X*Y;$			
BS	$\leq AS+Z;$			
AS:	2	2	8	8
BS:	2	2	5	11

## Delta delay

- Can not be explicitly specified
- Delta delays will never add up to a simulation delay in seconds (standard time)
- Sometimes referred to as Macro (simulation time) and micro (delta delays) timing.
- Time may stand still in simulation by continuous signal updates
  - Example: process triggered by a signal that it is updating
  - Combinatorial loops without macro delay in assignments
  - Delta delay is increasing but not the simulation time

# Simulation models

- Delta delay only
  - Functional verification of models
- Standard time unit delay only
  - Validate system timing
- Mixed
  - Delta delay where delay is not important
  - Standard time unit delay where delay is significant
  - Study system timing

# VHDL timing

- Two types of time in VHDL
  - Variables: no delay in update
  - Signals: standard time delay and/or delta delay
- Delta delay
  - Never adds up to a standard time unit
  - Default delay when assigning signals unless delay is specified
- Known as macro and micro timing

# Timing implementation in simulation

- Simulator program flow
  - 1) If no entries in queue then stop, else increase time to next time entry in queue
  - 2) Start a new simulation cycle without advancing simulation time. Remove all entries scheduled for current simulation time, update all signals. Activate triggered processes
  - 3) Execute activated processes. Schedule new time queue entries.
  - 4) If there are new transactions on signals due to assignment with delta delay, then goto 2, otherwise goto 1
- Concurrent assignment can be seen as processes

# Unexpected simulation results

- Time may stand still in simulation by continuous signal updates
  - Example: process triggered by a signal that it is updating
  - Combinatorial loops without macro delay in assignments

# Simulation models

- Delta delay only
  - Functional verification of models
- Standard time unit delay only
  - Validate system timing
- Mixed
  - Delta delay where delay is not important
  - Standard time unit delay where delay is significant
  - Study system timing

# Example of models

- A simple buffer examples
  - All buffer have different propagation delay
  - Difference in delta delays are difficult to see in waveform windows
  - Possible to create multiple delta delay

```
Entity BUFF is
  port (X: in BIT; Z out BIT);
end;
```

```
Architecture ONE of BUFF is
  signal Y: BIT;
begin
  process(X)
    variable Y : BIT;
  begin
    Z <= X;
  end process;
end ONE;
```

```
architecture TWO of BUF is
  signal Y: BIT;
begin
  process(X)
  begin
    Y <= X;
  end process
  Z <= Y;
end TWO;
```

```
architecture THREE of BUF is
  signal Y1,Y2: BIT;
begin
  Y1 <= X;
  Y3 <= Y2;
  Y2 <= Y1;
  Z <= Y3;
end THREE;
```

## Example models, cont.

- Two almost identical buffers
  - Have very different simulation behaviour
  - Both probably generate same hardware in synthesis
- Lacking entries in sensitivity list
  - Solution: Always add all input signals to the sensitivity list
- Drawback: unnecessary process triggering may give slower simulation

```
Architecture FIVE of BUFF is
signal Y5: BIT;
begin
  process(X)
  begin
    Y5 <= X;
    Z <= Y5;
  end process;
end FIVE;
```

```
architecture FIVE_A of BUF is
signal Y5: BIT;
begin
  process(X, Y5)
  begin
    Y5 <= X;
    Z <= Y5;
  end process
end FIVE_A;
```

## Inertial and Transport delay

- Delay can be of two types (3 in VHDL93)
  - Inertial  $Z \leq I$  after 10 ns;
    - If input change again before end of delay then do not update output
    - Filter out short glitches (RC delay)
  - Transport  $Z \leq \text{transport } I$  after 10 ns;
    - “True” delay of signal (like transmission lines)
  - Reject (VHDL93)  $Q \leq \text{reject } 4 \text{ ns inertial } a$  after 10 ns;
    - $Q\_tmp \leq A$  after 4 ns;  $Q \leq Q\_tmp$  after 6 ns;

# Implementation of Inertial and Transport delay in simulator

- Important to understand why a signal change may not reach the assigned signal
- Transaction
  - Pair of value and time. What value when
- Waveform
  - A series of transactions (sorted by time value)
- Current value of driver
- Value of transaction whose time is not greater than current simulation time. Removed when simulation time is updated if next transaction time is reached

# Waveform update algorithm

1. All old transactions with time at or after earliest new transaction are deleted. Add new transactions to the waveform

If inertial then

- 2. Mark all new transactions
  - 3. Mark old transaction if it immediately precedes a marked transition and its value is the same as the marked transaction
  - 4. Mark the current value transaction
5. All unmarked transactions are removed

## Waveform update example

- $Z \leq I$  after 10 ns; (I is a 5 ns pulse starting at  $t=0$ )
- First change Z updated to '1' at  $t=0$ , (10,'1') transaction added
  - Both current and transaction marked and kept
- Second change, Z updated to '0' at  $t=5$ , (15,'0') transaction added
- If inertial: (10,'1') not marked, removed
- End result: the pulse on I is not visible on Z (filtered out)

## Inertial delay side effects

- Process for generating reset signal Res
  - Only executed once at start
  - First assignment is eliminated by second assignment
- Use transport or combined assignment to get pulse
  - Res  $\leq$  transport '1' after 50 ns;
  - Res  $\leq$  transport '0' after 100 ns;
- Generate complete waveform instead
  - Res  $\leq$  '1' after 50 ns, '0' after 100 ns;

```

Process
begin
  Res <= '1' after 50 ns;
  Res <= '0' after 100 ns;
  wait;
end process;
  
```

# Modeling of combinational and sequential logic

- Simple approach.
  - Process sensitivity list = circuit inputs
  - Compute new value using variables
  - Assign output signal with delay
  - Possible to synthesize (ignoring delay)
- Models uses generic in the port
  - Adds parameters to components without need of a signal
  - May have default values in entity declaration

# Combinational logic examples

- Gates
  - Generic states delay
  - May have default delay defined

```
entity NAND2 is
  generic(DEL: TIME);
  port(I1,I2: in BIT; O: out BIT);
end NAND2;
```

```
architecture DF of NAND2 is
begin
  O <= I1 nand I2 after DEL;
end DF;
```

```
architecture STRUCTURAL of ONES_COUNT is
```

```
component XOR_GATE
port (X,Y : in bit; O : out bit);
end component;
```

```
component NAND_GATE
Generic (DEL: TIME := 3 ns);
port (X,Y : in bit; O : out bit);
end component
```

```
signal I1, I2, I3 : bit;
```

```
begin
```

```
U1 : XOR_GATE port map(A(0),A(1),I1);
U2 : XOR_GATE port map(I1,A(2),C(0));
U3 : NAND_GATE generic map(5 ns)
      port map(A(0),A(1),I2);
U4 : NAND_GATE port map(A(2),I1,I3);
U5 : NAND_GATE port map(I2,I3,C(1));
```

```
end STRUCTURAL;
```



## Combinational logic examples, cont.

- Two-to-4 decoder
  - Set one of the four outputs to '1' based on the I input value

```
entity TWO_TO_4_DEC is
  generic(DEL: TIME);
  port(I: in BIT_VECTOR(1 downto 0);
        O: out BIT_VECTOR(3 downto 0));
end TWO_TO_4_DEC;

architecture ALG of TWO_TO_4_DEC is
begin
  process(I)
  begin
    case I is
      when "00" => O<= "0001" after DEL;
      when "01" => O<= "0010" after DEL;
      when "10" => O<= "0100" after DEL;
      when "11" => O<= "1000" after DEL;
    end case;
  end process;
end ALG;
```

## Sequential logic process template

- Must check both event and level to detect clock edge
  - Alternative functions available in the std\_logic libraries
    - rising\_edge, falling\_edge
- Do NOT do the following:
- This is acting as a flip-flop based design, but is synthesized to a latch based one!


```
process(clk, ...)
begin
  if <async expressions> then
    async behavior
  elsif clk'event and clk='1' then
    sync behavior
  endif
end process;
```

```
process(clk)
begin
  if clk='1' then
    sync behavior
  endif
end process;
```

```
process(clk)
begin
  if clk='1' then
    Q <= D;
  endif
end process;
```
 
## Sequential logic, cont.

- Latch
  - Latches missing the edge detection
  - Bad design style
  - Synthesis result not working
- Flipflop would only copy D when a positive edge on Clk



```
entity LATCH is
  generic(LATCH_DEL:TIME);
  port(D: in BIT_VECTOR(7 downto 0);
        CLK: in BIT;
        LOUT: out BIT_VECTOR(7 downto 0));
end LATCH;

architecture DFLOW of LATCH is
begin
  LATCH: process(clk,D)
  begin
    if (clk='1') then
      LOUT <= D after LATCH_DEL;
    end if;
  end process;
end DFLOW;
```

## Sequential logic

- JK flipflop with asynchronous set/reset
  - Edge triggered using 'event
  - Asynchronous update
    - Higher priority than clocked circuit function
  - Synchronous update
    - Note use of elsif (must be used)
    - Edge triggered using 'event

```
entity JKFF is
  generic(SRDEL,CLKDEL: TIME);
  port(S,R,J,K,CLK: in BIT;
        Q,QN: inout BIT);
end JKFF;
```

```
architecture ALG of JKFF is
begin
  process(CLK,S,R)
  begin
    if S = '1' and R = '0' then
      Q <= '1' after SRDEL;
      QN <= '0' after SRDEL;
    elsif S = '0' and R = '1' then
      Q <= '0' after SRDEL;
      QN <= '1' after SRDEL;
    elsif CLK'EVENT and CLK = '1' and
          S='0' and R='0' then
      if J = '1' and K = '0' then
        Q <= '1' after CLKDEL;
        QN <= '0' after CLKDEL;
      elsif J = '0' and K = '1' then
        Q <= '0' after CLKDEL;
        QN <= '1' after CLKDEL;
      elsif J = '1' and K = '1' then
        Q <= not Q after CLKDEL;
        QN <= not QN after CLKDEL;
      end if;
    end if;
  end process;
end ALG;
```

## Sequential logic, cont.

- Register with alternative design
  - Use a guarded statement
  - Use 'STABLE instead of 'EVENT

```
entity REG is
  generic(DEL: TIME);
  port(RESET,LOAD,CLK: in BIT;
        DATA_IN: in BIT_VECTOR(3 downto 0);
        Q: inout BIT_VECTOR(3 downto 0));
end REG;

architecture DF of REG is
begin
  REG: block(not CLK'STABLE and CLK ='1')
  begin
    Q <= guarded "0000" after DEL when RESET ='1' else
      DATA_IN after DEL when LOAD ='1' else
      Q;
  end block REG;
end DF;
```

## Output feedback problems

- Entity output can NOT be read in the architecture
- Three solutions
  - Use INOUT
    - Does not match OUT, enables output values to influence internal signal values
  - Use BUFFER
    - Does not match OUT, complicates building testbenches etc.
  - Use OUT with a temporary signal
    - use temporary signal everywhere needed (read and assign), assign entity out signal at the end of the architecture

# Sequential logic, oscillator

- Run signal indicate when to start generating clock pulses.
- Feedback example
  - Need extra variable to guarantee complete clock cycles
  - Simulation use only, will not synthesize

```
entity CLOCK_GENERATOR
  generic(PER: TIME);
  port(RUN: in BIT;
        CLK: out BIT);
end CLOCK_GENERATOR;
```

```
architecture ALG of CLOCK_GENERATOR is
  signal CLOCK: BIT;
begin
  process (RUN,CLOCK)
    variable CLKE: BIT := '0';
  begin
    if RUN='1' and not RUN'STABLE then
      CLKE := '1';
      CLOCK <= transport '0' after PER/2;
      CLOCK <= transport '1' after PER;
    end if;
    if RUN='0' and not RUN'STABLE then
      CLKE := '0';
    end if;
    if CLOCK='1' and not CLOCK'STABLE
      and CLKE = '1' then
      CLOCK <= transport '0' after PER/2;
      CLOCK <= transport '1' after PER;
    end if;
    CLK <= CLOCK;
  end process;
end ALG;
```

# Sequential logic, oscillator

- Wait statement based
  - Can not have both wait and sensitivity list in process

```
entity COSC is
  generic(HI_TIME,LO_TIME: TIME);
  port(RUN: in BIT; CLOCK: out BIT := '0');
end COSC;
```

```
architecture ALG of COSC is
begin
  process
  begin
    wait until RUN = '1';
    while RUN = '1' loop
      CLOCK <= '1';
      wait for HI_TIME;
      CLOCK <= '0';
      wait for LO_TIME;
    end loop;
  end process;
end ALG;
```

# Numeric calculations

- Bit-vectors (and `std_logic_vectors`) does not directly correspond to a value
  - "1011" could mean 11 in decimal (unsigned), or -5 in decimal (2's complement)
- Datatypes are included in supporting packages to enable arithmetic on bit-vectors
  - `ieee.numeric_bit.all`
  - `ieee.numeric_std.all`
- Must use defined types signed or unsigned to allow calculations
  - Same definitions as `bit_vector` and `std_logic_vector`
  - Can copy values between types due to same element type

# Numeric calculations example

- Counter incrementing 3-bit count value each clock cycle
  - Asynchronous reset

```
library ieee;
use ieee.numeric_bit.all;
```

```
entity INL3_KB is
port (
  C : in bit;
  R : in bit;
  Q : out bit_vector(1 to 3));
end entity;
```

```
architecture KB of INL3_KB is
begin
```

```
  process(C,R)
    variable count : unsigned(1 to 3);
  begin
    if R = '1' then
      count := (others => '0');
    elsif C'event and (C='1') then
      count := count + 1;
    end if;
    Q <= bit_vector(count);
  end process;
```

```
end architecture;
```

## Numeric calculations details

- Addition does not increment wordlengths
  - May get overflow
  - Must signextend to detect carry
- Adding different length vectors will sign extend the shortest one
  - May still get overflow
- Multiplication always generates an output number of bits equal to the total number of input bits
  - Multiplying a 3-bit input with a 4-bit input generates a 7-bit output result

101	0101
+011	+0011
-----	-----
000	1000

## Avoid old packages

- Before the introduction of `numeric_std` and `numeric_bit` there were other libraries
  - `std_logic_unsigned`, `std_logic_signed`
  - `std_logic_arith`
- Do NOT use these, they are obsolete
  - Made it difficult/impossible to mix signed and unsigned

# Including integers

- Integers can be used for synthesis
  - If synthesis tool cannot figure out the limits, the result is 32-bit arithmetic
  - Subtypes (limiting range) help to reduce hardware and catch unexpected use
- Integers will be implemented as bitvectors
  - Either unsigned or signed (2's complement)
  - Translation between integer and bitvectors exist
    - `x_signed := to_signed(y_int, x_signed'size);`
  - Translation other way around (unsigned to integer value)
    - `y_int = to_integer(x_signed);`

# Another aspect of signal assignment

- One signal can be assigned from different parts of the code
  - Support multiple entities driving the same wire
  - Example: Databus in a computer connecting multiple memories and CPU
- Modelling must be strict and clear
  - Same result independant of simulator tool
  - Should not be able to detect the order the processes where calculated
- Not all data types support multiple sources for the value

# Multiple assignment on one signal

- Each process containing a signal assignment will have a driver in the simulator generating a contribution to the final signal value
  - Concurrent signal assignments will have one driver each
  - Processes only have one driver for each signal (even with multiple assignment)
  - The signal update seen before is done individually on each driver
  - One driver does not know anything about other drivers
- When the value of a signal is fetched, the contributions from the different drivers current values are collected.
  - The resulting signal value depends on the definition of how to combine the values from the different drivers, using a resolution function

# Example of data types supporting multiple drivers

- Signals driven by multiple drivers must be resolved
  - Use a special function that resolves multiple drivers
- Resolution function
  - Example: Wired-OR
    - `signal X1 : WIRED_OR Bit;`
    - `subtype STD_LOGIC is RESOLVED STD_ULOGIC;`
    - `signal Y2 : STD_LOGIC;`
  - RESOLVED is the resolution function name
    - Called every time the value of the signal is calculated
    - Gets all driver values as input



## Multivalued logic

- Not enough with 0 and 1 to model “real” logic
- Example: Bus
  - Requires bus release
  - Signal assignment driver can not drop its value
  - Use a value to indicate not driven, and indicate non-driven signals (Z)
  - Need to indicate conflicting driver (X)

## Multivalued logic in VHDL

- Alternative to data type BIT

```
Type MVL4 is ('X', '0', '1', 'Z');
```

```
Type MVL4_VECTOR is array(NATURAL  
range <>) of MVL4;
```
- X leftmost to make it the initial value unless explicitly initialized in the code

## Multidriver signals

- Requires a resolution signal
- Different combinations possible
  - X always overrides others
  - 0 and 1 at the same time gives X
  - Z and Z gives Z

## Resolution function definition

Subtype DotX is wiredX MVL4;

- WiredX is the name of the resolution function

```
Function wiredX (V:MVL4_VECTOR)  
  return MVL4;
```

- Where V is a vector containing all values of all drivers of a signal

## Resolution function implementation

- Implement as a loop and lookup table

```
Function wiredX (V: MVL4_VECTOR) return MVL4 is
  Variable result: MVL4:= 'Z';
Begin
  For i in V'RANGE loop -- range not known in advance
    Result = table_WIREDX(result,V(i));
    Exit when result = 'X';
  End loop;
  Return result;
End wiredX;
```

## Resolution function impl., cont.

- Check of X in loop is not necessary, but speed up simulation
- Table should then look like:

```
Type MVL4_TABLE is array (MVL4, MVL4) of MVL4;
Constant table_WIREDX : MVL4_TABLE :=
--
--      X      0      1      Z
--
--      (('X', 'X', 'X', 'X'), -- X
--       ('X', '0', 'X', '0'), -- 0
--       ('X', 'X', '1', '1'), -- 1
--       ('X', '0', '1', 'Z')); -- Z
```

## Resolution function impl. Cont.

- Table lookup may be used for most functions
  - Not possible to know the order of the value in  $V$ , may therefore require a more complex algorithm