

10.2 A *latch* holds its digital value during one of the clock phases. During the other clock phase, it is transparent and propagates to input to the output.

There is never any transparency between the input and the output in the flip-flop.