

- A1.1) Represent a full adder at Behavioral/Functional and Structural Level
- A1.2) Apply decomposition to compute 8-point DFT by using radix-2 DFTs